

Home
Parts & Components
Test Gear
Mic PreAmps
IC OpAmps
Discrete OpAmps
Power Amplifiers
Power Supplies
Miscellaneous
Gerber Files
PCB Design
Gallery
About Me

Discrete OpAmps

Designing and building discrete operational amplifiers is a fascinating business for me. Although IC technology is pretty mature today there are still situations where discrete design beats ICs—typical advantages of discrete amplifiers are potentially high supply voltages, high maximum dissipation (e.g. class A output stages), much extended options with respect to choice of passive components and the possibility to tweak even the last bit of the amplifier for the task at hand. Here you'll find several schematics and links about this topic.

918 Discrete OpAmp

[918_documentation.pdf](#)

With the great help of Steven Hogan (www.soundsteward.com) and Larry Hathaway (www.jensen-transformers.com) I'm able to provide this unique documentation. The 918 was designed by Deane Jensen and is the predecessor of the famous 990.

SGA-SOA-1 Simple Discrete Operation Amplifier

[SGA-SOA-1_documentation.pdf](#)

A simple yet well performing and widely proven circuit designed by me. Provided with a 2520 style footprint and comprehensive documentation. Some [pictures](#) to check out. The typical specifications for $R_L = 600 \Omega$ and $V_{supply} = \pm 18 V$:

- Input offset voltage: < 20 mV
- Input bias current: $-1.1 \mu A$
- Input voltage noise: $1.5 nV/\sqrt{Hz}$ at 1 kHz
- Current noise density: $0.6 pA/\sqrt{Hz}$ at 1 kHz
- Open loop voltage gain: 80 dB
- Gain-bandwidth product: 30 MHz at 10 kHz
- Unity-gain bandwidth: 15 MHz
- Slew rate: $\pm 10 V/\mu s$
- Output swing: $\pm 17 V$
- Class A output drive: 600Ω for full voltage swing
- Maximum output current: $\pm 300 mA$
- Supply current: 21 mA (no load)

Gerber files for this design can be downloaded in the [Gerber files](#) section.

SGA-SOA-2 Simple Discrete Operation Amplifier

[SGA-SOA-2_r1.pdf](#)

The successor of the SGA-SOA-1 which is now fully tested. Improvements have been made mainly regarding slew-rate, gain-bandwidth product and CMRR; all this at the same parts count and quiescent current. The typical specifications for $R_L = 600 \Omega$ and $V_{supply} = \pm 18 V$:

- Input offset voltage: < 20 mV
- Input bias current: $-1.1 \mu A$
- Input voltage noise: $1.5 nV/\sqrt{Hz}$ at 1 kHz
- Current noise density: $0.6 pA/\sqrt{Hz}$ at 1 kHz
- Open loop voltage gain: 80 dB
- Gain-bandwidth product: 40 MHz at 10 kHz
- Unity-gain bandwidth: 15 MHz
- Slew rate: $\pm 14 V/\mu s$
- Output swing: $\pm 17 V$
- Class A output drive: 600Ω for full voltage swing
- Maximum output current: $\pm 230 mA$
- Supply current: 21 mA (no load)

R6 should be altered for lower supply voltages to maintain the 1.6 mA bias current through D3/D4. Suggested values are 18 k Ω ($\pm 15 V$), 15 k Ω ($\pm 12 V$) and 12 k Ω ($\pm 10 V$).

SGA-HVA-1 High Voltage Discrete Operational Amplifier

[SGA-HVA-1_r1.pdf](#)

A discrete opamp for high supply voltages, fully tested. This is a real general-purpose opamp which will perform very well in various implementations. The typical specifications for $R_L = 600 \Omega$ and $V_{\text{supply}} = \pm 40 \text{ V}$:

- Input offset voltage: $< 5 \text{ mV}$
- Input bias current: $-1.1 \mu\text{A}$
- Input voltage noise: $1.5 \text{ nV}/\sqrt{\text{Hz}}$ at 1 kHz
- Current noise density: $0.6 \text{ pA}/\sqrt{\text{Hz}}$ at 1 kHz
- Open loop voltage gain: 130 dB
- Gain-bandwidth product: 65 MHz at 10 kHz
- Unity-gain bandwidth: 10 MHz
- Slew rate: $\pm 21.7 \text{ V}/\mu\text{s}$
- Output swing: $+37.3/-37.5 \text{ V}$
- Class A output drive: $1.9 \text{ k}\Omega$ for full voltage swing
- Maximum output current: $+85/-95 \text{ mA}$
- Supply current: 18 mA (no load)

R_6 should be altered for lower supply voltages to maintain the 1.6 mA bias current through D_3/D_4 . Suggested values are $33 \text{ k}\Omega$ ($\pm 30 \text{ V}$), $27 \text{ k}\Omega$ ($\pm 24 \text{ V}$), $20 \text{ k}\Omega$ ($\pm 18 \text{ V}$), $16 \text{ k}\Omega$ ($\pm 15 \text{ V}$), $12 \text{ k}\Omega$ ($\pm 12 \text{ V}$) and $10 \text{ k}\Omega$ ($\pm 10 \text{ V}$).

SGA-LNA-1 Low Noise Discrete Operation Amplifier

[SGA-LNA-1_r1.pdf](#)

An opamp with very low voltage noise; typical applications include moving coil preamplifiers and noise measurement amplifiers. Stable at noise gains of about three and above. Fully tested. The typical specifications for $R_L = 600 \Omega$ and $V_{\text{supply}} = \pm 24 \text{ V}$:

- Input offset voltage: $< 10 \text{ mV}$
- Input bias current: $\pm 100 \text{ nA}$
- Input voltage noise: $0.5 \text{ nV}/\sqrt{\text{Hz}}$ at 1 kHz
- Current noise density: $1.7 \text{ pA}/\sqrt{\text{Hz}}$ at 1 kHz
- Open loop voltage gain: 80 dB
- Gain-bandwidth product: 145 MHz at 100 kHz
- Slew rate: $\pm 48 \text{ V}/\mu\text{s}$
- Output swing: $\pm 22 \text{ V}$
- Class A output drive: $1.4 \text{ k}\Omega$ for full voltage swing
- Maximum output current: $\pm 50 \text{ mA}$
- Supply current: 25 mA (no load)

SGA-JFA-1 JFET Discrete Operational Amplifier

[SGA-JFA-1_r1.pdf](#)

A discrete opamp with JFET input stage I'm currently working on. The JFET input pair is bootstrapped for good common-mode performance; for low distortion and high slew-rate a compensation scheme which includes the output stage is used. Can be used at lower supply voltages (down to about 20 V) without any circuit change. Higher supply voltages up to $\pm 40 \text{ V}$ are basically possible as well but care should be given to the heat dissipation of the circuit. The preliminary specifications for $R_L = 600 \Omega$ and $V_{\text{supply}} = \pm 30 \text{ V}$:

- Input offset voltage: $< 1 \text{ mV}$
- Input bias current: very low
- Input voltage noise: $1.5 \text{ nV}/\sqrt{\text{Hz}}$ at 1 kHz
- Current noise density: very low
- Open loop voltage gain: 130 dB
- Gain-bandwidth product: 12 MHz at 10 kHz
- Unity-gain bandwidth: 12 MHz
- Slew rate: $\pm 38 \text{ V}/\mu\text{s}$
- Output swing: $+27.9/-28.2 \text{ V}$
- Class A output drive: 900Ω for full voltage swing
- Maximum output current: $\pm 190 \text{ mA}$
- Supply current: 38 mA (no load)

SGA-HSA-1 High Speed Discrete Operational Amplifier

[SGA-HSA-1_r1.pdf](#)

A very high speed discrete opamp, under development. It achieves its exceptional speed by means of a heavily degenerated input stage, and a second stage with capacitive high-frequency level shifter (C4) to remove secondary slew-rate and settling time limitations. Noise and DC precision performance is necessarily reduced compared to my other designs, but still rather good

compared to some high-speed monolithic opamps. The preliminary specifications for $R_L = 600 \Omega$ and $V_{\text{supply}} = \pm 15 \text{ V}$:

- Input offset voltage: $< 30 \text{ mV}$
- Input bias current: $-3.3 \mu\text{A}$
- Input voltage noise: $4.7 \text{ nV}/\sqrt{\text{Hz}}$ at 1 kHz
- Current noise density: $1 \text{ pA}/\sqrt{\text{Hz}}$ at 1 kHz
- Open loop voltage gain: 130 dB
- Gain-bandwidth product: 45 MHz at 10 kHz
- Unity-gain bandwidth: 49 MHz
- Slew rate: approximately $\pm 450 \text{ V}/\mu\text{s}$
- Output swing: $+13.8/-13.1 \text{ V}$
- Class A output drive: $1.4 \text{ k}\Omega$ for full voltage swing
- Maximum output current: approximately $\pm 50 \text{ mA}$
- Supply current: 18 mA (no load)

NDFL-DOA-1 NDFL Discrete Operational Amplifier

[NDFL-DOA-1_r1.pdf](#)

An untested conceptual study implementing nested differentiating feedback loops as presented by Edward M. Cherry. As the shown design essentially uses two operational amplifiers in series the resulting open-loop gain is drastic. Some preliminary specifications for $R_L = 600 \Omega$ and $V_{\text{supply}} = \pm 18 \text{ V}$:

- Input offset voltage: $< 5 \text{ mV}$
- Input bias current: $-1.1 \mu\text{A}$
- Input voltage noise: $1.5 \text{ nV}/\sqrt{\text{Hz}}$ at 1 kHz
- Current noise density: $0.6 \text{ pA}/\sqrt{\text{Hz}}$ at 1 kHz
- Open loop voltage gain: 240 dB
- Gain-bandwidth product: 10 GHz at 10 kHz
- Unity-gain bandwidth: 13 MHz
- Slew rate: probably around $\pm 180 \text{ V}/\mu\text{s}$
- Class A output drive: 600Ω for full voltage swing
- Maximum output current: approximately $\pm 250 \text{ mA}$
- Supply current: 40 mA (no load)

Resources

[The Philbrick Archive](#)

Cool site with many pictures, datasheets and application notes from the grandfather of opamp manufacture.

[990-2007.pdf](#)

Sales brochure with a lot of information about the 990 discrete operational amplifier.

[JFET Opamp.PDF](#)

Paper by Fred Forssell about a JFET discrete opamp design.

www.eisenaudio.com/diy500/tables/opamps/

Good overview of discrete opamps for audio.

Terms Of Use

The designs described on these pages are not commercial in any way. This means that I do not sell PCBs, kits, or anything like that. It also means that any for-profit use of the information on these pages is strictly prohibited—you may not sell PCBs, kits (neither partial, nor complete) or finished (or unfinished) units of the designs on this site, without the express written consent of Samuel Groner/SG-Acoustics.

Disclaimer

Notice that all information, schematics, layouts etc. are supplied *as is*, and that I can in no way be held responsible for its accurateness, functionality or even safety. Samuel Groner/SG-Acoustics shall not be responsible and disclaims all liability for any loss, liability, damage (whether direct or consequential) or expense of any nature whatsoever, which may be suffered as a result of, or which may be attributable, directly or indirectly, to the use of or reliance upon any information, links or service provided through this website.