

2. SCHEMA ELECTRONICĂ

GX400 – un amplificator audio Hi-Fi de 400W - compact si performant

Not for commercial use! For DIY purposes only!

