

Project 499


validity of the earthing arrangement. If at all possible, the pc board published should be used, as departures from this design could seriously affect amplifier performance.

Commence construction by soldering all the resistors onto the circuit board with the exception of the four 0R22 output resistors. These effectively connect all the sources of the MOSFETs together and make it difficult to locate faults in the mounting of the MOSFETs. Solder the 1 W resistors slightly above the circuit board since these can become hot under certain conditions. The components marked with an asterisk on the circuit diagram are mounted on the rear of the pc board. They should be mounted close to the MOSFETs. Do not solder the resistors to the rear of the circuit board at this stage. These are best left until after the MOSFETs have been mounted.

Solder the capacitors onto the circuit board with the exception of those on the rear of the board and the two large

ALL 4 mm DIA.
MATERIAL 40 x 12 x 3 ALUMINIUM ANGLE EXTRUSION
Drilling details for the heatsink bracket assembly. All dimensions are in millimetres.
Suitable aluminium angle stock is available from Alcan Handyman stores.

BRACKET DRILLING DETAILS

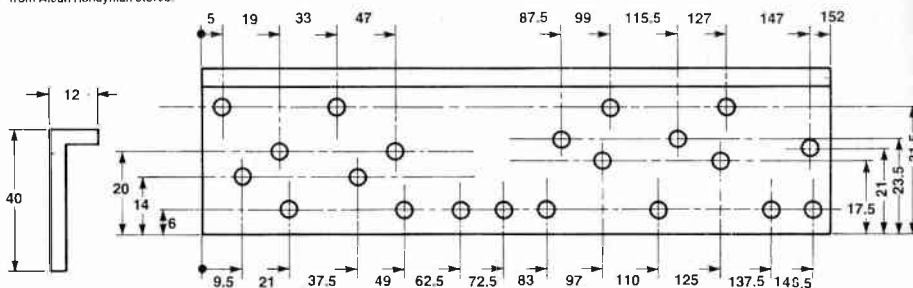

electrolytics. The 100u capacitor C3 is the only other electrolytic, so be careful with the orientation of this component. The capacitor is marked to indicate which of its leads are to be connected to a positive or negative voltage. Check the correct orientation on the overlay diagram. This also applies to the diodes and zener diodes used in the circuit, which can be mounted next.

Both the driver and power transistors are mounted on a length of aluminium angle extrusion, which is bolted to the pc board by bolts through the transistor mounting holes. This is shown in the accompanying diagrams. The extrusion is used to conduct the heat generated by the output and driver transistors to the heatsink, which will also be bolted to the extrusion. If you purchase the mod-

PARTS LIST — ETI-499

Resistors all 1/2 W, 5% unless stated

R1, R2	100k
R3, R11	1k
R4, R5, R18-R21	220R
R6, R7	3k9
R8	22k
R9	680R
R10	10k
R12, R15, R16, R17	100R
R13	33k
R14	10k 1 W
R22-R25	0R22 W
R26	4R7 1 W
R27	1R 1 W
RV1	100R preset
RV2	250R preset

Capacitors

C1, C9	220n greencap
C2	2n2 greencap
C3	100u/25 V electrolytic
C4	33p ceramic

C5	6n8 greencap
C6, C8	330p ceramic
C7	47n greencap
C10, C11	100n greencap
C12, C13	8000u/75 V electrolytic

Semiconductors

Q1, Q2, Q3	BC546
Q4, Q5	BF470
Q6, Q7	BF469
Q8, Q9	2SK134 Hitachi
	MOSFET
Q10, Q11	2SJ49 Hitachi
	MOSFET
D1-D4	1N914
D5-D8	1N5404
ZD1, ZD2	12 V 400 mW zener

Miscellaneous

ETI-499 pc board; plastic bobbin (from P26/16 potcore or similar); 5 A fuse (speaker fuse, not

mounted on pc board); fuse holder; 1 m of 0.8 mm enamel-covered copper wire; 155 mm length of aluminium extrusion, 40 mm x 12 mm, for use as the heatsink bracket; assorted nuts and bolts, hookup wire, etc; two solder lugs.

Price estimate

We estimate the cost of purchasing all the components for this project will be in the range:

\$75-\$85

(heatsink & transformer extra)

Note that this is an **estimate** only and **not** a recommended price. A variety of factors may affect the price of a project, such as — quality of components purchased, type of pc board (fibreglass or phenolic base), type of front panel supplied (if used), etc — whether bought as separate components or made up as a kit.

