

*Fig. 1. Suggested amended circuit for 8 or 15Ω, use employing a simplified power supply. The dotted components reduce the h.f. response and should be used with capacitive loads.*