



**FIGURE 9**

Excessive lead lengths not only reduce the resonant frequency of paralleled capacitors (A), but can also nullify the effects of the added parallel capacitor (B).