

Measurement

## LED Audio Clipping Indicator

**Measurement** | [Previous Circuit](#) | [Next Circuit](#) |

**Detects clipping in preamp stages, mixers and amplifiers.**

This circuit was intended to be used as a separate, portable unit, to signal by means of a LED when the output wave form of a particular audio stage is "clipping" i.e. is reaching the onset of its maximum permitted peak-to-peak voltage value before an overload is occurring. This will help the operator in preventing severe, audible distortion to be generated through the audio equipment chain.


This unit is particularly useful in signaling overload of the input stages in mixers, PA or musical instruments amplification chains, but is also suited to power amplifiers.

A careful setting of Trimmer R5 will allow triggering of the LED with a wide range of peak-to-peak input voltages, in order to suit different requirements. Unfortunately, an oscilloscope and a sine wave frequency generator are required to accurately setup this circuit.

Obviously, the unit can be embedded into an existing mixer, preamp or power amplifier, and powered by the internal supply rails in the 9 - 30V range.




**Clipping indicator schematic diagram**

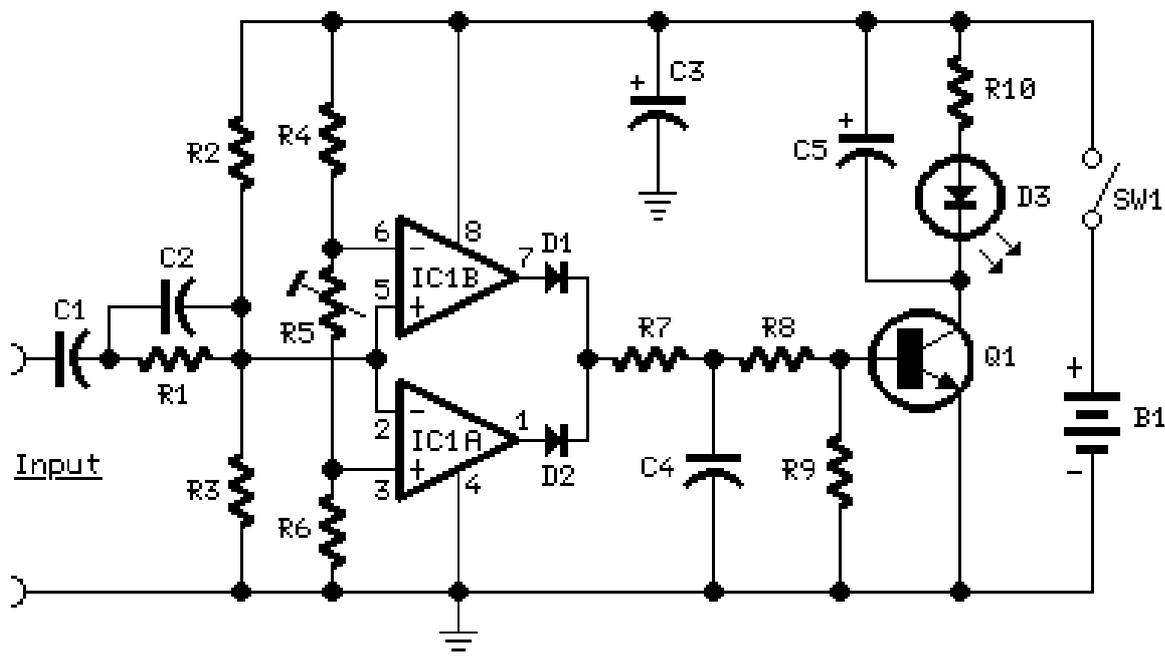

The heart of the circuit is a window comparator formed by two op-amps packaged into IC1. This technique allows to detect precisely and symmetrically either the positive or negative peak value reached by the monitored signal. The op-amps outputs are mixed by D1 and D2, smoothed by C4, R7 and R8, and feed the LED driver Q1 with a positive pulse. C5 adds a small output delay in order to allow detection of very short peaks.

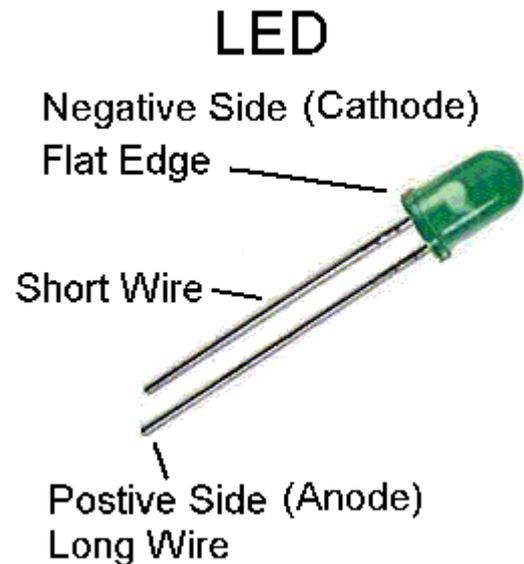
### Parts:

- R1 1M 1/4W Resistor (See Notes)
- R2 100K 1/4W Resistor
- R3 100K 1/4W Resistor
- R4 10K 1/4W Resistor
- R5 5K 1/2W Trimmer Cermet or Carbon
- R6 10K 1/4W Resistor
- R7 2K2 1/4W Resistor
- R8 100K 1/4W Resistor
- R9 22K 1/4W Resistor
- R10 1K 1/4W Resistor (See Notes)
- C1 220nF 63V Polyester Capacitor
- C2 4p7 63V Ceramic Capacitor (See Notes)
- C3 220 $\mu$ F 25V Electrolytic Capacitor
- C4 220nF 63V Polyester Capacitor
- C5 10 $\mu$ F 25V Electrolytic Capacitor (See Notes)
- D1 1N4148 75V 150mA Diode
- D2 1N4148 75V 150mA Diode
- D3 LED (Any dimension, shape and color)
- Q1 BC547 45V 100mA NPN Transistor
- IC1 TL062 Dual Low current BIFET Op-Amp or TL072, TL082
- SW1 SPST Toggle or Slide Switch (See Text)
- B1 9V PP3 Battery (See Text)


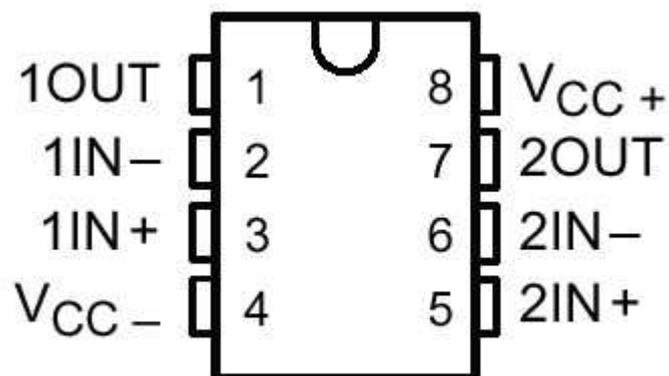
### Notes:

- With the values shown, the circuit can be easily set up to detect sine wave clipping from less than 1V to 30V peak-to-peak (i.e. 15W into 8 Ohms). If you need to detect higher output peak-to-peak voltages, R1 value must be raised. On the contrary, if the circuit will be used to detect only very low peak-to-peak voltages, it is convenient to lower R1 value to, say, 220K omitting C2. In this way, the adjustment of R5 will be made easier.



- Using a TL062 chip at 9V supply, stand-by current drawing is about 1.5mA and less than 10mA when the LED illuminates. With TL072 or TL082 chips, current drawing is about 4.5mA and 13mA.
- When using power supplies higher than 12V, the value of R10 must be raised.
- When using power supplies higher than 25V, the working voltage value of C5 must be raised to 50V.

- - [Electronic circuits](#)
  - [22 Watt Audio Amplifier](#)
  - [LED Audio Clipping Indicator](#)
  - [Resistor Color Code Calculator](#)
  - [2x20 Watt Hi-Fi Stereo Amp](#)
  - [USB Powered mini Amplifier](#)
  - [1W BTL Audio Amplifier](#)
  - [3 Channel Audio Mixer](#)
  - [Laptop Audio Amplifier](#)
  - [NE5532 Headphone Amplifier](#)
  - [LM317 Power Amplifier](#)
  - [Simple microphone preamplifier](#)
  - [Audio Spectrum Analyzer](#)
  - [Ambient Power Module](#)
  - [LED Solar Garden Lights](#)
  - [20 Watt Class-A Power Amp](#)
  - [Bipolar Stepper Motor Controller](#)
  - [Car-Stereo LED Power Meter](#)
  - [LM386 Amplifier](#)
  - [Class AB Power Amplifier](#)
  - [MC3479 Stepper Controller](#)
  - [Electronic Schematic Symbols](#)
  - [Manually Operated Digital Pot](#)
  - [WEBENCH Designer](#)
  - [Simple FM Transmitter](#)
  - [Computer Fan Controller DIY](#)
  - [Temperature regulated Fan Controller](#)
  - [Arduino](#)
  - [Arduino DAC solutions](#)

Google Translate

Select Language

 Gadgets powered by Google

 US 2,828	 CA 482
 IN 876	 DE 444
 ID 608	 GB 425
 PH 608	 RS 348
 RO 547	 IT 306

 FLAG counter

- [Live Traffic Feed](#)

### Unlimited DOMAINS

A visitor from Moldova, Republic of arrived from [google.md](#) and viewed "[LED Audio Clipping Indicator | Measurement](#)" 0 secs ago

A visitor from Saint Petersburg, Saint Petersburg City arrived from [google.com](#) and viewed "[NE5532 Headphone Amplifier | Audio Amplifier](#)" 17 mins ago

A visitor from Banja Luka, Republika Srpska arrived from [google.ba](#) and viewed "[Audio Spectrum Analyzer | Measurement](#)" 57 mins ago

A visitor from Manama, Al Manamah viewed "[Temperature regulated Fan Controller | Measurement](#)" 58 mins ago

A visitor from Jakarta, Jakarta Raya arrived from [google.com](#) and viewed "[USB Powered mini Amplifier | Audio Amplifier](#)" 1 hour 9 mins ago

A visitor from Linz, Oberosterreich arrived from

CPM



Powered by [LifeType](#) and [Blog.rs](#). © 2012. Electronic circuits. All rights reserved.  
We do not take any responsibility and we are not liable for any damage  
caused through use of products, schematic, software or services from this website.



[Outsourcing Services?](#) Try [Freelancer.com](#).

[Testing of Outsourcing Marketplace Website built on PHP](#)

A freelance with excellent skills in PHP, jquery, java is

[Project For Anamul Haque Do Not Bid Others Freelancer](#)

No activities may put the site at risk of punishment by

[Losing money with Adsense?](#)

Display job classifieds instead and make great money! Start earning big

[Inspiration Blog - repost](#)

Proyek yang saya tawarkan adalah penulisan blog mengenai sesuatu hal yang bisa membuat seseorang

required to run a quick test on an Testing of Outsourcing Marketplace Website built on PHP... Jobs: PHP, Software Testing, Testing / QA, Usability Testing, Website Testing, Budget: \$30 - \$250 [Bid on this project](#) - ends in 6d 22h 56m

Google.nnWe need: - 2000 facebook likes total... Jobs: Facebook, Internet Marketing, Social Networking, Twitter, Budget: \$155 - \$155 [Bid on this project](#) - ends in 6d 22h 55m

money with FreelancerCash. Get going in just only a few minutes. Our great affiliate program is the best way to monetize traffic. [Click here to signup now!](#)

merasa terinspirasi dengan postingan blog ini... Jobs: Article Rewriting, Articles, Blog, Creative Writing, Medical Writing, Budget: \$250 - \$750 [Bid on this project](#) - ends in 6d 22h 54m

[Freelancer.com](#) is #1 for [crowdsourcing!](#)