

An Easier Implementation of a 4th order State-Variable Active Filter

Johannes Linkels

November 2024

Contents

1	Introduction	3
2	4th order Linkwitz-Riley compared to Butterworth	3
3	4th order transfer function	4
4	Implementation	6
5	Circuit synthesis	7
5.1	Calculations	7
5.2	Example	8
6	Switch between Linkwitz-Riley or Butterworth	9
7	Simulation	9
8	The actual circuit	12
9	Measurement	16

1 Introduction

This document describes the analysis and design of a 4th order State Variable filter with either a Linkwitz-Riley transfer characteristic or a Butterworth characteristic.

A State Variable filter is a very elegant solution if a filter with both high-pass and low-pass outputs at the same cut-off frequency are required, like in audio active cross-over applications. Because both frequencies are equal by design, component selection or frequency adjustment becomes quite easy. Deviations of 5-10% of a cross-over frequency do not usually have any effects on performance as an audio filter.

The contents relies heavily on a technical paper written by Janne Ahonen: "The analysis of fourth-order state variable filter and its application to Linkwitz-Riley filters" [1]. However, the circuit design described in that paper is somewhat complicated due to interdependencies of components in the feedback loop.

The analysis as described here uses a different approach with an active inverter element in the feedback loop. This allows for very easy adjusting the gain and Q of the filter. In addition it is demonstrated that the LR characteristic can easily be converted to a 4th order Butterworth filter.

This design does not offer any better performance than Ahonen's design. It is also questionable if the more complicated synthesis actually is such a burden given the today's available calculation applications. For me it was just fun to see if it could be done.

I should emphasize that without the paper of Ahonen, I would not have been able to understand the analysis of the 4th order State Variable filter, and hence I could not have changed the design to something easier to implement.

2 4th order Linkwitz-Riley compared to Butterworth

An electronic filter circuit is broadly characterized by its characteristic or Q, cut-off frequency ω_0 , its category (low-pass, high pass, etc) and its order. Common for all filters is that *by definition* the attenuation is $-3dB$ at the cut-off frequency.

This also holds for a 4th order filter other than Linkwitz-Riley. Despite of the attenuation of $24dB/oct$ the attenuation at the defined ω_0 still is $3dB$.

However, the 4th order Linkwitz-Riley filter has a defined attenuation of $6dB$ at ω_0 . This is preferable for audio applications¹ and enables simple cascading of two 2nd order Butterworth filters with an equal Q of 0.707 each, yielding an attenuation of $6dB$ at ω_0 .

The design of the 4th order State Variable filter in this report describes both options, a 4th order Butterworth with $3dB$ attenuation at ω_0 and a 4th order Linkwitz-Riley with $6dB$ attenuation at ω_0 .

¹More specific for loudspeaker active crossover filters. Since the resulting sound pressure level of two speakers driven in phase is summed, the attenuation for each driver should be $6dB$ at the crossover frequency.

The 4th order Butterworth is formed by changing the Q's of each 2nd order transfer functions to an appropriate value.

Since the Linkwithz-Riley filter is considered optimal for analog audio applications, the 4th order Butterworth is not intended as an alternative, but it might be applicable in other applications.

3 4th order transfer function

Note: Equations 1 thru 4 are copied from [1]

The transfer function $H(s)$ for a 2nd order high pass filter is:

$$H_{hp2}(s) = \left(\frac{Ks^2}{s^2 + s \left(\frac{\omega_0}{Q} \right) + \omega_0^2} \right) \quad (1)$$

A 4th order filter can be synthesized by cascading two 2nd order filters. For the transfer function is obtained by multiplying two 2nd order functions:

$$H_{hp4}(s) = H_{hp2}(s) \cdot H_{hp2}(s) = \left(\frac{K_1 s^2}{s^2 + s \left(\frac{\omega_{01}}{Q_1} \right) + \omega_{01}^2} \right) \cdot \left(\frac{K_2 s^2}{s^2 + s \left(\frac{\omega_{02}}{Q_2} \right) + \omega_{02}^2} \right) \quad (2)$$

$$H_{hp4}(s) = \frac{K_1 K_2 s^4}{s^4 + s^3 \left(\frac{\omega_{01}}{Q_1} + \frac{\omega_{02}}{Q_2} \right) + s^2 \left(\omega_{01}^2 + \frac{\omega_{01}\omega_{02}}{Q_1 Q_2} + \omega_{02}^2 \right) + s \left(\frac{\omega_{01}^2 \omega_{02}}{Q_1} + \frac{\omega_{01}\omega_{02}^2}{Q_2} \right) + \omega_{01}^2 \omega_{02}^2} \quad (3)$$

This transfer function can be simplified by these assumptions:

$$\omega_{01} = \omega_{02} = \omega_0$$

$$K_1 = K_2 = K$$

but deviating from the design by Ahonen Q_1 and Q_2 are not made equal to keep the option for a Butterworth filter.

$$H_{hp4}(s) = \frac{K K s^4}{s^4 + s^3 \left(\frac{\omega_0}{Q_1} + \frac{\omega_0}{Q_2} \right) + s^2 \left(\omega_0^2 + \frac{\omega_0 \omega_0}{Q_1 Q_2} + \omega_0^2 \right) + s \left(\frac{\omega_0^2 \omega_0}{Q_1} + \frac{\omega_0 \omega_0^2}{Q_2} \right) + \omega_0^2 \omega_0^2} \quad (4)$$

and further reduced to:

$$H_{hp4}(s) = \frac{K^2 s^4}{s^4 + s^3 \left(\frac{(Q_1+Q_2)\omega_0}{Q_1 Q_2} \right) + s^2 \left(\frac{(2Q_1 Q_2 + 1)\omega_0^2}{Q_1 Q_2} \right) + s \left(\frac{(Q_1+Q_2)\omega_0^3}{Q_1 Q_2} \right) + \omega_0^4} \quad (5)$$

To obtain an expression for a high pass output, the definition of the transfer function is used:

$$H_{hp4}(s) = \frac{U_{hp}(s)}{U_{in}(s)} \quad (6)$$

By cross multiplying the nominator and denominator with U_{in} and U_{hp} :

$$U_{hp}(s) \left(s^4 + s^3 \left(\frac{(Q_1 + Q_2) \omega_0}{Q_1 Q_2} \right) + e^2 \left(\frac{(2Q_1 Q_2 + 1) \omega_0^2}{Q_1 Q_2} \right) + s \left(\frac{(Q_1 + Q_2) \omega_0^3}{Q_1 Q_2} \right) + \omega_0^4 \right) = U_{in}(s) K^2 s^4 \quad (7)$$

Then divide both sides by s^4 :

$$U_{hp}(s) \left(1 + \left(\frac{(Q_1 + Q_2) \omega_0}{Q_1 Q_2} \right) \frac{1}{s} + \left(\frac{(2Q_1 Q_2 + 1) \omega_0^2}{Q_1 Q_2} \right) \frac{1}{s^2} + \left(\frac{(Q_1 + Q_2) \omega_0^3}{Q_1 Q_2} \right) \frac{1}{s^3} + \frac{\omega_0^4}{s^4} \right) = U_{in}(s) K^2 \quad (8)$$

The State-Variable filter is synthesized using a summing circuit, and number of integrators which voltage is used for feedback with various attenuation factors. After reworking equation 8 the desired form is obtained:

$$U_{hp}(s) = U_{in}(s) K^2 - \frac{(Q_1 + Q_2)}{Q_1 Q_2} \left(\frac{\omega_0}{s} U_{hp}(s) \right) - \frac{(2Q_1 Q_2 + 1)}{Q_1 Q_2} \left(\frac{\omega_0^2}{s^2} U_{hp}(s) \right) - \frac{(Q_1 + Q_2)}{Q_1 Q_2} \left(\frac{\omega_0^3}{s^3} U_{hp}(s) \right) - \frac{\omega_0^4}{s^4} U_{hp}(s) \quad (9)$$

This form can easily be converted into a block diagram as in figure 1.

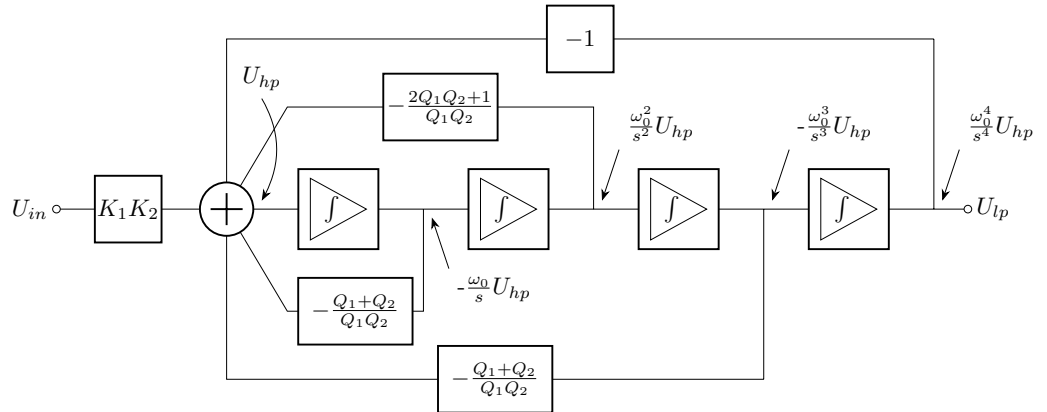


Figure 1: Block diagram of a 4th order State Variable filter

Recalling equation 5 for the transfer function of a high-pass filter we can now write out the transfer function of the output of the fourth integrator in equation

10:

$$\begin{aligned}
U_{lp} &= U_{hp} \cdot \frac{\omega_0}{s^4} \\
&= \frac{K^2 s^4}{s^4 + s^3 \left(\frac{(Q_1+Q_2)\omega_0}{Q_1 Q_2} \right) + s^2 \left(\frac{(2Q_1 Q_2 + 1)\omega_0^2}{Q_1 Q_2} \right) + s \left(\frac{(Q_1+Q_2)\omega_0^3}{Q_1 Q_2} \right) + \omega_0^4} \cdot \frac{\omega_0^4}{s^4} \\
&= \frac{K^2 \omega_0}{s^4 + s^3 \left(\frac{(Q_1+Q_2)\omega_0}{Q_1 Q_2} \right) + s^2 \left(\frac{(2Q_1 Q_2 + 1)\omega_0^2}{Q_1 Q_2} \right) + s \left(\frac{(Q_1+Q_2)\omega_0^3}{Q_1 Q_2} \right) + \omega_0^4}
\end{aligned} \tag{10}$$

This indeed is the expression for a 4th order low pass filter.

4 Implementation

When the block diagram as in figure 1 is straightforwardly implemented a circuit as proposed by Ahonen results, figure 2.

The problem here is that the integrator outputs for the first and third order integrations $\frac{1}{s}$ and $\frac{1}{s^3}$ already are inverted with respect to the input signal and U_{hp} . Subtracting these signals from the input signal U_{in} means that they have to be added in the summing stage by connecting them to the non-inverting input of the summing opamp OP1.

The non-inverting input of the opamp has a very high input impedance, hence the voltage at this summing point is a superposition of the input voltage and the two feedback signals. Every change in one of the resistors connected to this summing point will affect the amplification of all three signals. But this, in turn, means that every change in the feedback constants affects the other feedback constant as well as the overall gain of the input stage,

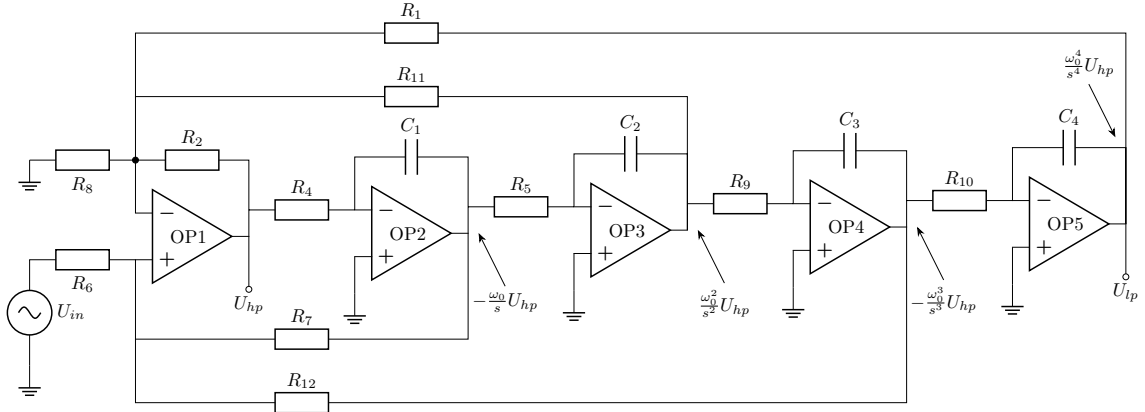


Figure 2: Implementation using the non-inverting input of the summing amplifier as summing point

The complexity of calculating the resistors in the non-inverting path can be overcome by adding one additional inverting amplifier OP6, figure 3. This

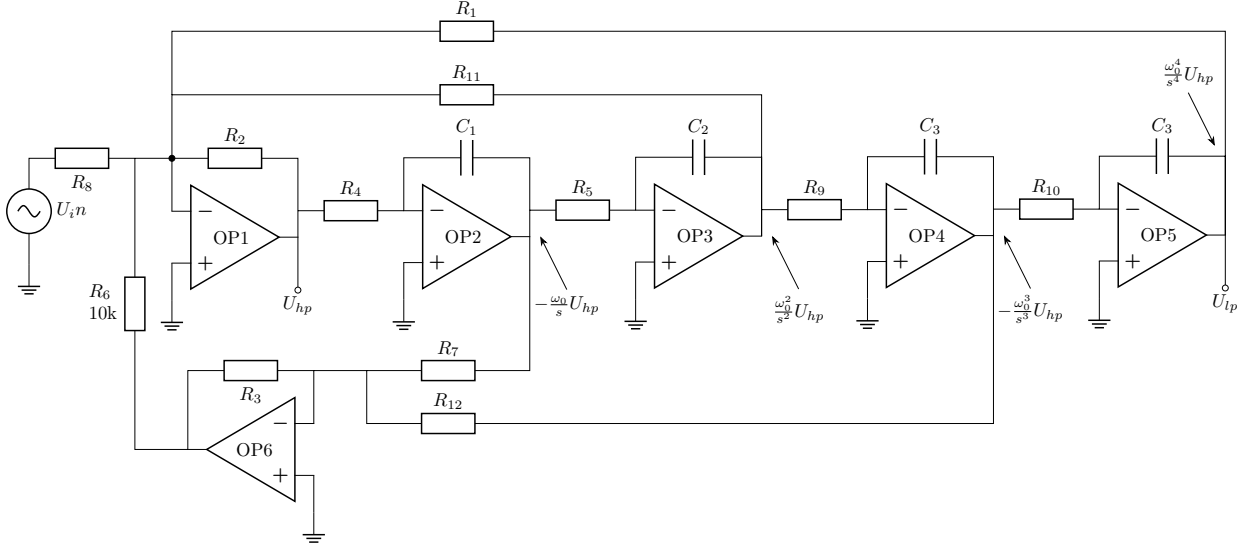


Figure 3: *Implementation with an additional inverter*

amplifier inverts the phase of the $\frac{1}{s}$ and $\frac{1}{s^3}$ terms. In this way these signals can be added to the inverting input of the summing amplifier.

Both terms have to be feed back to the summing amplifier with a gain of $\frac{Q_1+Q_2}{Q_1Q_2}$ so the gain of the inverter must be set to this value. The output signal of the inverter is summed with unity gain in the summing amplifier.

The signal input has also been moved to the inverting input of the summing amplifier. It is mandatory that the source has a low output impedance.

5 Circuit synthesis

5.1 Calculations

The component designation is according to figure 3.

When determining the component values it is assumed that R_2 is chosen first. This determines the gain of the summing amplifier. The value is not critical and values for the other resistors used for summation are derived using this value.

R_8 : gain K^2 :

$$K^2 = \frac{R_2}{R_8} \Rightarrow R_8 = \frac{R_2}{K^2} \quad (11)$$

R_6, R_3, R_7, R_{12} Gain of the inverting amplifier OP6 and feedback constant for $\frac{1}{s}$ and $\frac{1}{s^3}$: R_6 is set equal to R_2 so gain of this amplifier must be:

$$\frac{Q_1 + Q_2}{Q_1 Q_2} \quad (12)$$

The feedback constant for both $\frac{1}{s}$ and $\frac{1}{s^3}$ is equal. By choosing an arbitrary value for R_7, R_{12} the value for R_3 can be calculated.

$$\frac{R_3}{R_7, R_{12}} = \frac{Q_1 + Q_2}{Q_1 Q_2} \Rightarrow R_3 = R_7, R_{12} \frac{Q_1 + Q_2}{Q_1 Q_2} \quad (13)$$

R_1 : Feedback constant for $\frac{1}{s^4}$ The feedback constant is -1 so the value for R_1 is equal to R_2 .

R_{11} : Feedback constant for $\frac{1}{s^2}$ The feedback constant for this branch is:

$$\frac{R_2}{R_{11}} = \frac{2Q_1 Q_2 + 1}{Q_1 Q_2} \Rightarrow R_{11} = R_2 \frac{Q_1 Q_2}{2Q_1 Q_2 + 1} \quad (14)$$

$R_4, C_1; R_5, C_2; R_9, C_3; R_{10}, C_4$ corner frequency ω_0 Each RC pair sets the integrator time constant

$$RC = \frac{1}{\omega_0} = \frac{1}{2\pi f_0} \quad (15)$$

The time constant must be equal for all integrator stages.

5.2 Example

In this example corner frequency is set at $f_0 = 185Hz$ and transfer characteristic is Linkwitz-Riley.

$$\omega_0 = 2\pi \cdot f_0 = 2\pi \cdot 185 = 1162rad^{-1}$$

Usually for capacitors less standard values are available than for resistors. In this case C1-C4 are set at 220nF.

$$RC = \frac{1}{\omega_0} \Rightarrow R = \frac{1}{1167 \cdot 220 \cdot 10^{-9}} = 3895\Omega$$

R_4, R_5, R_9 and R_{10} are set at $3.9k\Omega$

The value R_2 is quite arbitrary and normal design rules for opamp summing amplifiers should be followed. Here $R_2 = 10k\Omega$ is chosen.

For the application this circuit was built for a gain of approximately 10dB was needed. A gain of 10dB is a gain factor of $10^{\frac{10}{20}}$ or approximately 3.2 times. From equation 11 we recall:

$$R_8 = \frac{R_2}{K^2} \Rightarrow R_8 = \frac{10 \cdot 10^3}{3.2} = 3.12k\Omega$$

A standard value of $3.3k\Omega$ will suffice

The value for R_6 is equal to R_2 , in this case also $10k\Omega$

The gain factor for the feedback circuit through OP6 is set to unity by choosing $R_6 = R_1 = 10k\Omega$.

To determine R_3 first R_7 and R_{12} must be chosen. These values are non-critical and chosen is $R_7 = R_{12} = 10k\Omega$.

This example is for a Linkwitz-Riley characteristic, hence $Q_1 = Q_2 = 0.707$. Then from equation 13:

$$R_3 = R_7, R_{12} \frac{Q_1 + Q_2}{Q_1 Q_2} \Rightarrow R_3 = 10 \cdot 10^3 \frac{0.707 + 0.707}{0.707 \cdot 0.707} = 28.4k\Omega$$

This value is critical and for actual circuit implementation the value must be chosen as close to this value as possible. For the simulation this exact value was used.

R_{11} from equation 14

$$R_{11} = R_2 \frac{Q_1 Q_2}{2Q_1 Q_2 + 1} = 10 \cdot 10^3 \frac{0.707 \cdot 0.707}{0.707 + 0.707} = 2.5k\Omega$$

6 Switch between Linkwitz-Riley or Butterworth

As mentioned previously in paragraph 3 if Q_1 and Q_2 are both 0.7 the 4th order filter behaves as 2 cascaded Butterworth filters. However Q_1 and Q_2 can be set to the values which make up a real Butterworth 4th order filter with an attenuation of 3dB at f_0 .

From [3] we get the values $Q_1 = 0.543$ and $Q_2 = 1.31$ for 2 cascaded 2nd order filters with a Butterworth transfer characteristic. To change the filter circuit, remarkable few changes have to be made. In table the Q-values, feedback constants and resistor values have been summarized.

	Q_1	Q_2	$\frac{Q_1+Q_2}{Q_1 Q_2}$	$\frac{2Q_1 Q_2+1}{Q_1 Q_2}$	R_8	R_{10}
Butterworth	0.543	1.31	2.60	3.40	2.93k	26 k
Linkwitz-Riley	0.707	0.707	2.84	4.00	2.50k	28.4 k

Table 1: *Q-values and feedback constant for Butterworth and Linkwitz-Riley variants*

Unfortunately only Linkwitz-Riley and Butterworth filter characteristic have two 2nd order sections which have the same cutoff frequency f_0 . For other characteristics both Q_1 and Q_2 are different *and also* ω_{01} and ω_{02} from equation 3 are different. For implementation that would incur multiple integrator chains with multiple corner frequencies f_0 . While certainly doable, it would void the elegance and simplicity of this circuit.

7 Simulation

The circuit of figure 3 has been entered in QUCS-S [2] and simulated. The QUCS diagram is according to the drawing on page 11. For the initial runs the theoretical resistance values from table 1 were used to prove the concept. A final run was made using the practical resistor values which were used to built the circuit with a Linkwitz-Riley characteristic. Although the State-Variable filter is not extremely sensitive to component tolerances, nevertheless seemingly small

deviations from the theoretical values have a noticable impact. The Butterworth and Linkwitz-Riley response using the theoretical values are shown in 4 and 5. The signal levels and y-scales of the graphs have been modified to be the same as for the actual measurements. The reference level is set at $-47dB$ to accomodate for the reference level in the real measurement.

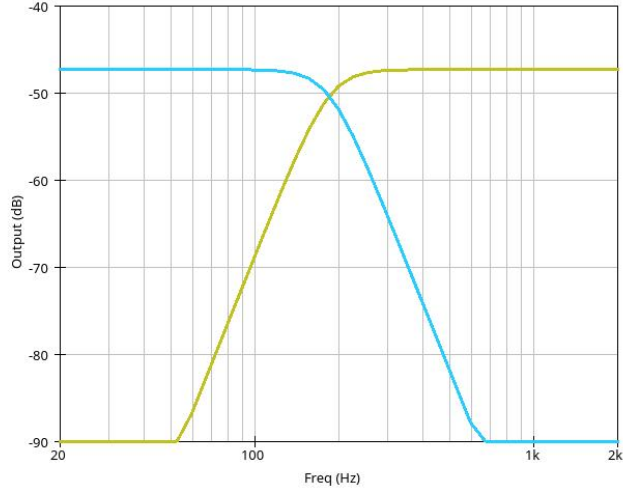


Figure 4: *Simulated transfer characteristic Butterworth adjustment $f_0 = 185Hz$*


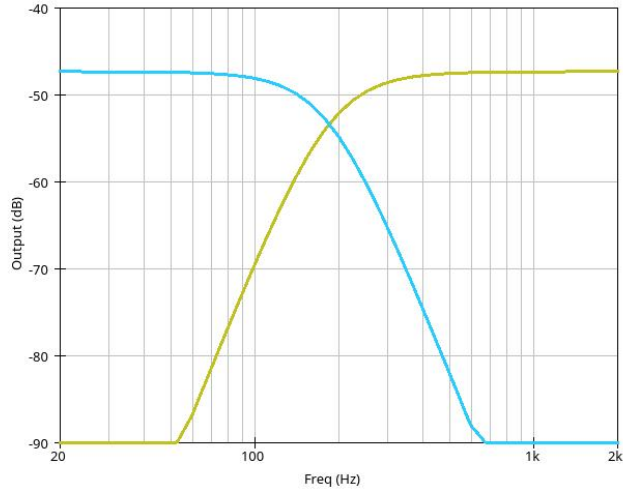


Figure 5: *Simulated transfer characteristic Linkwitz-Riley adjustment $f_0 = 185Hz$*

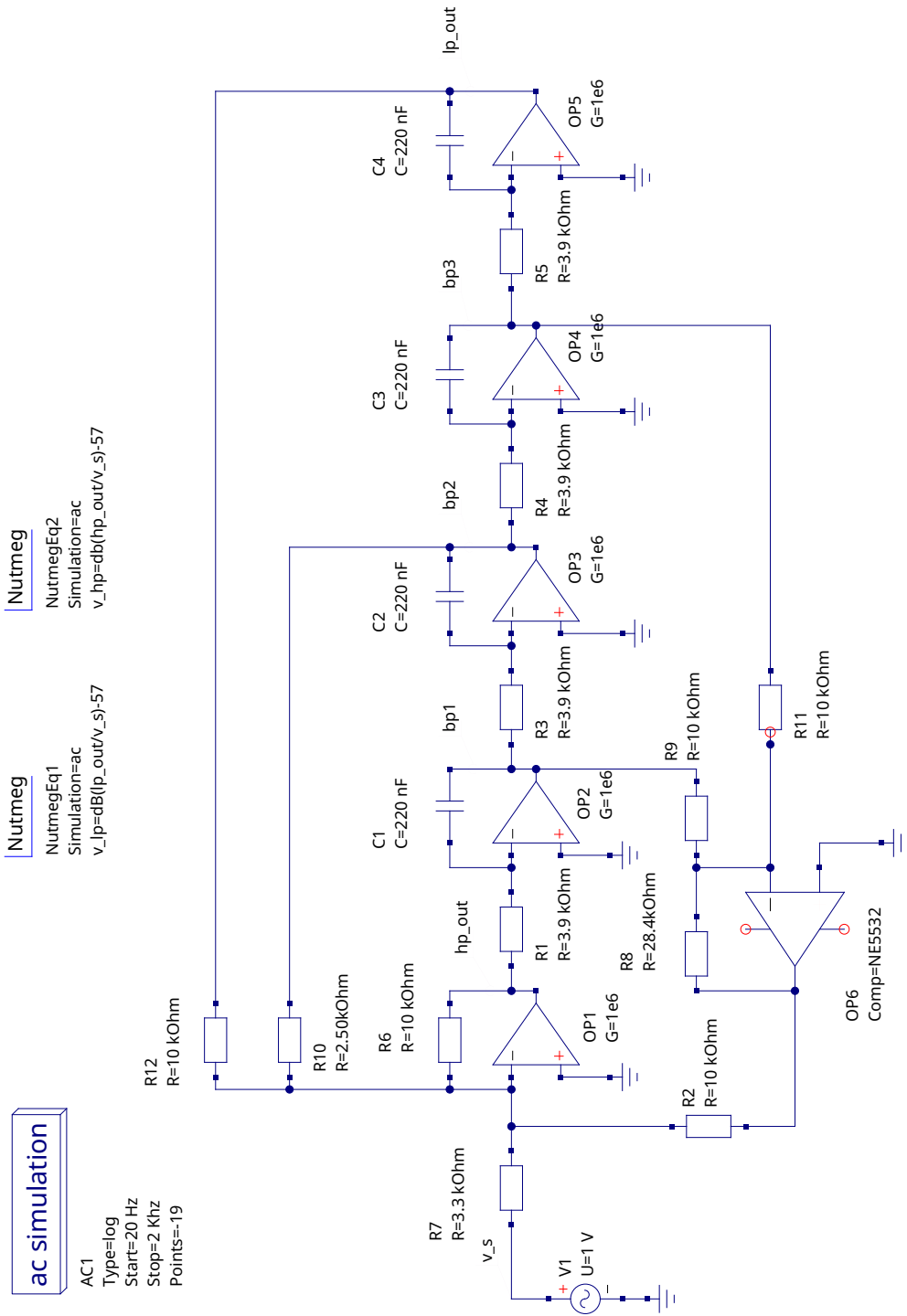


8 The actual circuit

The actual design of the filter part is unchanged with respect to the simulated version. Some trivial input and output buffers are added but these have no effect on the filter part.

The complete schematic is included on page 13. A differential input amplifier acts as the low impedance source to the input of the summing amplifier. The high-pass output is adjustable and buffered to provide a low-impedance output after the potentiometer. The low-pass output is intended as an input to another amplifier to sum Left and Right signals for a subwoofer. Therefore no additional gain adjusted output is added.

A nice touch is the addition of R_{18} to the contact of the adjustable resistor. It is very hard to obtain such an adjustable resistor in a logarithmic version. By adding R_{18} the output of the adjustable resistor is delinearized and somewhat resembles a logarithmic curve. Which is nice to have when controlling audio levels.

The circuit was built on breadboard as shipping costs for PCB services are prohibitively high for the area where I live. The breadboard layout is shown in figure 6. A picture of the assembled breadboard is in figure 7.

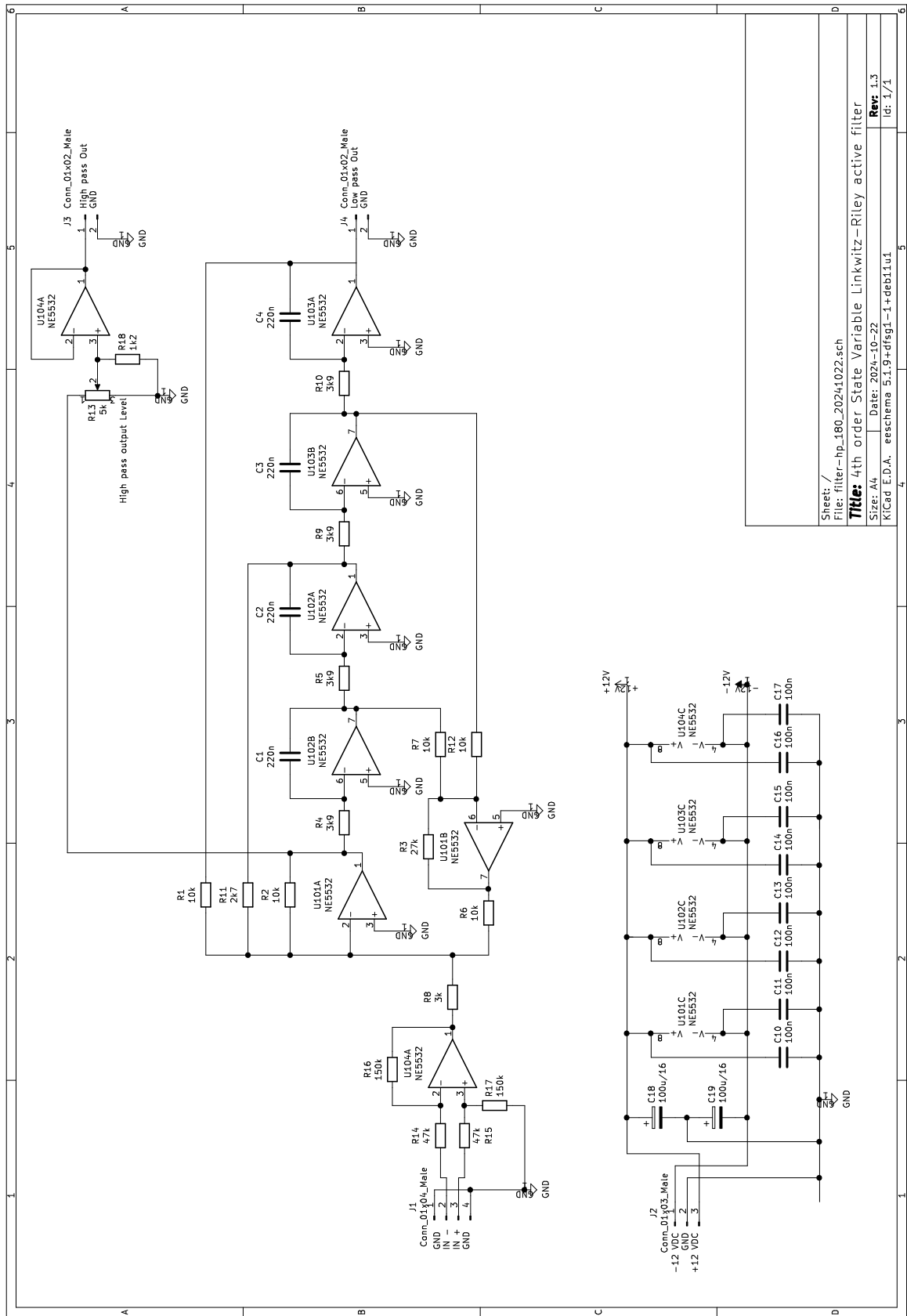

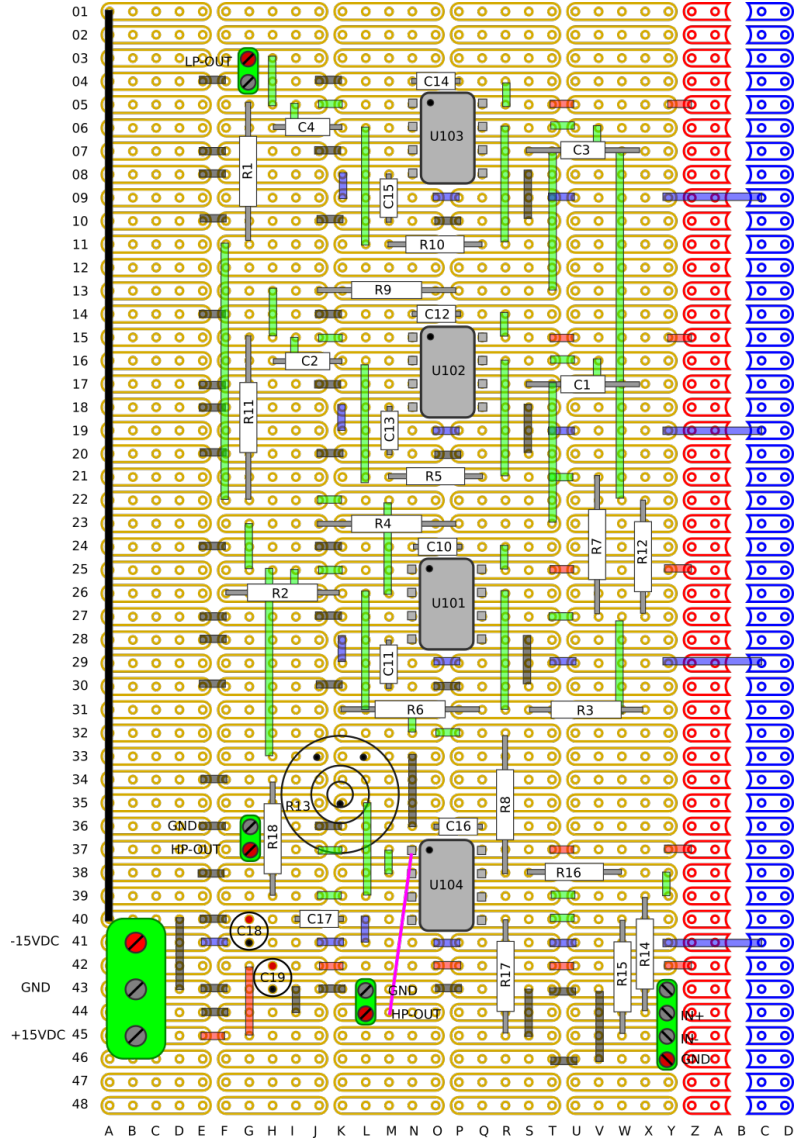


Figure 6: *Component layout as assembled on breadboard PCB*

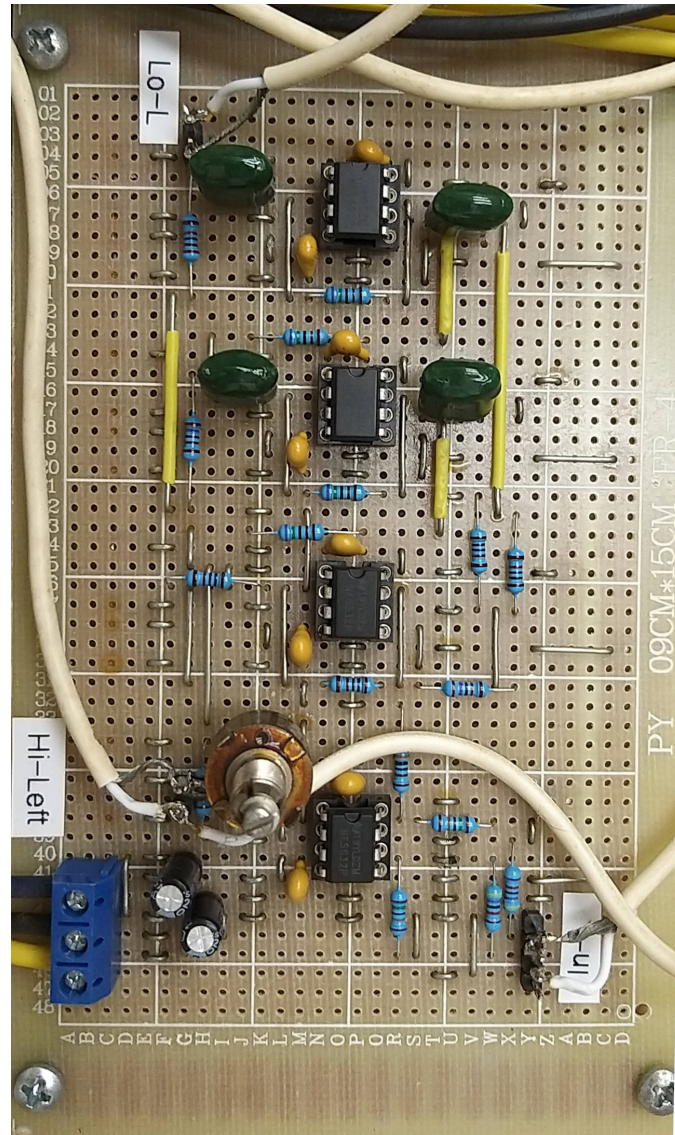


Figure 7: Assembled breadboard PCB

9 Measurement

A measurement was taken on simultaneously the High-pass and Low-pass outputs. The measured curve is shown in figure 8. The curves are nearly identical with the simulation result in figure 5. In the real world situation the damping at the crossover frequency is slightly less than -6dB. This is caused by choosing the resistors not exactly as calculated because of the availability of such values. In a later simulation it was obvious that this indeed causes a different damping at f_0 .

The reference level of -47dB is a result of the measurement circuit used. This value bears no relevance.

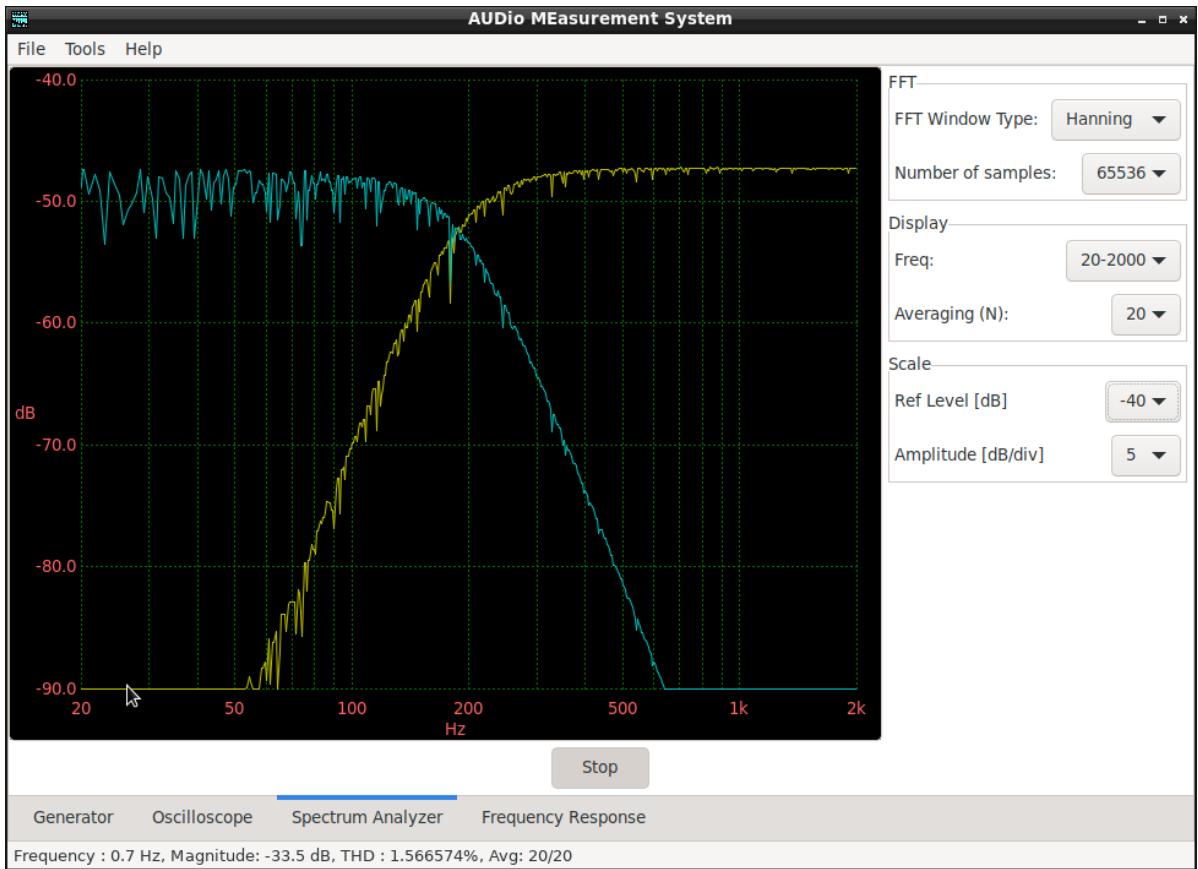


Figure 8: Measurement on actual implementation of 4th order Linkwitz-Riley filter. $F_c = 185\text{Hz}$

References

- [1] Janne Ahonen, *The analysis of fourth-order state variable filter and it's application to Linkwitz- Riley filters*, Linearteam tech paper, 2002
- [2] Mike Brinson (mbrin72043@yahoo.co.uk) and Vadim Kusnetsov (ra3xdh@gmail.com), *Qucs-S Help documentation : User Manual and Reference Material*, <https://qucs-s-help.readthedocs.io/en/latest/>, 2018
- [3] *Active Filter Cookbook*, Synergetic Press, New Mexico, 2nd edition, 1995