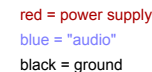


R3
- 33K was suggested online
for a different circuit (see
"JFET buffer and more" post
pdf... for an acoustic mag
pickup)

High



from standard
mag pickups

CircuitB - Mixer and Gain Circuit

(in "inverting mode", acting as virtual earth mixer)

- each can act as an "input capacitor"
[the following from LDT datasheet]
- 480pF source capacitance
[the following from D7series datasheet]
- Min. impedance- 10MΩ recommended 10MΩ
- Output voltage- mV to 100's of volts
- the capacitance is proportional to the area and inversely proportional to the thickness of the element
[the following from "Piezoelectricity" referring to DT1]
- Capacitance: 1.36 nF; Dissipation Factor of 0.018 @ 10 KHz; Impedance of 12 KΩ@ 10 KHz

- potentially try a 1pF capacitor back here to shunt RF to ground
- suggested "try 1pF-100pF 100 pF) to GND at the amplifier pin. The capacitor's impedance profile can create a notch filter at the system's most sensitive frequency"

UA22 soundcard

- [from spec sheet]
- Input impedance:
 - INPUT 1, 2 (XLR type): 4 k Ω balanced)
 - INPUT 1, 2 (1/4-in TRS phone type): 34 k Ω balanced)
 - INPUT 1 jack supports high impedance

Firewire1814 soundcard

- [from spec sheet]
- Line Inputs
 - nominal input level -10dBV
 - max input level +2.1dBV, typical
 - input impedance 10K Ohms, typical
- Mic/Inst. Inputs 1-2 (Balanced; at Minimum Gain)
 - max input level -3.8dBu, typical
 - input impedance