



FIGURE 11.8

A source-follower L-MOSFET design intended for professional audio applications. Maximum output power equals 250 watts RMS into a 4-ohm load at 0.02 percent THD.