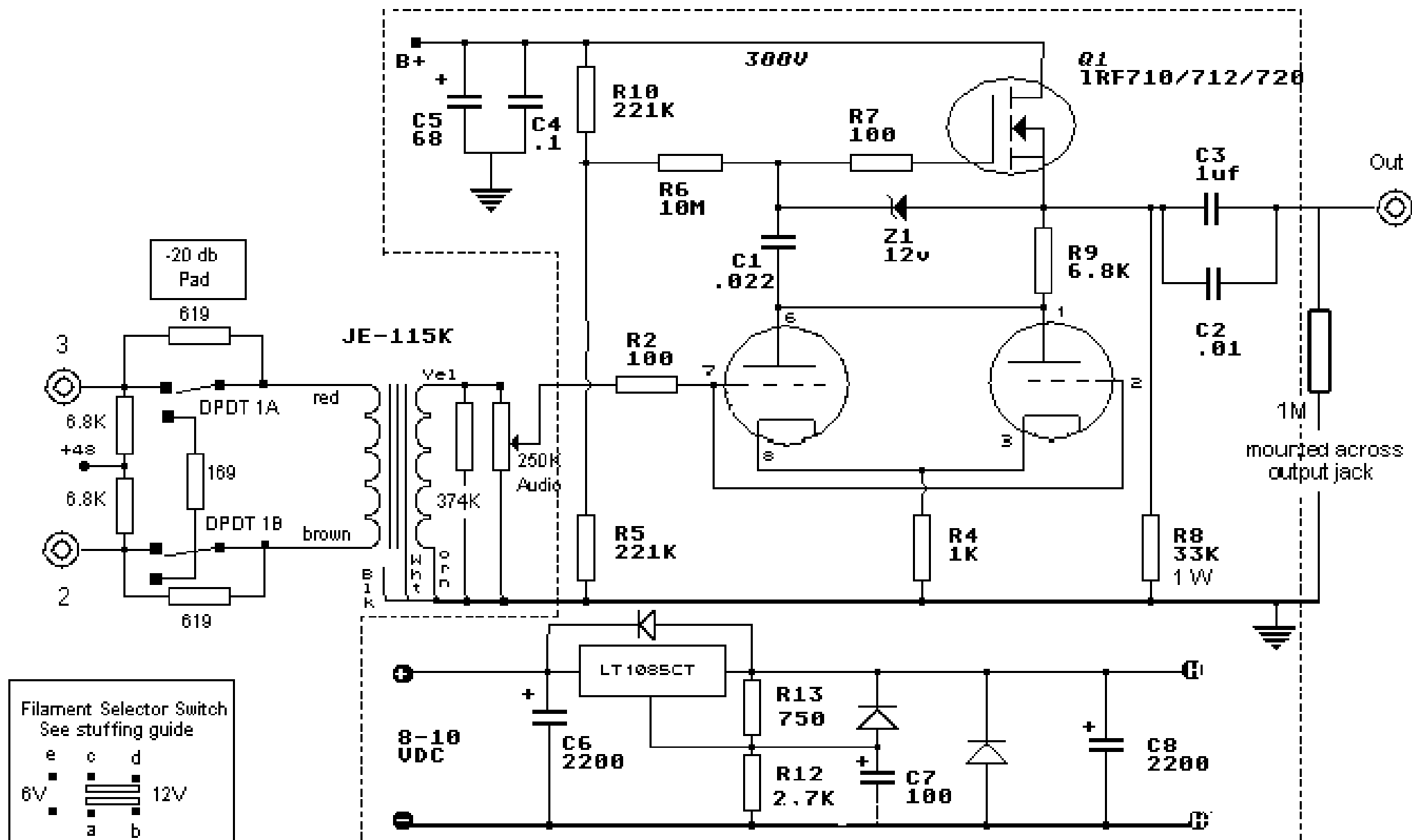


This is a schematic for a very nice sound microphone preamp based on a Jensen transformer and an [Alan Kimmel](#) designed "Mu-mode" gain stage taken from the Welborne Labs catalog. If you are going to build this mic-pre, I recommend buying the catalog for the "[Mu Stage Philosophy](#)" [article](#).



Voltage Gain = 20 (transformer) + mu of tube


Output Z = 180 (measured)

[Download the printed circuit board layout](#) (a zipped tif)

Here is the parts layout and stuffing guide. This is the Top view.



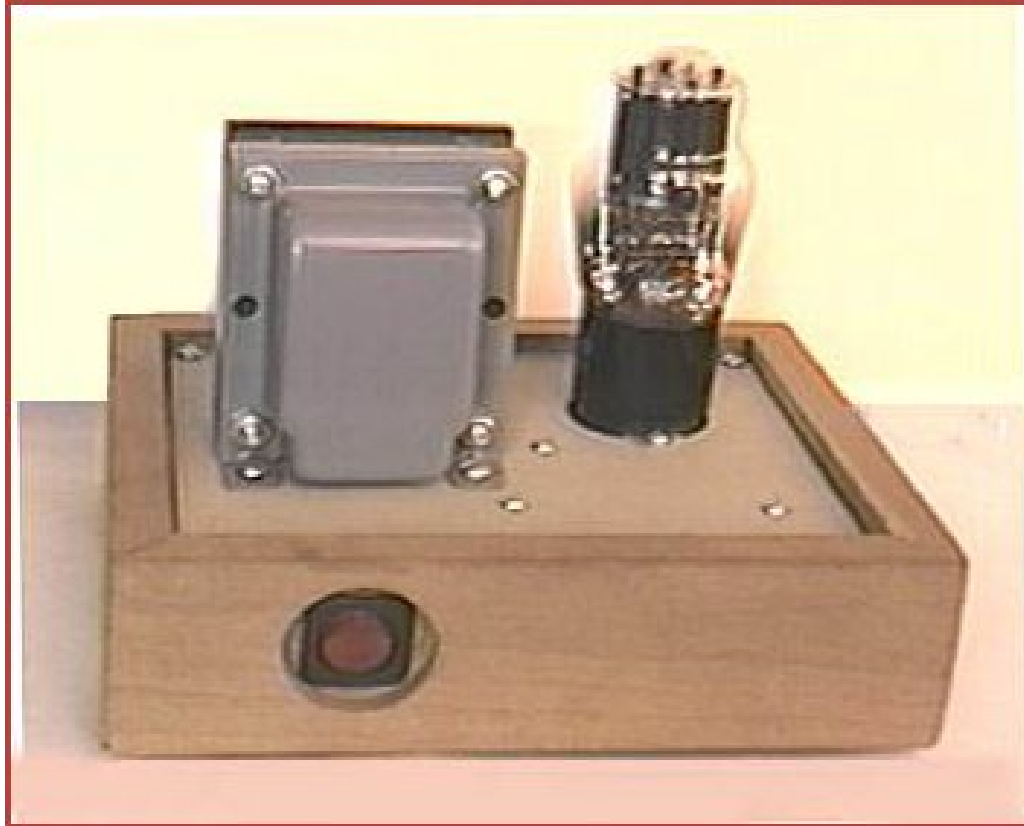Here is the separate power supply, a small transformer for phantom power is inside the case.



[Taos Amp](#)
[Home](#)
