

subsequent cascaded filters cut off at lower frequencies, and the circuit can switch these filters in or out depending on the desired output (Table 1). The  $\mu\text{C}$ 's speed, code efficiency, the number of discrete frequencies to be generated, and the spacing between those frequencies all determine the maximum frequency of operation. The number of loops for one-half cycle of output frequency (50% duty cycle) equals the number of cycles per loop  $\times$  time/cycle. With a 3.58-MHz crystal, the time per software cycle is 558 nsec. (The 705J1A  $\mu\text{C}$  uses one-half of the oscillation frequency for its internal operating frequency.) Table 1 shows some example frequencies and the corresponding number of loops.

The RC filters have a cutoff frequency, or  $-3\text{-dB}$  point, at the generated frequency for maximum linearity and minimum distortion. You should note that the out-

```

LISTING 1—FREQUENCY-GENERATING SUBROUTINE

fgen  sta temp1          ;store accumulator in a temp variable
      lda #04           ;number of interrupts for 250mS (5*65mS)
timer bset 2,tscr        ;clear real time interrupt flag
innr3 bset 4,output     ;turn on oscillator output
      ldx frec          ;number for one half cycle
innr1 decx              ;count down for half cycle
      bne innr1        ;if not finished, keep counting
      bclr 4,output    ;turn off oscillator output
      ldx frec          ;number for other half of cycle
innr2 decx              ;count down for half cycle
      bne innr2        ;if not finished, keep counting
      brclr 6,tscr,innr3 ;if 65mS not passed (see timer/counter
section of docs) do another cycle
total deca              ;subtract from the five 65mS for 250mS
repeat bne timer        ;have 250mS gone by? If not go back and
      lda temp1        ;restore accumulator
      rts
  
```

put is approximately the same level across all frequencies because the resistors are always in series when driving a high-impedance load. However, because of leakage when a capacitor is active, or grounded, the lowest frequency has a lower output than the highest frequency. You should optimize the R and C values in Figure 1 for your application, desired out-

put frequencies, and impedance. You can switch the filters on and off sequentially, independently, or in combinations to suit different needs. (DI #2278)

To Vote For This Design,  
Circle No. 36


## 74ACT74 makes low-skew clock divider

Tom Napier, Consultant, North Wales, PA

Serial-data systems often generate an internal clock at twice the data rate for mid-bit sampling or for generating bi-phase codes. External equipment and some internal processes require a clock that runs at the data rate. Simply dividing the twice-rate clock with a flip-flop generates a data-rate clock that is skewed by one logic delay with respect to the input. This delay can be a significant fraction of the bit period. You can use specialized PLL-based low-skew divider chips to deal with this problem, but these chips have a limited frequency range and are not designed to follow rapid changes in the data rate.

The circuit in Figure 1 uses a dual flip-flop, the 74ACT74, to generate both clock rates as well as both clock polarities with negligible skew. One half of the chip,  $\text{IC}_{1\text{A}}$ , acts as a normal divide-by-two circuit. The other half,  $\text{IC}_{1\text{B}}$ , tracks the input clock because the input's leading edge triggers  $\text{IC}_{1\text{B}}$  high and the input's trailing edge resets  $\text{IC}_{1\text{B}}$ . The divider transitions are synchronous within a few hundred picoseconds with the positive transitions of the twice-

Figure 1

 

The 74ACT74 dual flip-flop generates two clock rates with negligible skew.

rate clock that the chip's other half generates. This circuit works with inputs from a few hertz to more than 100 MHz.

Without  $R_1$ , the input removes the reset from the twice-rate flip-flop at the same moment as the input clocks this flip-flop on. Theoretically, this setup is allowable because the 74ACT74's reset-recovery time is

specified as 0 nsec. In practice, a resistor in the 100 to 500 $\Omega$  region, in conjunction with the chip's input capacitance, delays the clock inputs slightly and adds a useful safety margin. (DI #2282)

To Vote For This Design,  
Circle No. 37