

$$R_2 = \frac{Q}{(2Q^2 - A_0) \omega_0 C_1} \quad (2.16.3)$$

For checking and trimming, use the following:

$$A_0 = \frac{R_3}{2R_1} \quad (2.16.4)$$

$$f_0 = \frac{1}{2\pi C_1} \sqrt{\frac{R_1 + R_2}{R_1 R_2 R_3}} \quad (2.16.5)$$

$$Q = \frac{1}{2} \omega_0 R_3 C_1 \quad (2.16.6)$$

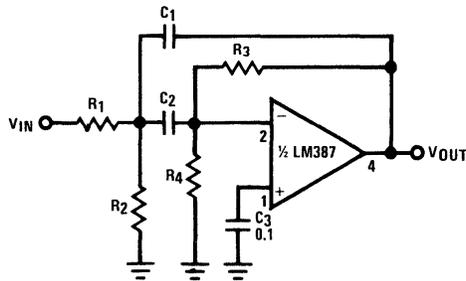


FIGURE 2.16.1 LM387 Bandpass Active Filter

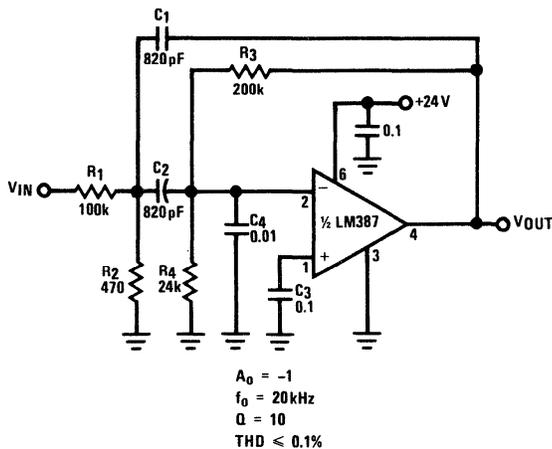


FIGURE 2.16.2 20kHz Bandpass Active Filter

### Example 2.16.1

Design a two-pole active bandpass filter with a center frequency  $f_0 = 20\text{kHz}$ , midband gain  $A_0 = 1$ , and a bandwidth of  $2000\text{Hz}$ . A single supply,  $V_s = 24\text{V}$ , is to be used.

#### Solution

$$1. Q \triangleq \frac{f_0}{\text{BW}} = \frac{20\text{kHz}}{2000\text{Hz}} = 10, \quad \omega_0 = 2\pi f_0$$

$$2. \text{ Let } R_4 = 24\text{ k}\Omega.$$

$$3. R_3 = \left(\frac{V_s}{2.6} - 1\right) R_4 = \left(\frac{24}{2.6} - 1\right) 24\text{k} = 1.98 \times 10^5$$

Use  $R_3 = 200\text{k}$

4. From Equation (2.16.1):

$$R_1 = \frac{R_3}{2A_0} = \frac{200\text{k}}{2} = 100\text{k}$$

$$R_1 = 100\text{k}$$

5. Let  $C_1 = C_2$ ; then, from Equation (2.16.2):

$$C_1 = \frac{Q}{A_0 \omega_0 R_1} = \frac{10}{(1)(2\pi)(20\text{k})(1 \times 10^5)} = 796\text{pF}$$

Use  $C_1 = 820\text{pF}$

6. From Equation (2.16.3):

$$R_2 = \frac{Q}{(2Q^2 - A_0) \omega_0 C_1} = \frac{10}{[(2)(10)^2 - 1] (2\pi)(20\text{k})(820\text{pF})} = 488\Omega$$

Use  $R_2 = 470\Omega$

The final design appears as Figure 2.16.2. Capacitor  $C_3$  is used to AC ground the positive input and can be made equal to  $0.1\mu\text{F}$  for all designs. Input shunting capacitor  $C_4$  is included for stability since the design gain is less than 10.

## 2.17 OCTAVE EQUALIZER

An octave equalizer offers the user several bands of tone control, separated an octave apart in frequency with independent adjustment of each. It is designed to compensate for any unwanted amplitude-frequency or phase-frequency characteristics of an audio system.

The midrange tone control circuit described in Section 2.14 can be used separately to make a convenient ten band octave equalizer. Design equations result from a detailed analysis of Figure 2.17.1, where a typical section is shown. Resistors  $R_3$  have been added to supply negative input DC bias currents, and to guarantee unity gain at low frequencies. This circuit is particularly suited for equalizer applications since it offers a unique combination of results depending upon the slider position of  $R_2$ . With  $R_2$  in the flat position (i.e., centered) the circuit becomes an all-pass with unity gain; moving  $R_2$  to full boost results in a bandpass characteristic, while positioning  $R_2$  in full cut creates a band-reject (notch) filter.

Writing the transfer function for Figure 2.17.1 in its general form for max boost (assuming only  $R_3 \gg R_1$ ) results in Equation (2.17.1).

$$\frac{e_o}{e_i} = \frac{s^2 + \left[ \frac{2R_1 R_2 C_1 + R_3 (R_1 + R_2) C_2}{R_1 R_2 R_3 C_1 C_2} \right] s + \frac{2R_1 + R_2}{R_1 R_2 R_3 C_1 C_2}}{s^2 + \left[ \frac{(R_1 + R_2) C_2 + 2R_2 C_1 + R_3 C_2}{R_2 R_3 C_1 C_2} \right] s + \frac{2R_1 + R_2}{R_1 R_2 R_3 C_1 C_2}} \quad (2.17.1)$$

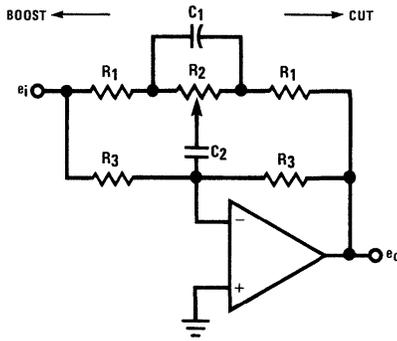


FIGURE 2.17.1 Typical Octave Equalizer Section

Equation (2.17.1) has the form of Equation (2.17.2):

$$\frac{e_o}{e_i} = -\frac{S^2 + K2\rho\omega_0S + \omega_0^2}{S^2 + 2\rho\omega_0S + \omega_0^2} \quad (2.17.2)$$

where:  $Q = \frac{1}{2\rho}$ ,  $A_o = \text{gain @ } f_o = K$ ,  $\omega_o = 2\pi f_o$

Equating coefficients yields Equations (2.17.3)-(2.17.5):

$$\omega_o = \sqrt{\frac{2R_1 + R_2}{R_1 R_2 R_3 C_1 C_2}} \quad (2.17.3)$$

$$A_o = -\frac{2R_1 R_2 C_1 + R_3(R_1 + R_2)C_2}{2R_1 R_2 C_1 + R_1(R_2 + R_3)C_2} \quad (2.17.4)$$

$$Q = \sqrt{\frac{2R_1 + R_2}{R_1 R_2 R_3 C_1 C_2} \left( \frac{R_2 R_3 C_1 C_2}{(R_1 + R_2)C_2 + 2R_2 C_1 + R_3 C_2} \right)} \quad (2.17.5)$$

In order to reduce these equations down to something useful, it is necessary to examine what is required of the finished equalizer in terms of performance. For normal home use,  $\pm 12\text{dB}$  of boost and cut is adequate, which means only a moderate amount of passband gain is necessary; and since the filters will be centered one octave apart in frequency a large  $Q$  is not necessary ( $Q = 1-2$  works fine). What *is* desirable is for the passband ripple (when all filters are at maximum) to be less than 3dB.

Examination of Equation (2.17.5) in terms of optimizing the ratio of  $C_1$  and  $C_2$  in order to maximize  $Q$  shows a good choice is to let  $C_1 = 10C_2$ . A further design rule that is reasonable is to make  $R_3 = 10R_2$ , since  $R_3$  is unnecessary for the filter section. Applying these rules to Equations (2.17.3)-(2.17.5) produces some useful results:

$$\omega_o = 2\pi f_o = \frac{1}{10R_2 C_2} \sqrt{2 + \frac{R_2}{R_1}} \quad (2.17.6)$$

$$A_o = 1 + \frac{R_2}{3R_1} \quad (2.17.7)$$

$$Q = \sqrt{\frac{2R_1 + R_2}{9.61R_1}} \quad (2.17.8)$$

Rewriting (2.17.7) and (2.17.8) yields:

$$R_2 = 3(A_o - 1)R_1 \quad (2.17.9)$$

$$R_2 = (9.61Q^2 - 2)R_1 \quad (2.17.10)$$

Combining (2.17.9) and (2.17.10) gives:

$$A_o = \left( \frac{9.61Q^2 - 2}{3} \right) + 1 \quad (2.17.11)$$

From Equation (2.17.11) it is seen that gain and  $Q$  are intimately related and that large gains mean large  $Q$ s and vice versa. Equations (2.17.9) and (2.17.10) show that  $R_1$  and  $R_2$  are not independent, which means one may be arbitrarily selected and from it (knowing  $A_o$  and/or  $Q$ ) the other is found.

#### Design

1. Select  $R_2 = 100\text{k}$ .
2.  $R_3 = 10R_2 = 10(100\text{k})$   
 $R_3 = 1 \text{ Meg}$
3. Let  $A_o = 12\text{dB} = 4\text{V/V}$  and from Equation (2.17.9):

$$R_1 = \frac{R_2}{3(A_o - 1)} = \frac{100\text{k}}{3(4 - 1)} = 1.11 \times 10^4$$

Use  $R_1 = 10\text{k}$ .

4. Check  $Q$  from Equation (2.17.8):

$$Q = \sqrt{\frac{2(10\text{k}) + 100\text{k}}{(9.61)(10\text{k})}}$$

$Q = 1.12$ , which is satisfactory.

5. Calculate  $C_2$  from Equation (2.17.6) and  $C_1 = 10C_2$ :

$$C_2 = \frac{1}{2\pi f_o (10R_2)} \sqrt{2 + \frac{R_2}{R_1}}$$

$$C_2 = \frac{1}{2\pi f_o (10)(100\text{k})} \sqrt{2 + \frac{100\text{k}}{10\text{k}}}$$

$$C_2 = \frac{5.513 \times 10^{-7}}{f_o}$$

A table of standard values for  $C_1$  and  $C_2$  vs.  $f_o$  is given below:


TABLE 2.17.1

$f_o$ (Hz)	$C_1$	$C_2$
32	0.18 $\mu\text{F}$	0.018 $\mu\text{F}$
64	0.1 $\mu\text{F}$	0.01 $\mu\text{F}$
125	0.047 $\mu\text{F}$	0.0047 $\mu\text{F}$
250	0.022 $\mu\text{F}$	0.0022 $\mu\text{F}$
500	0.012 $\mu\text{F}$	0.0012 $\mu\text{F}$
1k	0.0056 $\mu\text{F}$	560 pF
2k	0.0027 $\mu\text{F}$	270 pF
4k	0.0015 $\mu\text{F}$	150 pF
8k	680 pF	68 pF
16k	360 pF	36 pF

The complete design appears as Figure 2.17.2. While it appears complicated, it is really just repetitious. By using quad amplifier ICs, the whole thing consists of only three integrated circuits. Figure 2.17.2 is for one channel and would be duplicated for a stereo system. The input buffer amplifier guarantees a low source impedance to drive the equalizer and presents a large input impedance for the preamplifier. Resistor  $R_g$  is necessary to stabilize the LM349 while retaining its fast slew rate ( $2V/\mu s$ ). The output amplifier is a unity gain, inverting summer used to add each equalized octave of frequencies back together again. One aspect of the summing circuit that may appear odd is that the original signal is subtracted from the sum via  $R_{20}$ . (It is subtracted rather than added because each equalizer section inverts the signal relative to the output of the buffer and  $R_{20}$  delivers the original signal without inverting.) The reason this subtraction is necessary

is in order to maintain a unity gain system. Without it the output would equal ten times the input, e.g., an input of 1V, with all pots flat, would produce 1V at each equalizer output – the sum of which is 10V. By scaling  $R_{20}$  such that the input signal is multiplied by 9 before the subtraction, the output now becomes  $10V - 9V = 1V$  output, i.e., unity gain. The addition of  $R_4$  to each section is for stability. Capacitor  $C_3$  minimizes possibly large DC offset voltages from appearing at the output. If the driving source has a DC level then an input capacitor is necessary ( $0.1\mu F$ ), and similarly, if the load has a DC level, then an output capacitor is required.

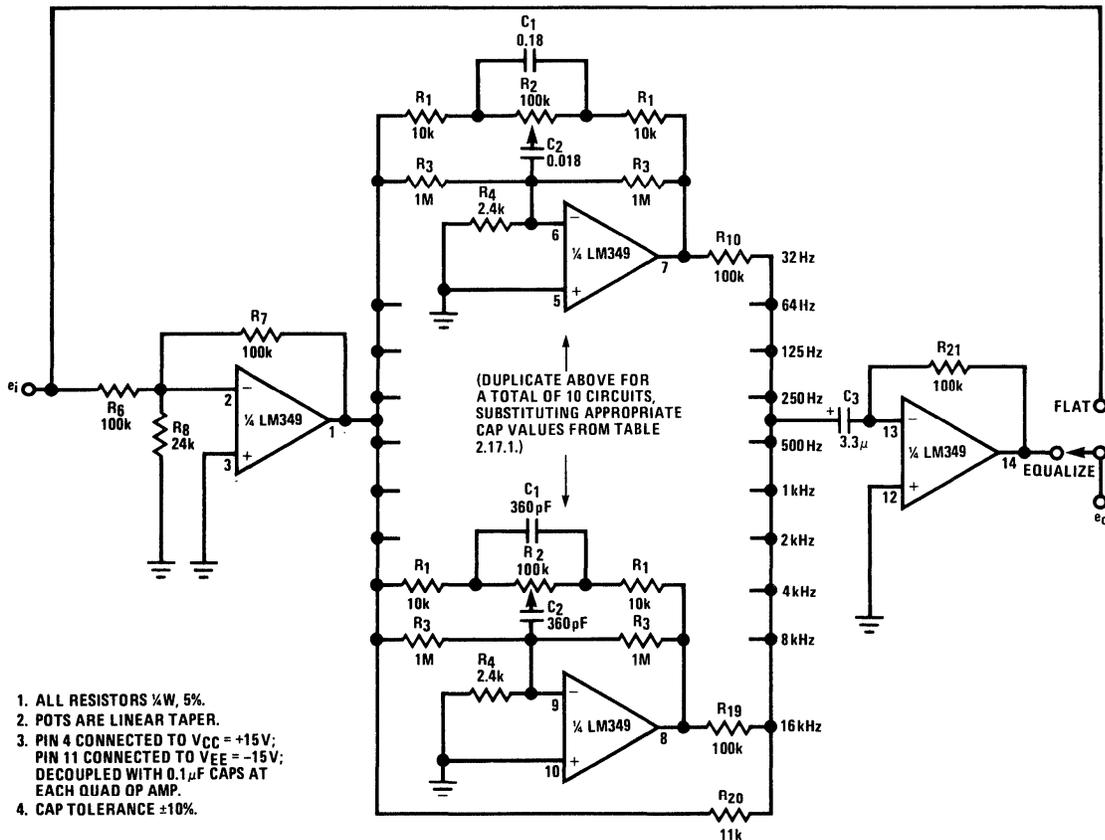It is possible to generate just about any frequency response imaginable with this ten band octave equalizer. A few possibilities are given in Figure 2.17.3.



1. ALL RESISTORS  $\frac{1}{4}W$ , 5%.
2. POTS ARE LINEAR TAPER.
3. PIN 4 CONNECTED TO  $V_{CC} = +15V$ ; PIN 11 CONNECTED TO  $V_{EE} = -15V$ ; DECOUPLED WITH  $0.1\mu F$  CAPS AT EACH QUAD OP AMP.
4. CAP TOLERANCE  $\pm 10\%$ .

FIGURE 2.17.2 Ten Band Octave Equalizer

- ① ALL CONTROLS FLAT
- ② 500 Hz BOOST/CUT, ALL OTHERS FLAT
- ③ 1 kHz BOOST/CUT, ALL OTHERS FLAT
- ④ 500 Hz, 1 kHz, 2 kHz, 4 kHz BOOSTED, ALL OTHERS FLAT

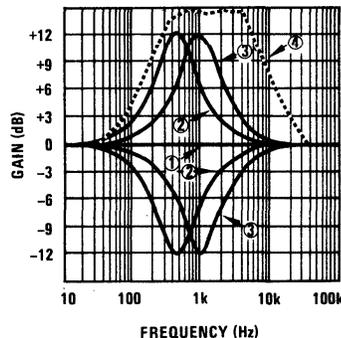


FIGURE 2.17.3 Typical Frequency Response of Equalizer