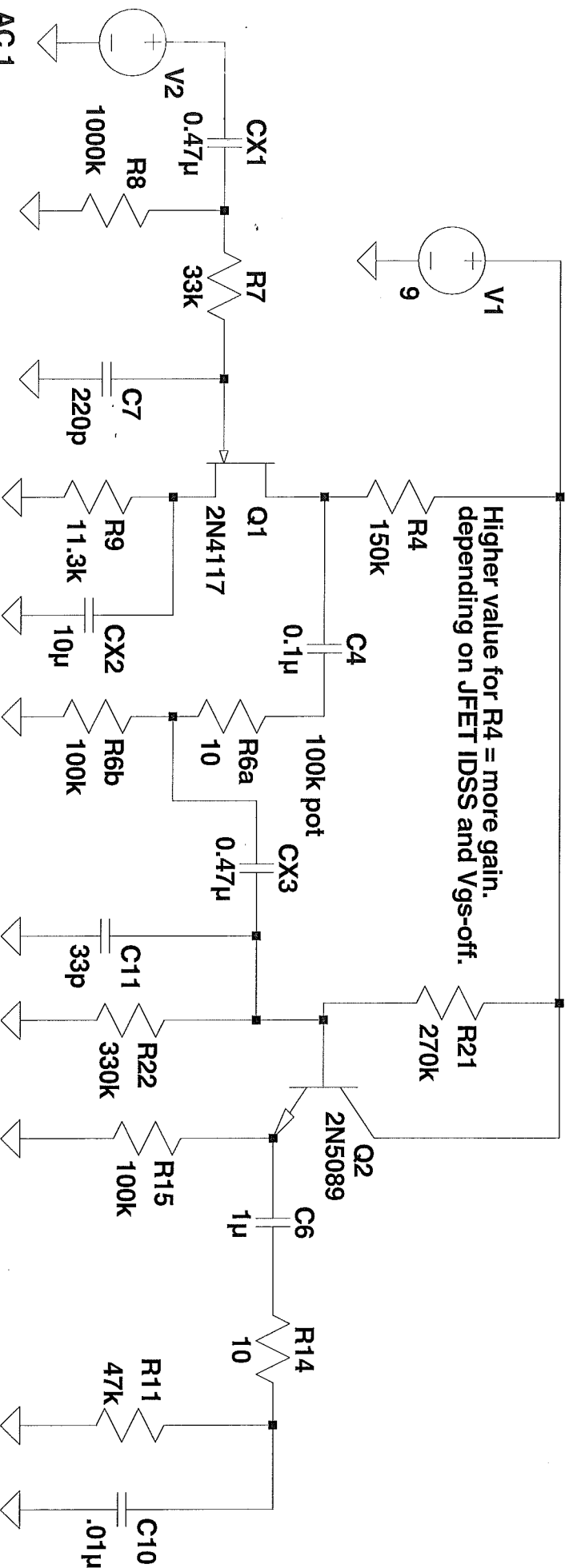


oNo_spaz Guitar Preamp

(a few suggestions)



Must have CX1 to maintain proper bias on Q1.

If desired, CX2 will give you more gain.

Must have CX3 to maintain proper DC bias on Q2.

AC 1
.tran .4
Rser=1

;ac dec 300 1 1000k