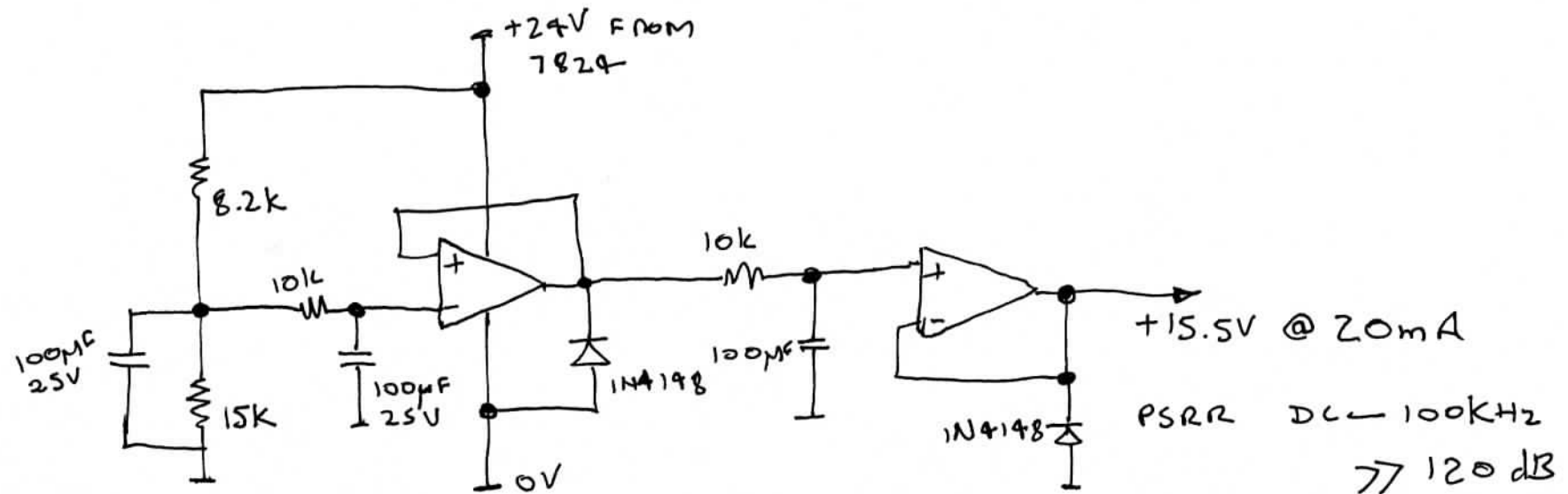


LOW VOLTAGE HIGH PSRR SUPPLY



OPAMP IS LM4562

YOU CAN USE SINGLE STAGE AS WELL - PERFORMANCE IS STILL +++ OVER NOT USING THIS APPROACH.

JUST MIRROR FOR -VE RAIL IF NEEDED

BONSAI