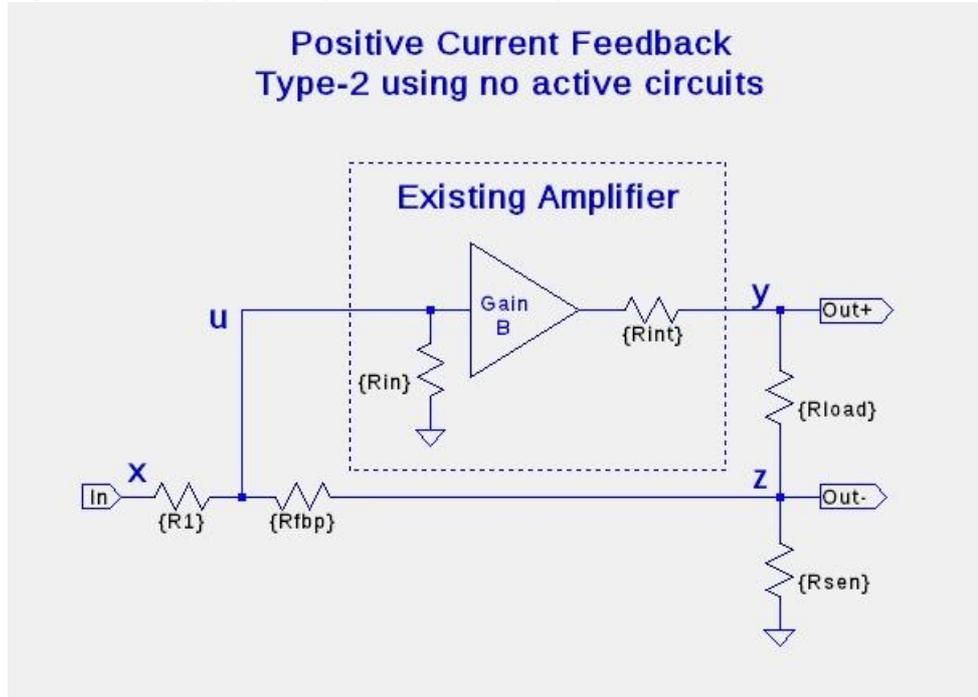


Positive Current Feedback (PCF) around existing Amplifier using no active circuits.

Figure 1: /m/m-rugby/rom1/quam/audio/circuits/spice/F7/DIYAudio-forum/PCF-T2-noFE-1.asc.jpg



Here is a Positive Current Feedback (PCF) circuit that can be used with an existing power amplifier to obtain closed loop gain (CLG) and output resistance (Rout) around the existing with no additional active circuitry.

Circuit Equations:

$$0 = (x-u)/R1 + (z-u)/Rfbp + (0-v)/Rin$$

$$Iload = (B*u-y)/Rint$$

$$Iload = (y-z)/Rload$$

$$Iload = z/Rsen$$

$$Zin=x/((x-u)/R1)$$

(Note: These circuit equations ignore the (minor) effects of currents through the feedback resistors on nodes y and z).

Parameters of the Existing Amplifier:

Rin: input resistance to ground

B: closed loop gain

Rint: internal output resistance

Arbitrary parameters of the Circuit:

Rsen

Parameters to obtain:

CLG: closed loop gain of the resulting amplifier

Rout: output resistance of the resulting amplifier

Circuit Unknowns to be determined:

R1, Rfbp and Zin

Solving the circuit equations for R1 and Rfbp gives the following:

$$R1 = \frac{Rin(-Rint + Rout + Rsen(-CLG + B - 1))}{Rsen CLG}$$

$$(\%0128) \quad R_{fbp} = \frac{R_{in} (-R_{int} + R_{out} + R_{sen} (-CLG + B - 1))}{R_{sen} - R_{out} + R_{int}}$$

$$(\%0129) \quad Z_{in} = \frac{R_{in} B (-R_{int} + R_{out} + R_{sen} (-CLG + B - 1))}{R_{sen} (B - CLG) CLG}$$

After some rearranging we get:

$$(\%0111) \quad \frac{R_1}{R_{in}} = \frac{-1 + \frac{R_{out} - R_{int}}{R_{sen}} + B}{CLG} - 1$$

$$(\%0112) \quad \frac{R_{fbp}}{R_{in}} = \frac{B - CLG}{\frac{R_{int} - R_{out}}{R_{sen}} + 1} - 1$$

In order that R1 and Rfbp are non-negative, must have

$$CLG \leq B - 1 - (R_{int} - R_{out}) / R_{sen}$$

Example:

FirstWatt F6

Rin = 100K

B = 5.0

Rint = 0.5 Ohms

Choose

CLG = 3.0

Rsen = 0.5 Ohms

Rout = 0.08 Ohms for DF=100

Get:

R1 = 5333

Rfbp = 8696

Zin = 13333

Figure 2: /m/m-rugby/rom1/quam/audio/circuits/spice/F7/DIYAudio-forum/PCF-T2-noFE-F6.asc.jpg

