
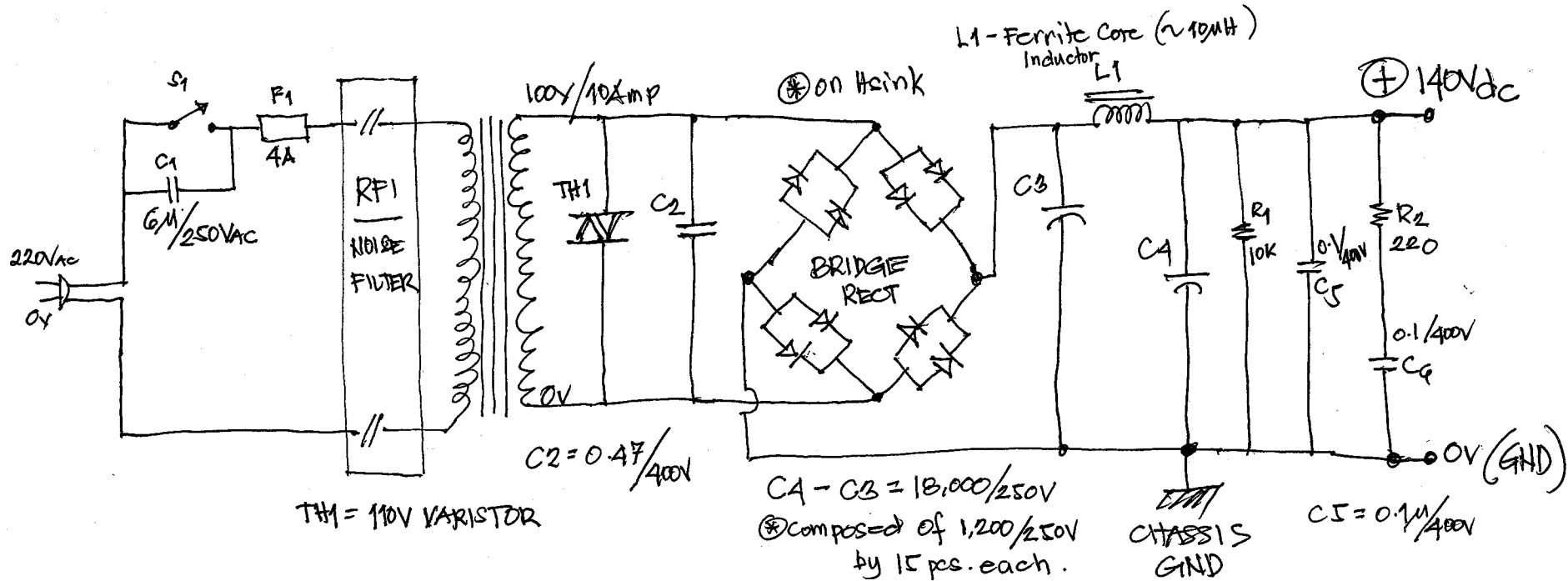


⑧ PROPOSED PSU FOR THE AMP.

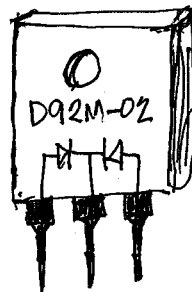


OPTION 1: USING D92M-02 (x4) Hi-speed Rect.

as BRIDGE :



HIGH SPEED DIODE  
STACK RECTIFIER.  
200V / 20A

OPTION 2: USING D20XB60 BRIDGE RECT.

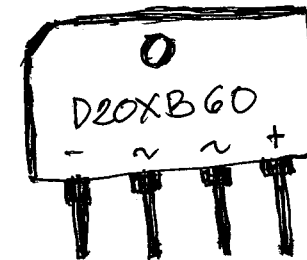

600V/20A