
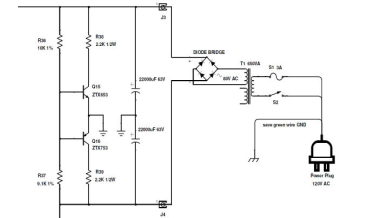


## QUAD 909

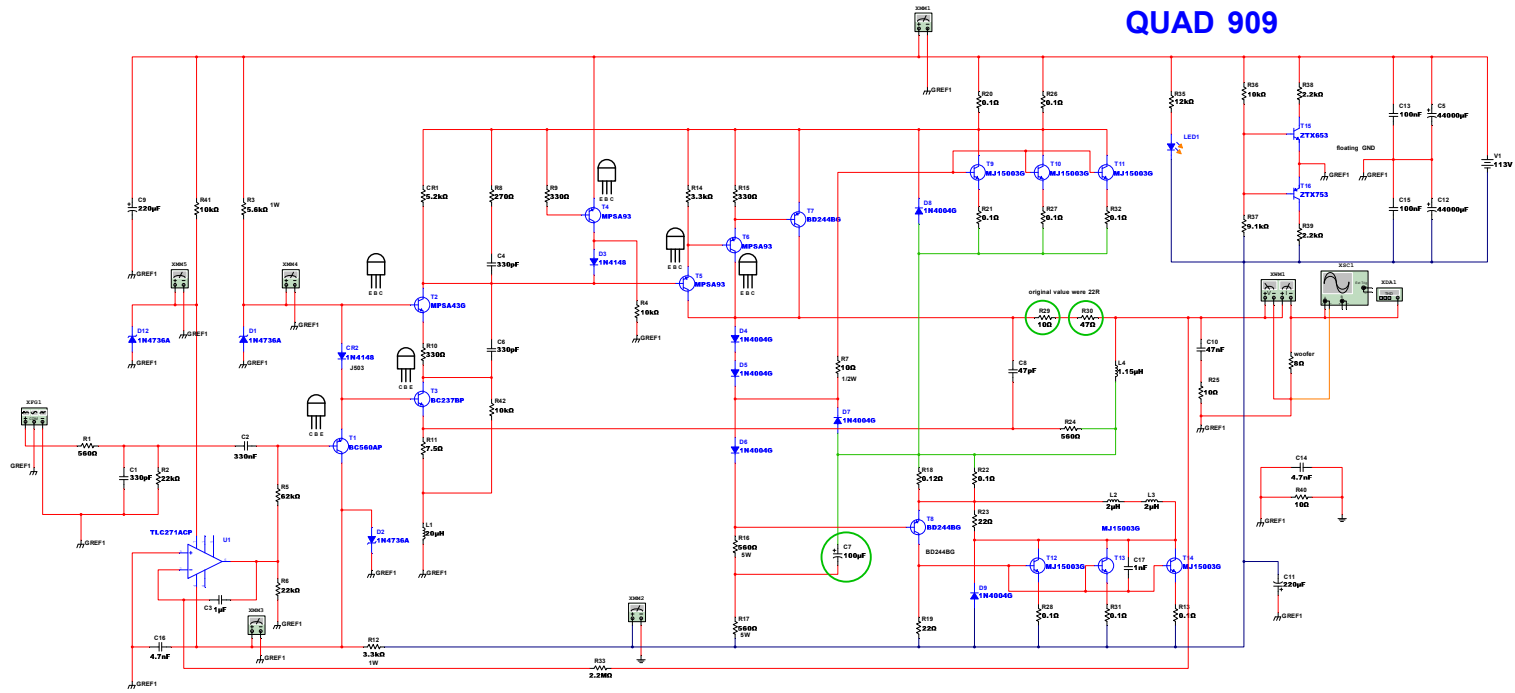

The circuit composed by T15 and T16 are really important the circuit creates a virtual or floating GND, the supply voltage of the secondaries are 82.5V AC a 500W toroidal will fit the amplifier well.

the components that have a circle are been change the values to lower it THD