

Reactive Loudspeaker Loads

Copyright: Michael Kiwanuka

The impedance $|Z\angle\theta^\circ|$ of any loudspeaker system may be assumed to consist of its *resistance* R (i.e. measured at DC) in series with an equivalent reactance X such that:

$$Z\angle\theta^\circ = (R \pm jX) \quad (1)$$

And

$$|Z\angle\theta^\circ| = \sqrt{(R^2 + X^2)} \quad (2)$$

The loudspeaker's resistance R (**fig. 1**) is *always* less than the magnitude of its impedance since $|Z\angle\theta^\circ|_{(R>X)} > R$ and $|Z\angle\theta^\circ|_{(X>R)} > X$.

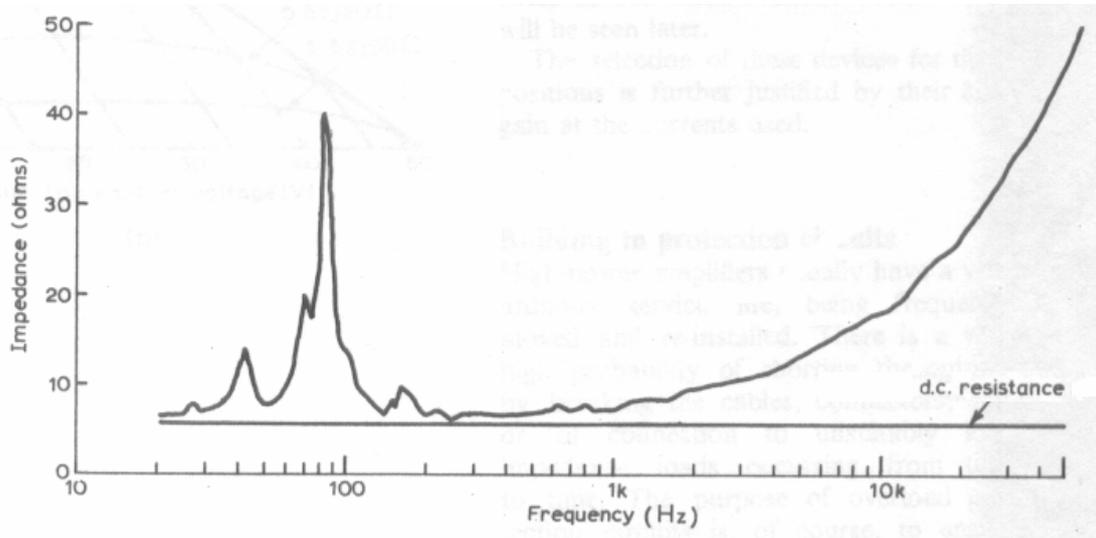


Fig. 1. Impedance frequency response of a nominal 8Ω loudspeaker. The horizontal line represents its resistance of roughly 5Ω5. (After R. B. H. Becker, *Wireless World* February 1972, pg. 7).

For instance at 1KHz a $9.7\Omega\angle -55.5^\circ$ impedance consists of a $5\Omega5$ resistor in series with a $19\mu9$ capacitor; in this case the resistance alone is nearly half the magnitude of the total impedance at 1KHz.

If a loudspeaker system's input *resistance* (in contradistinction to its *nominal input impedance*) is known, then all possible combinations of its impedance are wholly described by $Z\angle\theta^\circ = (R \pm j\infty)$.

It is shown (**fig. 2**) that all possible characteristics described by $Z\angle\theta^\circ = (R \pm j\infty)$ are bounded by a line (in red) of negative slope extending from the maximum current (V_{Supply}/R) demanded by the load to twice the magnitude $(2|V_{\text{Supply}}|)$ of each supply rail.