

Points frequency voltage voltage

12-28-15 4 resistor bridge made of 1% 1K Corning metal film.
The 1% resistors were randomly selected. The frequency generator was set then each lower resistor was measured alternating L to R, and repeated for each frequency setting.
DT

	Hz's	bottom L resistor	bottom R resistor
1	50	1.46228	1.46118
2	100	1.46199	1.461
3	500	1.46161	1.4605
4	1000	1.46144	1.46043
5	5000	1.46142	1.46034
6	10000	1.46159	1.46051
7	15000	1.4617	1.46066
8	20000	1.46194	1.46088
9	25000	1.46204	1.46091
10	30000	1.4622	1.46111
11	40000	1.46464	1.46351
12	50000	1.46485	1.46384
13	100000	1.46782	1.4667
14	150000	1.47038	1.46928
15	200000	1.4746	1.47352
16	300000	1.47709	1.47603

