



Fig. 1. Complete circuit diagram of the preamplifier. C_1 and C_7 are adjusted for given cartridge. Inductance of coil L is $32 \mu\text{H}$.