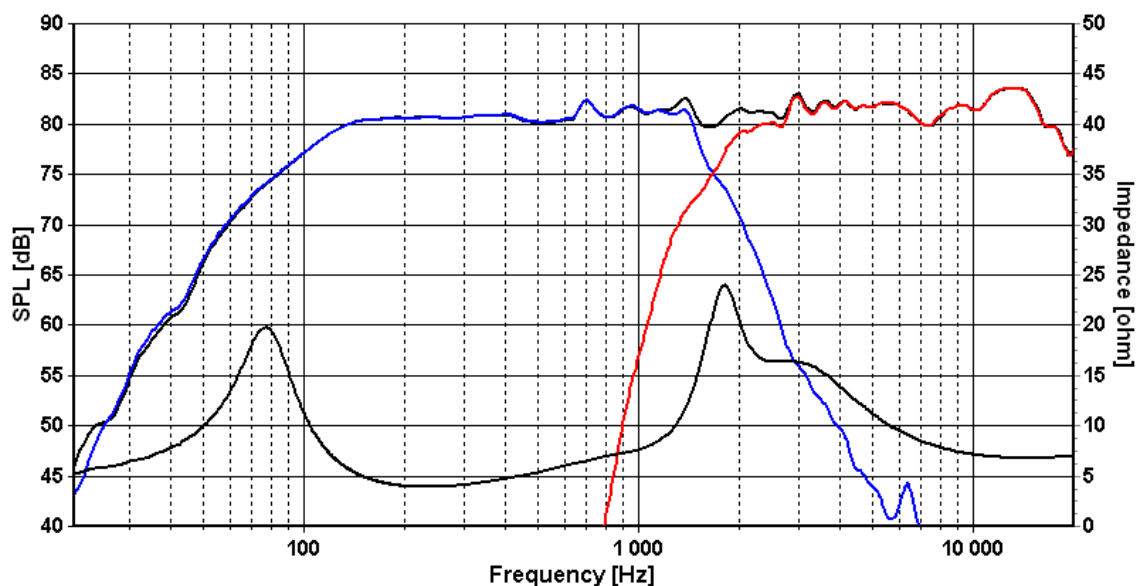


The crossover design in this application note results in a system with a very flat frequency response. The measurement is done at 20 degrees off-axis.



The 2nd order lowpass filter and 3rd order highpass filter result in a perfect in-phase summing of the drivers' output at the crossover frequency.

Crossover for H1602-04/06 L12RE/XFC

