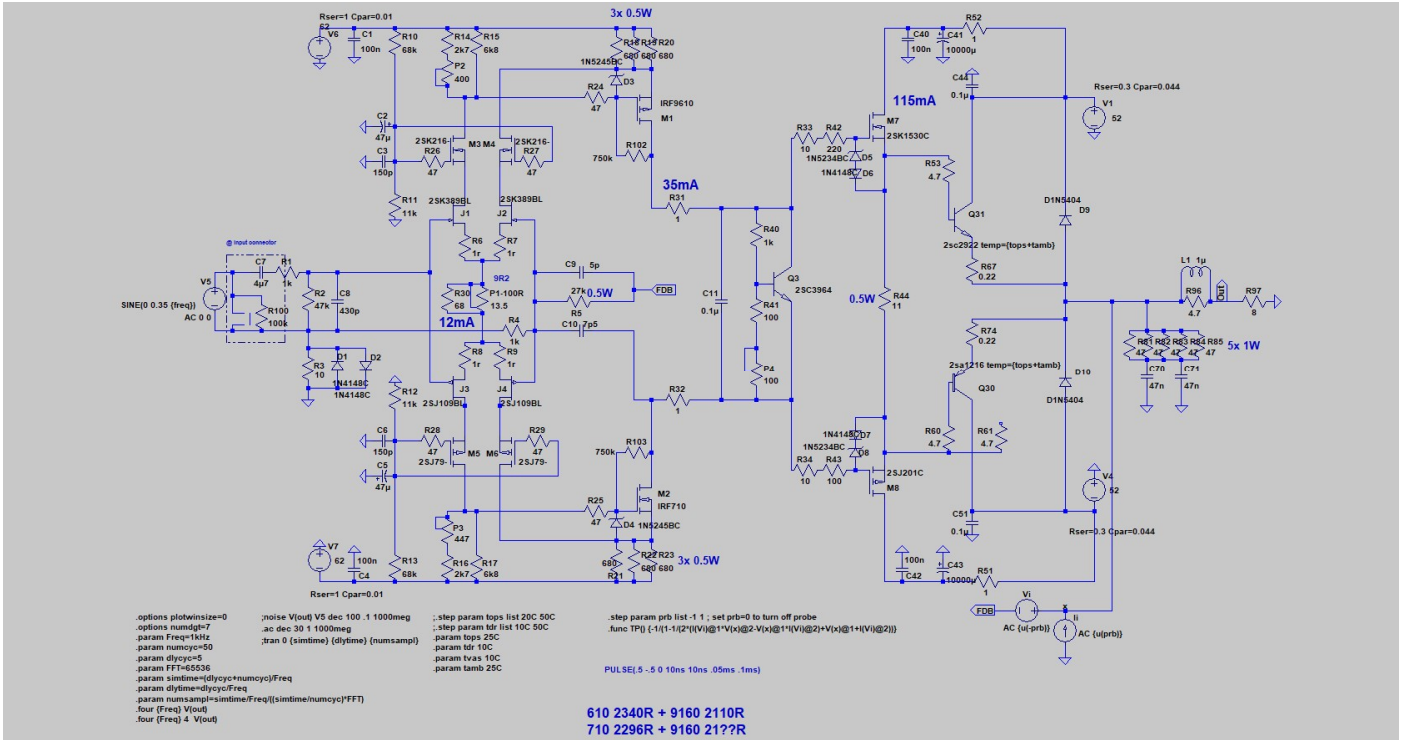



Sinus wave testing in to 80Ohm dummy load → Distorted wave form  
Circuit used, only 1 pair 2SC2922/2SA1216 OPS




Front end B-build PCB.



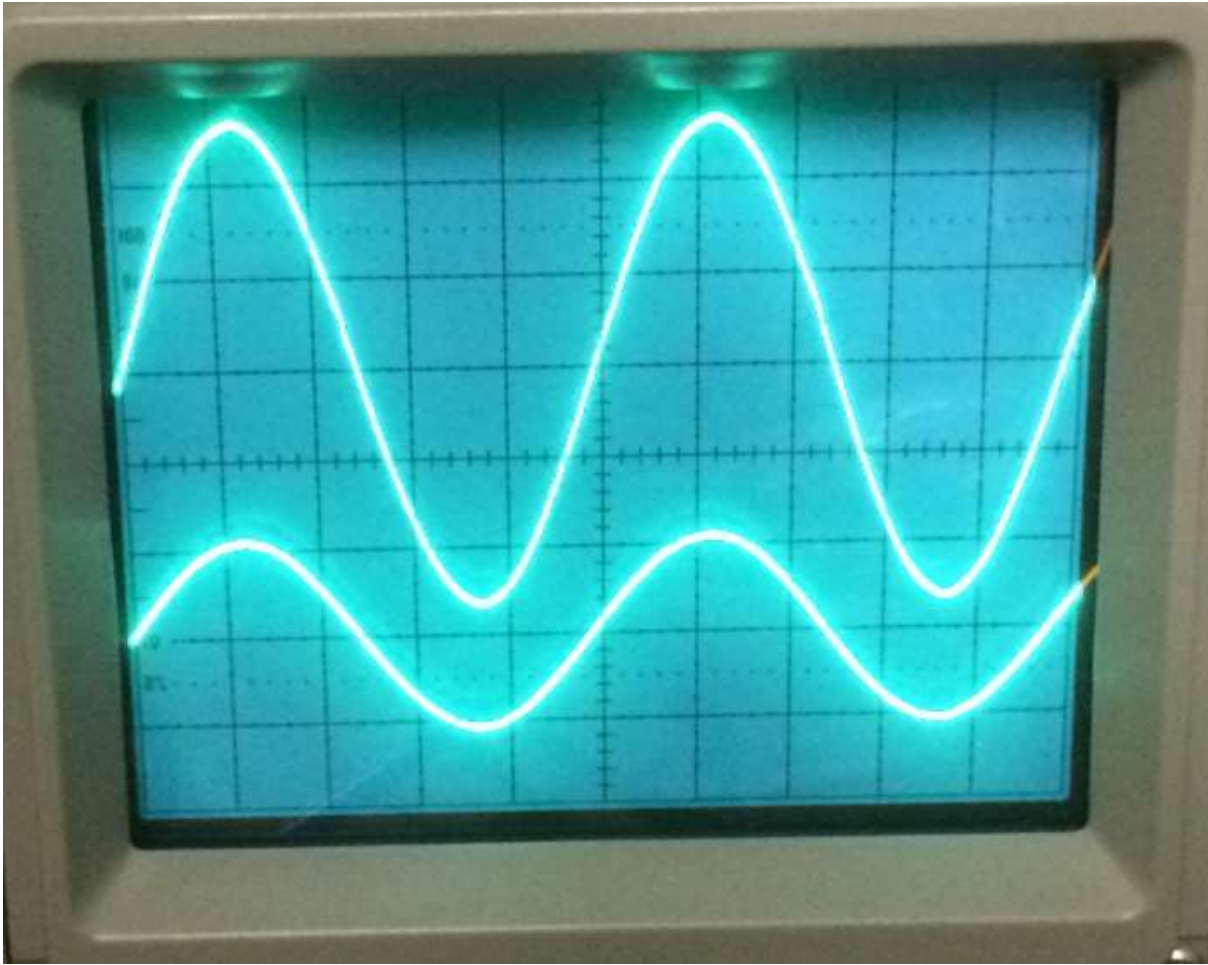Sinus wave testing in to 80hm dummy load → Distorted wave form  
10kHz: wave looks fine



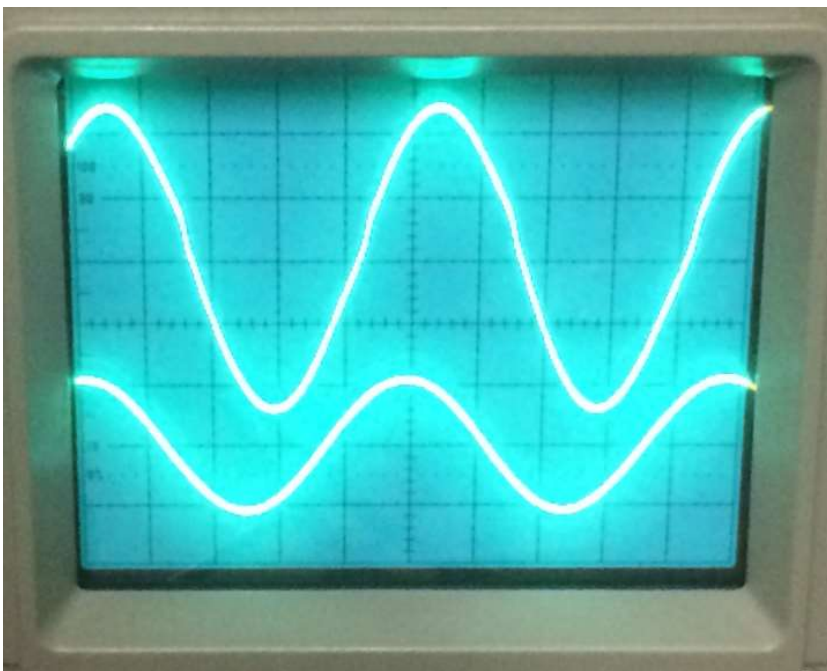100Khz: “vertical” area around crossover point



200Khz: more “vertical” area around crossover point

Sinus wave testing in to 80hm dummy load → Distorted wave form

