
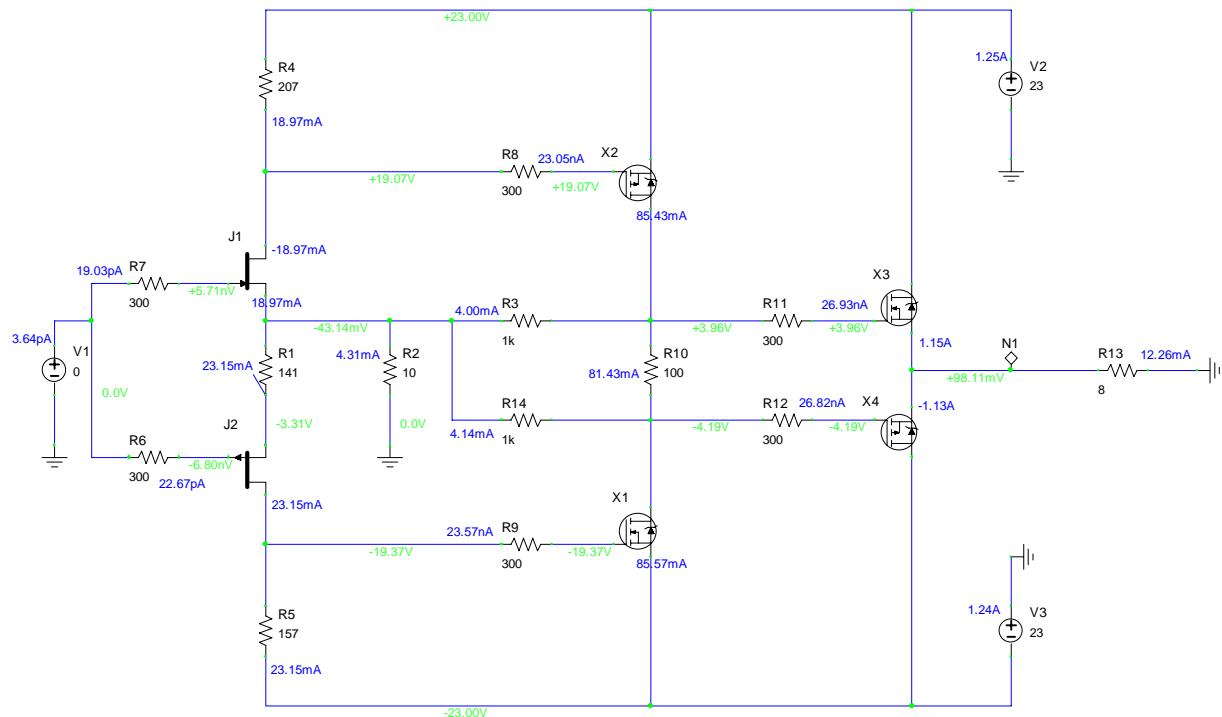


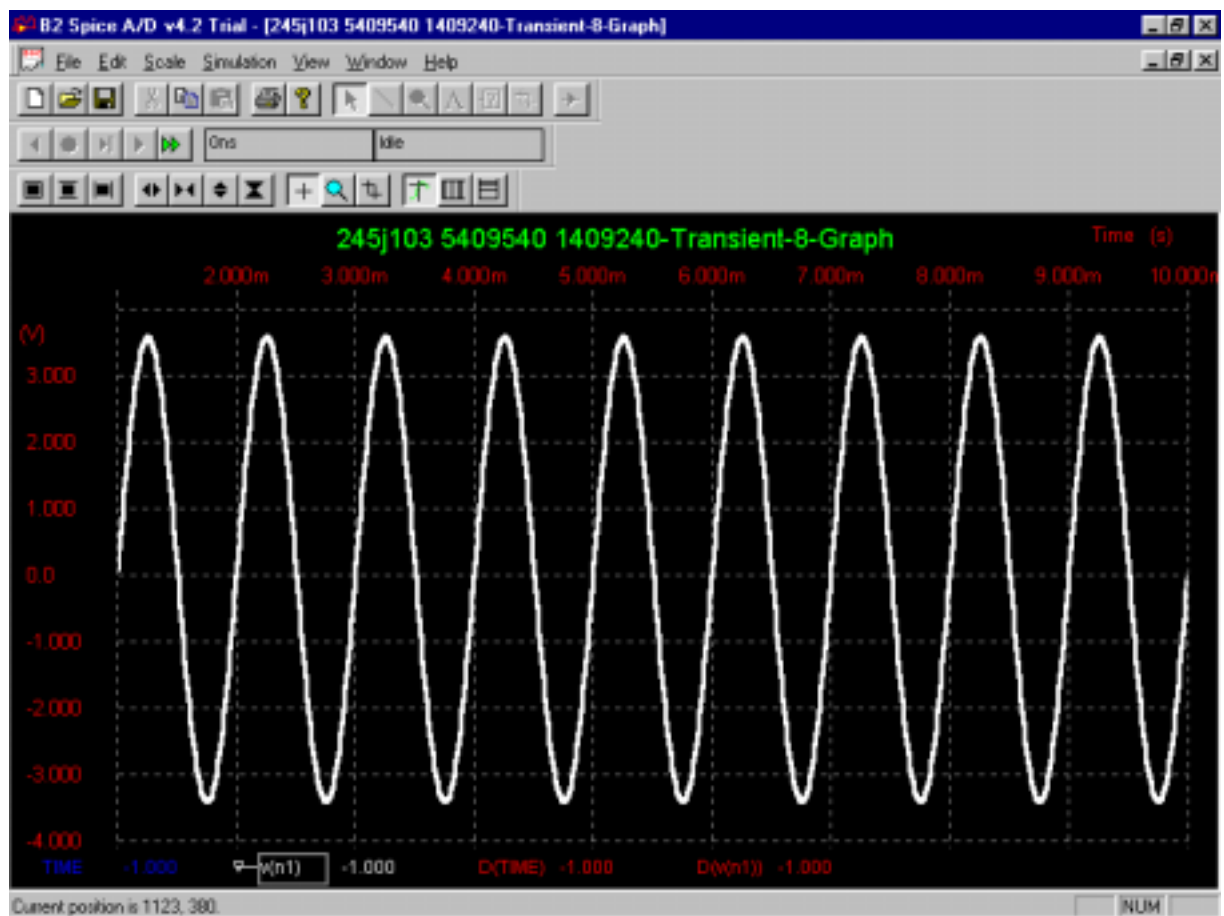
So this is the sketch of schematic (input pair BF245C/2SJ103, then IRF540/9540, then IRFP140/9240 – did not have better models):



This is 1kHz sinusoide at 8 Ohm, input 75mV:



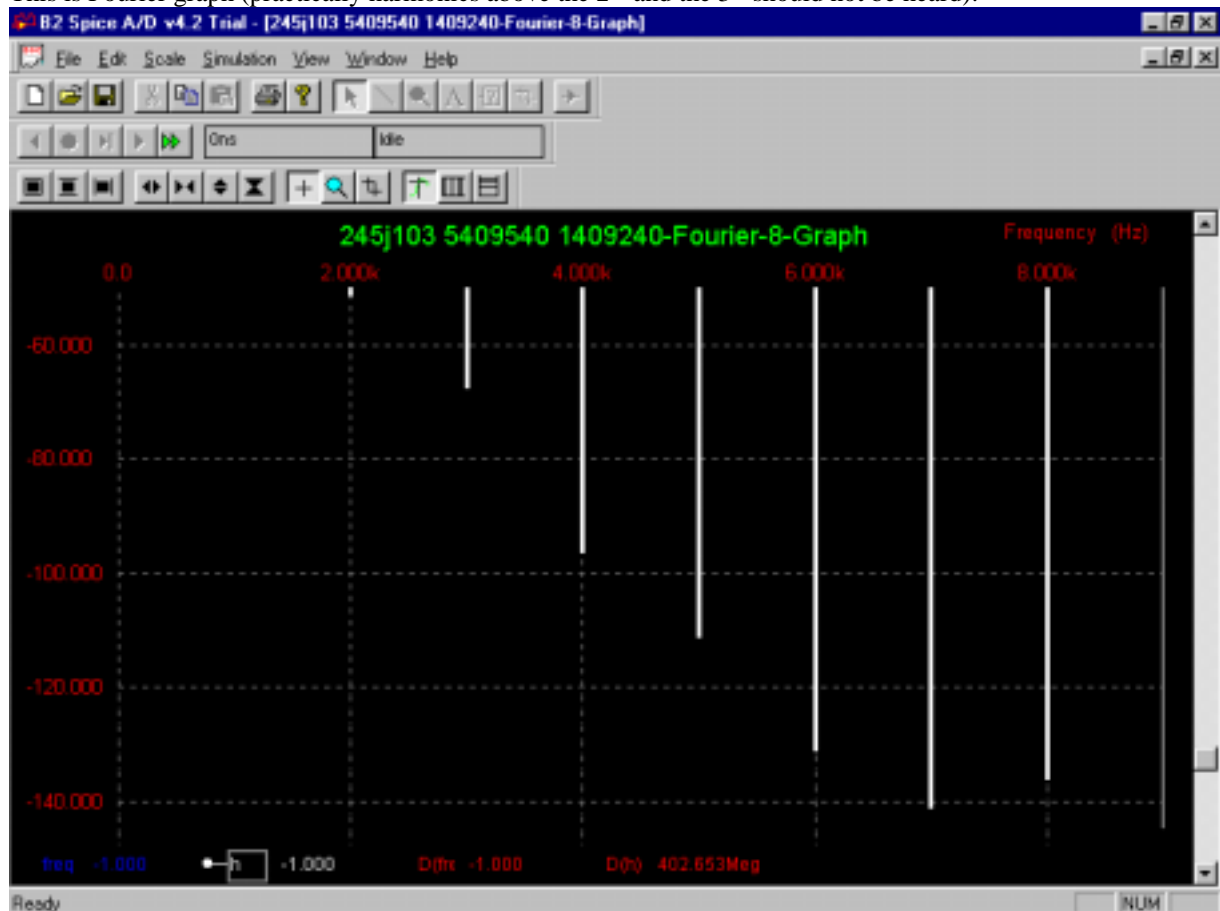This is Fourier graph (practically harmonics above the 2nd and the 3rd should not be heard):



Is it worth to improve?