

Development of a spice op-amp macro-model for current-feedback amplifiers (Part 2 of 2)

By Jian Wang and Tamara Schmitz, Intersil Corp.

(*Part 1* of this article discussed the overall approach, the input stage, gain stage, frequency-shaping stages, noise module, and output stage)

Simulation Results

The simulation results of the macromodel should be compared with the real world device to verify its functionality. The example op amp used in this article is the EL5165, a high-speed current-feedback amplifier. Some SPICE simulation results are compared with the real test curve. (Note: you can find the **EL5165 Macromodel Netlist** below the **About the Authors** box.)

The gain plots in **Figure 9** show a remarkable similarity between our model on the left at a gain of two and measurements from the EL5165 on the right. The measurements from the device are taken at both unity gain and a gain of two. There is less than 1% error between the -3-dB frequency of the two gain-of-two measurements.

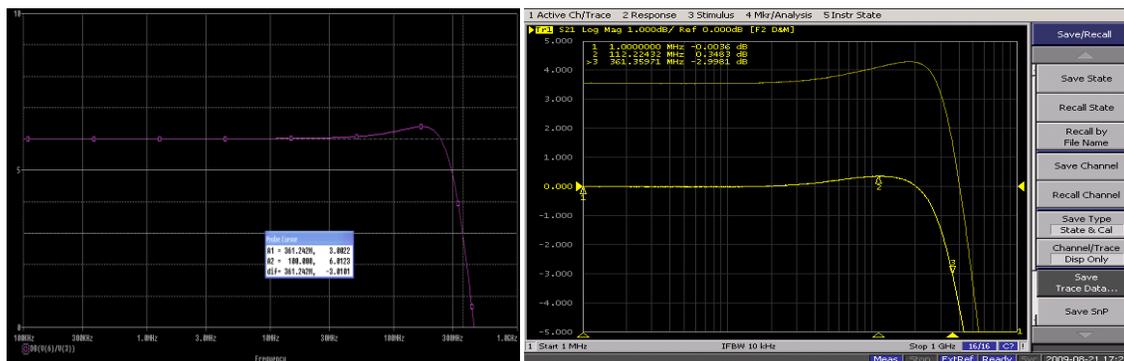


Figure 9: AC response for Gain=+2 of the macromodel (left) and EL5165 device (right).

At a gain of three, the discrepancy increases a bit as shown in **Figure 10**. Now the error in cut-off frequency is within 5%.

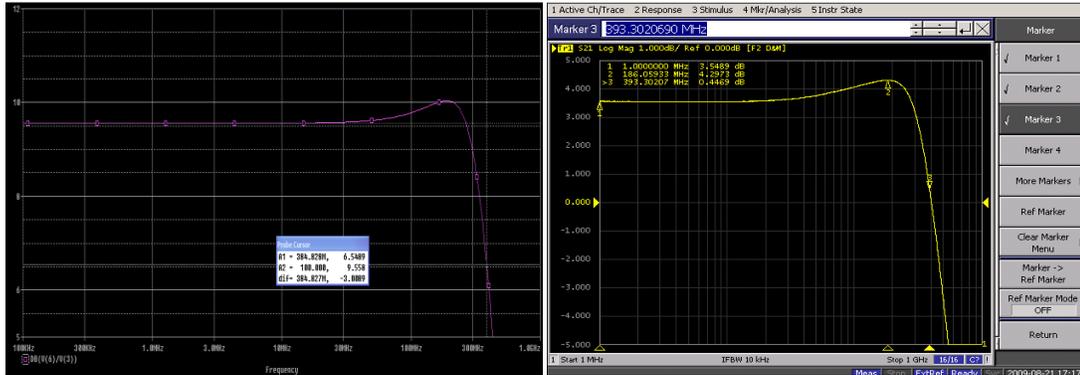


Figure 10: AC response for Gain = +3 of the macromodel (left) and EL5165 device (right).

Since the feedback resistor has an effect on bandwidth, we offer a comparison of frequency response for a range of resistors in **Figure 11**. The values of resistance are listed on the plot on the right that comes from the data sheet. The left plot is from our macromodel. Again, the matching of -3 dB frequency is within 5%.

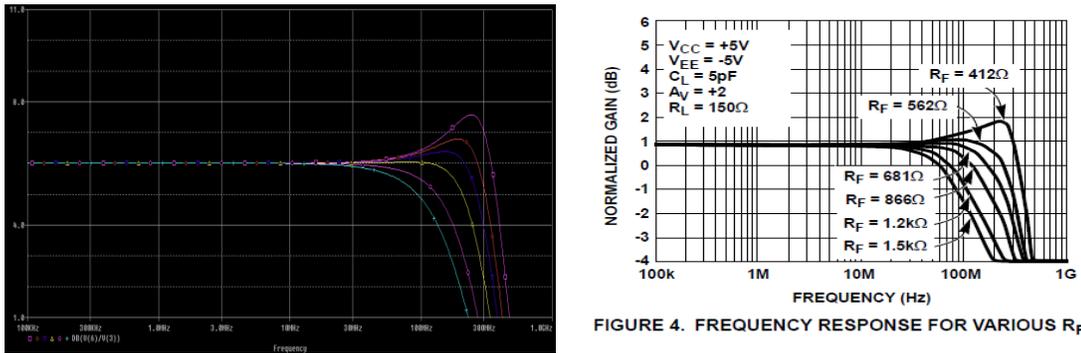


Figure 11: Frequency response with different R_f for the model (left) and the device (right).

After examining the small-signal response versus frequency, the next logical step is to inspect the large-signal response as shown in **Figure 12**. Here we look at the slew rate of the step response with a gain of two driving a load of 150 ohms from a dual 5-volt supply. While the time base (x-axis) is at different resolutions in the two plots, the slew rate of the macromodel shown on the left is 5000 V/us. This is approximately 5% from the slew rate on the output signal of the EL5165 on the right.

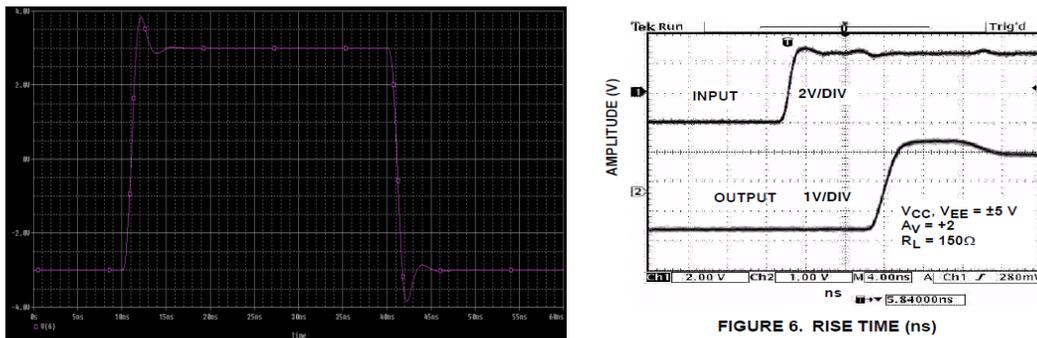


Figure 12: Large-signal step response for the macromodel (left) and from the device data sheet (right).

After frequency response and slew rate, our next goal is to match the noise performance, **Figure 13**. We have chosen to demonstrate the voltage noise, so the model in Figure 6 is included, but not the current noise model from Figure 7. The voltage noise model exhibits the spectrum shown in the plot on the left and has a value of $2.15 \text{ nV}/\sqrt{\text{Hz}}$ at 1 MHz. The datasheet curve for voltage noise is on the right and has a value of $2.1 \text{ nV}/\sqrt{\text{Hz}}$ at 1 MHz.

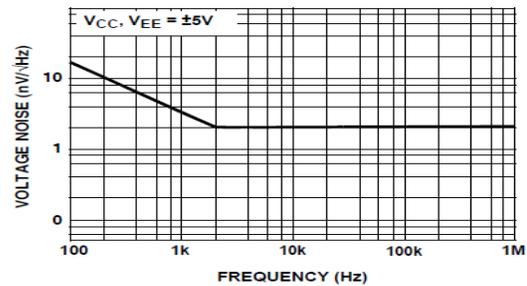
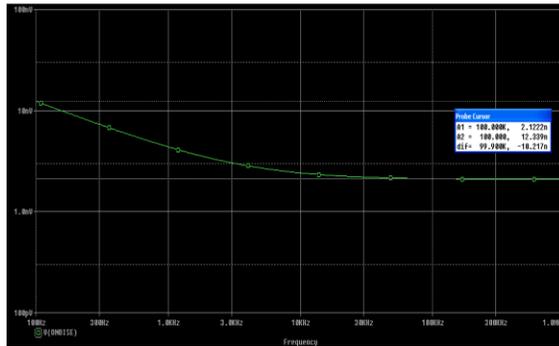


FIGURE 12. VOLTAGE NOISE

Figure 13: Input noise voltage versus frequency for macromodel (left) and device (right).

Conclusion

A truly comprehensive SPICE macromodel for a current-feedback amplifier is developed. This macromodel includes effects such as transfer response, accurate AC response, DC offset and voltage noise. It is convenient to use such a model and change the parameters to fit other current-feedback amplifiers. Several of Intersil's current-feedback amplifiers use the same model topology.

References

1. Derek Bowers, Mark Alexander, Joe Buxton, "A Comprehensive Simulation Macromodels for 'Current Feedback' Operational Amplifiers," IEEE Proceedings, Vol. 137, April 1990 pp.137-145.
2. Mark Alexander, Derek Bowers, "AN-138 SPICE-Compatible Op Amp Macro-Models", Analog Devices Inc., Application Note 138.
3. "AN-840 Development of an Extensive SPICE Macromodel for 'Current-Feedback' Amplifiers", National Semiconductor Corp., Application Note 840.
4. "Current-feedback amplifier Theory and Applications", Intersil Corp., Application Note 9420.

About the authors

Jian Wang was born in China in 1975 and has served as an applications engineer with Intersil since 2005, focusing on high speed amplifiers and drivers. He received a Ph.D. from the University of California at Davis in 2006.

Tamara Schmitz holds BS, MS, and PhD degrees in electrical engineering. She taught analog circuits and test development engineering as an assistant professor at San Jose State University. With eight years of part-time experience in applications engineering, she joined Intersil in August 2007 as a principal applications engineer.

EL5165 Macromodel Netlist

.subckt EL5165 3 2 7 4 6

*

*Input Stage

C_Cin1 0 3 1.8p
V_Vos 1 N4150175 1.5mVdc
I_I1 8 4 DC 85uA dc
I_I2 7 5 DC 85uA dc
I_Ib1 7 1 DC 2uA dc
I_Ib2 7 2 DC 2uA dc
G_Gi1 8 10 8 10 0.001
G_Gi2 5 9 5 9 0.001
G_Gi3 12 4 12 4 0.01
G_Gi4 7 11 7 11 0.01
G_Gb1 7 2 1 16 0.0000001
Q_Q1 7 1 8 Inpn
Q_Q2 11 9 2 Inpn
Q_Q3 4 1 5 Inpn
Q_Q4 12 10 2 Inpn
D_D9 19 11 DX
D_D10 12 18 DX
V_V7 7 19 1.5dc
V_V8 18 4 1.5Vdc
C_C1 9 7 0.03p
C_C2 4 10 0.03p
C_Cs1 2 7 0.25p
C_Cs2 4 2 0.25p
I_I3 7 4 DC 3mA dc

*Gain stage

C_C3 VV2 7 0.405p
C_C4 4 VV2 0.405p
D_D3 13 7 DX
D_D4 4 14 DX
G_G1 7 VV2 7 11 0.01
G_G2 VV2 4 12 4 0.01
R_R7 VV2 7 10meg
R_R8 4 VV2 10meg
R_R17 13 0 1G
R_R18 14 0 1G
V_V5 13 VV2 1.6Vdc
V_V6 VV2 14 1.6Vdc

*High-order poles

E_E3 16 4 7 4 0.5
C_C5 VV3 7 0.0032p
C_C6 4 VV3 0.0032p
C_C7 4 VV4 0.0009p

C_C8 VV4 7 0.0009p
 C_C9 4 VV5 0.0001p
 C_C10 VV5 7 0.0001p
 R_R9 VV3 7 100k
 R_R10 4 VV3 100k
 R_R11 VV4 7 100k
 R_R12 4 VV4 100k
 R_R15 VV5 7 100k
 R_R16 4 VV5 100k
 G_G3 4 VV3 VV2 16 0.00001
 G_G4 7 VV3 VV2 16 0.00001
 G_G9 7 VV4 VV3 16 0.00001
 G_G10 4 VV4 VV3 16 0.00001
 G_G11 7 VV5 VV4 16 0.00001
 G_G12 4 VV5 VV4 16 0.00001

*Output stage

G_G5 15 4 6 VV5 0.0001
 G_G6 17 4 VV5 6 0.0001
 G_G7 7 6 7 VV5 -0.04
 G_G8 6 4 VV5 4 -0.04
 R_R13 6 7 25
 R_R14 4 6 25
 D_D5 7 15 DX
 D_D6 7 17 DX
 D_D7 4 15 DY
 D_D8 4 17 DY

*Voltage noise

E_EN N4150175 3 101 103 1
 V_V15 102 0 0.5Vdc
 V_V16 104 0 0.5Vdc
 D_DN1 102 101 Iden
 D_DN2 104 103 Iden
 R_R21 0 101 55
 R_R22 0 103 55

*Current noise

R_R23 0 NI2 0.022
 R_R24 0 NI2 0.022
 R_R25 0 NI1 0.022
 R_R26 0 NI1 0.022
 G_Gn1 3 0 NI1 0 1
 G_Gn2 2 0 NI2 0 1

*

* Models

*

.model Ipn pnp(is=1e-15 bf=1E9 VAF=65)
 .model Inp npn(is=1e-15 bf=1E9 VAF=65)

```
.model Iden d(kf=100e-14 af=1)
.MODEL DY D(IS=1E-20 BV=50 Rs=1)
.MODEL DX D(IS=1E-15 Rs=1)
.ends EL5165
```