

# Subtractive Crossovers by Bansuri

## 1<sup>st</sup> Order BW

A **subtractive** crossover doesn't introduce additional phase change or delay, a **square wave** is perfectly reproduced, the drivers have to be wired **in phase**.

It has a flat impedance and power curve, perfect for tubes; but what happens when speakers and enclosures are added?

Each speaker has a low and high frequency -3dB point. The low end is well defined of at least second order and easily measurable. The upper limit has to be guessed from a frequency plot.

Several effects like cone break-up, cone shape, resonances and reflections on small obstacles (screws, gaps) and baffle/waveguide superimpose with the inductive impedance rise. Generally a 2<sup>nd</sup> order low-pass plus a notch filter can approximate radiation sufficiently.


## Driver Selection

**Tweeter:** Scan-Speak [10F4424-01](#) one of the finest fullrange drivers

With a notch at 9kHz a very linear response.

2L closed with 20g  
Angle-Hair damping

125Hz, Q= 0.48

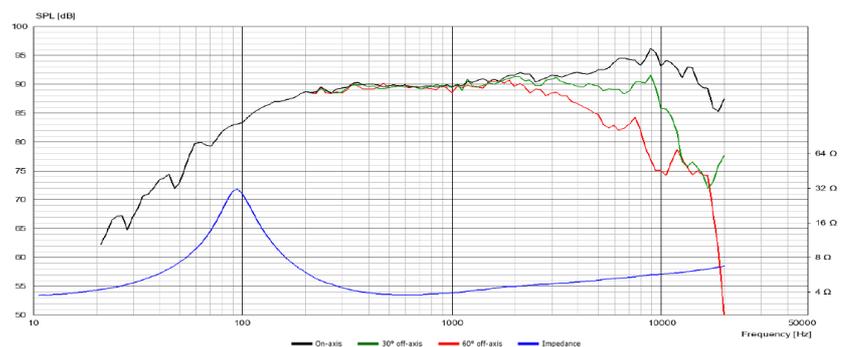


**Woofers:** Scan-Speak [18W8535-01](#) wideband and linear, 2 in parallel

2x28L vented f-3= 38Hz

2x20L closed f-3= 50Hz


2x11L closed + serial C  
f-3= 48Hz, 1200uF





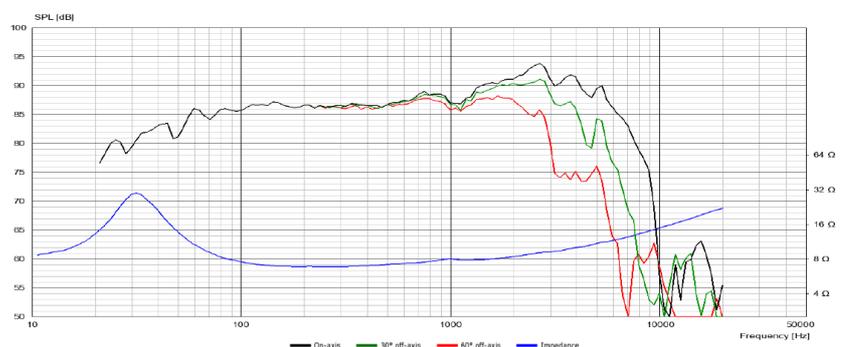
With 5mm excursion only  
96dB SPL @45Hz can be  
reached in a closed  
enclosure ⇒ dual.



Notch filters, better  
all active to avoid  
interaction with XO  
components.

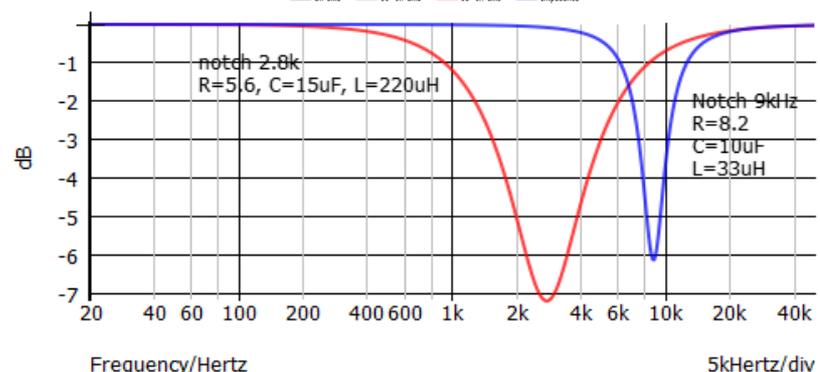Some simulations with  
the smallest enclosure.



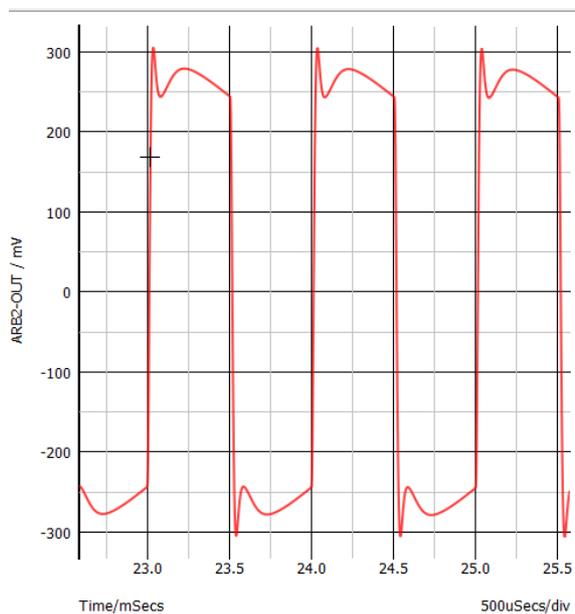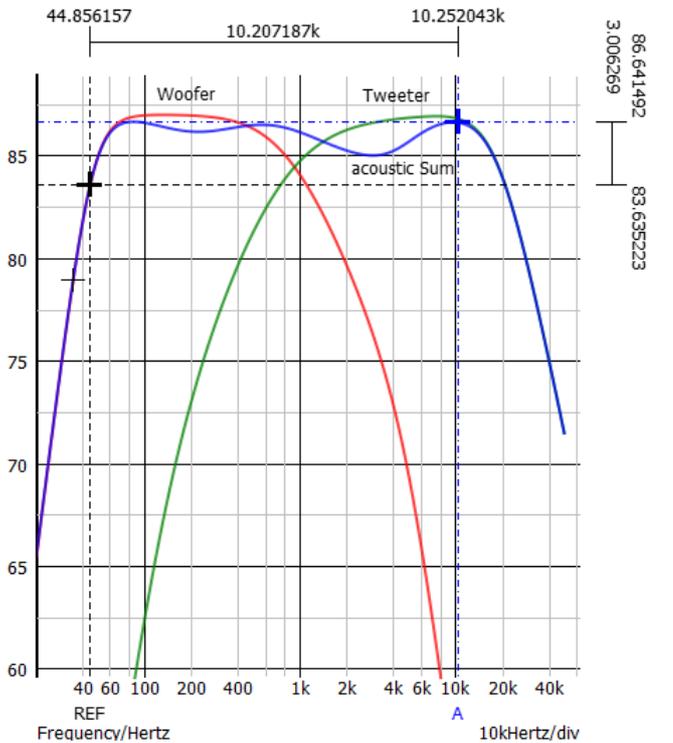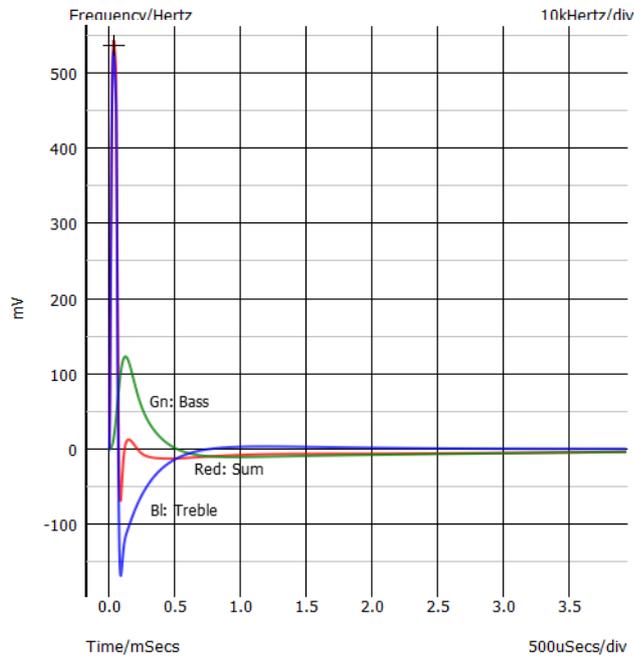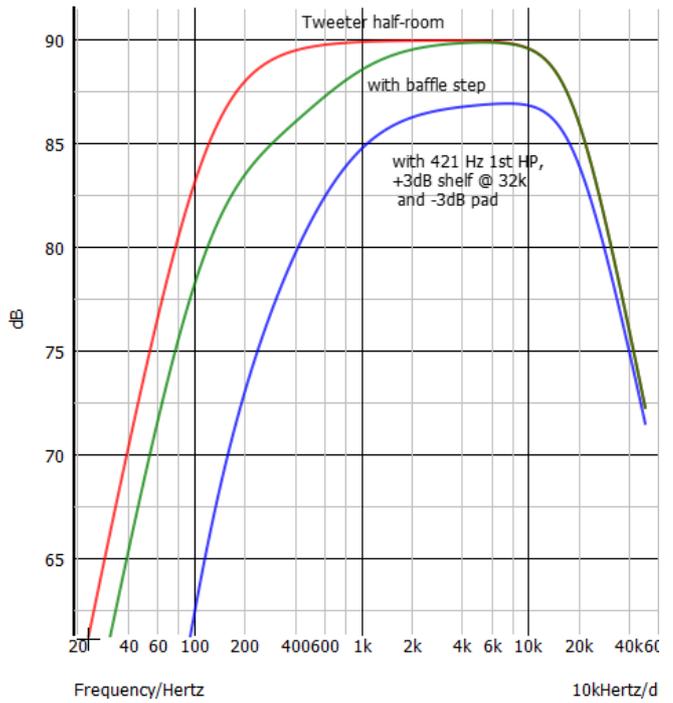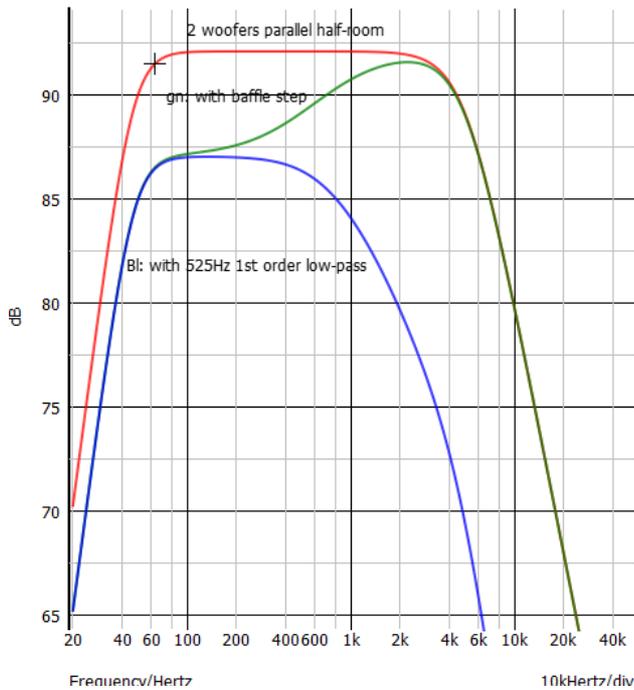


Baffle 25cm wide

Pulse response and 1k Square show the advantage of subtractive X-overs. No pre-echo or additional delay.

The effect of the low end resonance of the tweeter and  $f_{high}$  of the woofer is visible as (small) dips in the response.

It can be realized with passive components.

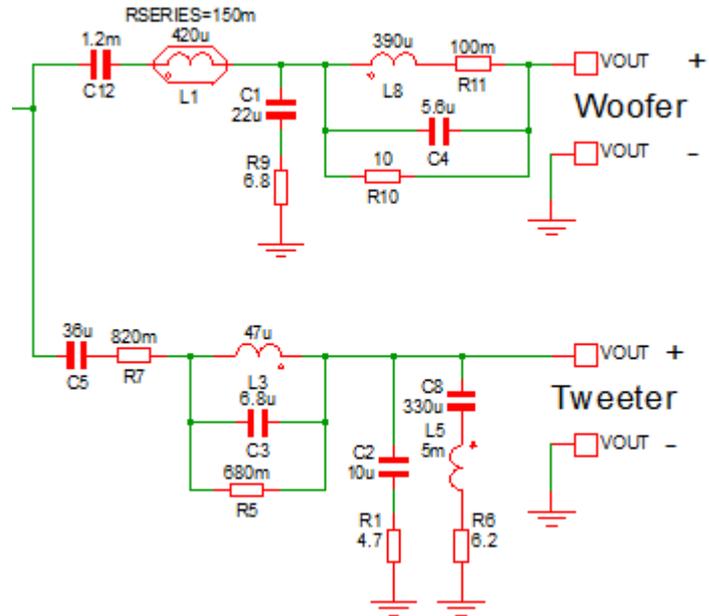Just a rough estimate of values for a passive implementation.  
 With a 100W amp 103dB SPL is reached.





## 2<sup>nd</sup> Order modified Gauss

Laplace:  $1 = (1+s)^4 / (1+s)^4 = (1+4s+6s^2+4s^3+s^4) / (1+s)^4$   
 cutting:  $(1+4s+3s^2) / (1+s)^4 + (3s^2+4s^3+s^4) / (1+s)^4$

1<sup>st</sup> part = Woofer  $(1+4s+3s^2) / (1+s)^4 = (1+s)+3s(1+s) / (1+s)^4$   
 $= (1+s)(1+3s) / (1+s)^4 = 1 / (1+s)^2 * (1+3s) / (1+s)$

So the 2<sup>nd</sup>Gauss  $1 / (1+2s+s^2)$  multiplied with a shelf  $(1+3s) / (1+s)$

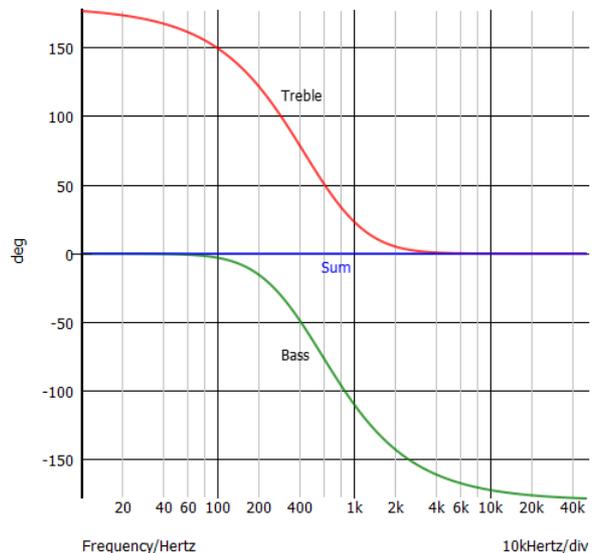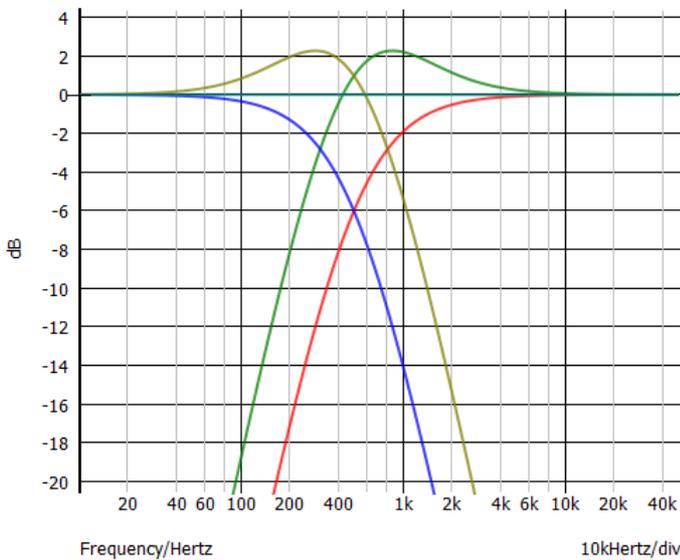
2<sup>nd</sup> part = Tweeter  $s^2 / (1+2s+s^2) * (3+s) / (1+s)$



Theoretically 100% flat frequency- and phase-response.  $X0=500\text{Hz}$

When we add the drivers low and high ends need to be perfectly matched, to avoid a boost or dip at the xover frequency.

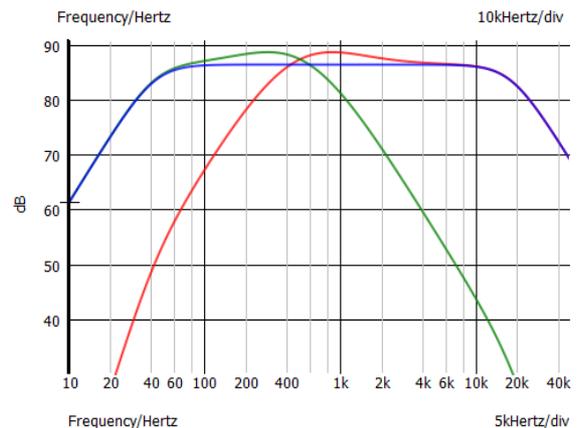The drivers overlap from 100Hz to 2kHz, the boost is +2.2dB near the  $X0$  frequency.



The woofers were limited by the excursion, there is no problem to boost the treble with a bigger amp, but the tweeter would not allow the boost because of thermal limit.

It is easy to add a midrange which could work together with the tweeter:

$$s^2/(1+2s+s^2)*(3+s)/(1+s) =$$


$$s^2/(1+2s+s^2)*s/(1+s) + s^2/(1+2s+s^2)*3/(1+s)$$

tweeter                      midrange

This solution is very convenient, the tweeter can output a higher level 105dB.

The mid should be very broadband, as the slope to the tweeter is only 6dB/oct

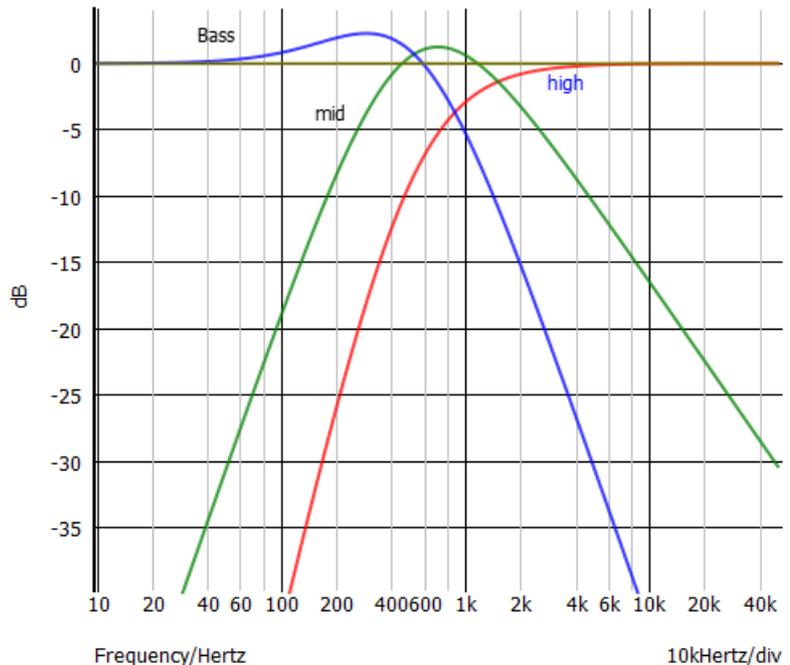We could do the same with the bass and have a 4-way XO with a single 500Hz crossover frequency.



A perfect pulse response:

