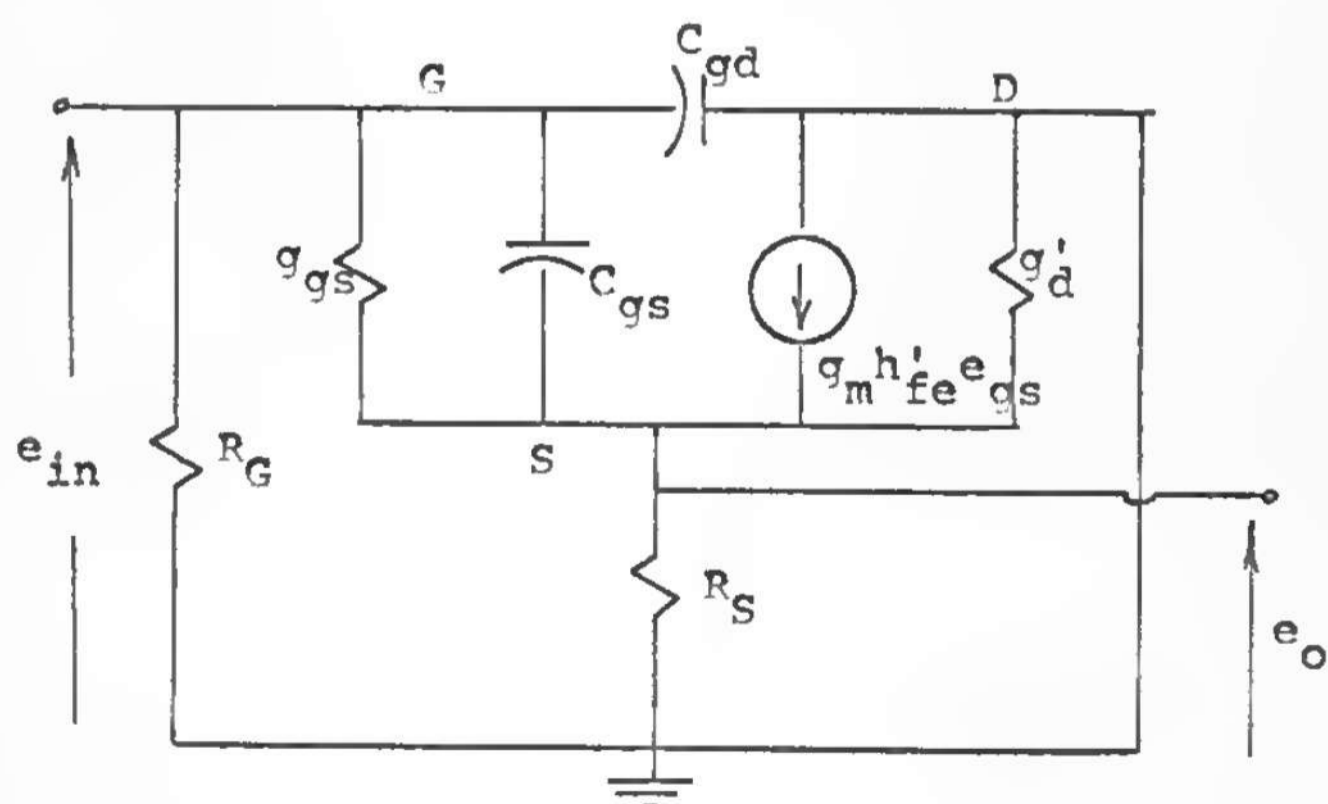


(a)



(b)

Fig. 20 (a) Unipolar-bipolar cascade amplifier  
(b) Equivalent circuit.