

TUBE AMP POWER SUPPLIES.

Contents of this page includes:-

Definition of linear power supplies.

Fig 1. Basic wave forms for V_{ac} and I_{ac} in rectifier circuits.

Earthing all devices for safety.

Mains Active, Neutral and Earth.

Basic operation of C, L in CLC filters.

Fig 2. PSU for 8585 amp, 2011.

List of all power supply requirements for a tube amp.

Discuss peak currents in diode rectifiers.

Fig 3. SHEET 3. 300W amp PSU chassis.

Fig 4. SHEET 4. 300W amp chassis.

Fig 5. Crest Factors for various wave forms.

I had many questions about power supplies. "Power supply" usually means a "linear" type with mains power transformer, diode rectifiers, capacitors, chokes, possibly protection circuitry and regulators.

Linear power supplies are different to switch mode power supplies, SMPS, which rectify the incoming 50Hz or 60Hz mains frequency without a heavy mains transformer. A single electrolytic C is charged by diodes so that 240Vrms mains makes +335Vdc. A solid state circuit converts the stored energy to a HF square wave, usually above 100kHz, and this is fed to a very small HF transformer with ferrite core to make square wave output that has peak V_{ac} equal to wanted Vdc.

Diodes charge small value C to make the wanted Vdc without any 50Hz ripple, and there may be a small LC filter to remove the small amount of 200kHz ripple.


SMPS are 1/20 of the weight and size of the traditional linear types. They are routinely used in all PCs and in many solid state amps.

AFAIK, no manufacturer has ever made a tube amp with a SMPS power supply to give say +450Vdc and say +6.3Vdc for B+ and for tube heaters.

In all tubed amplifiers, the mains V_{ac} is applied across a primary winding which has no direct connection to several secondary windings which may produce say 330Vac to make +450Vdc, and 6.3Vac for output tube heaters, and 50Vac for a -70Vdc bias winding. Such simple linear PSU do not have any complex solid state devices beyond silicon diodes or some discrete transistors for regulation.

Fig 1. Basic wave forms.

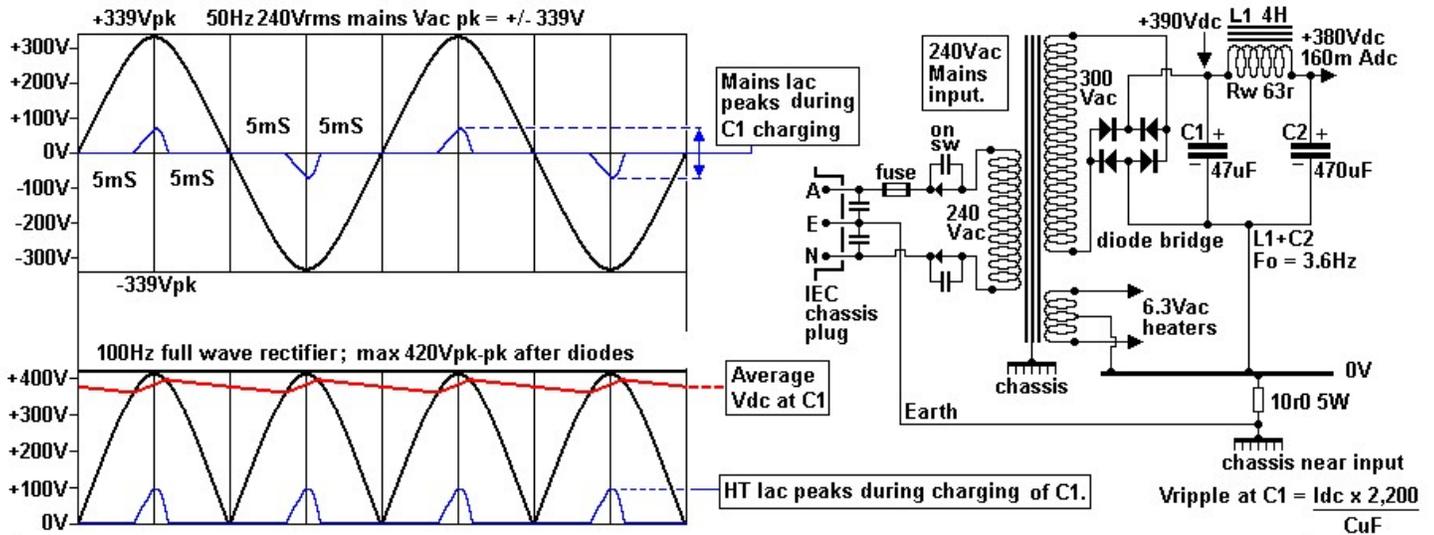BASIC WAVE FORMS FOR FULL WAVE RECTIFIER WITH 50Hz MAINS Vac.



The waveforms in rectifier circuits rectifier should be understood to avoid excessive Vpk across diodes and excessive current peaks. I show a brief schematic for B+ where a 300Vac HT winding makes approximately +380Vdc at 160mAdc at output of CLC filter.

The first issue is safety.

All power amps and preamps with PSU MUST have their chassis connected directly to the Earth connection at IEC socket.

The connection point should away from PT and to chassis near input, with thick green-yellow cable well bolted to chassis.

The 0V rail of the amp can be connected to chassis near input using 10r0 x 5W. This avoids noise between Earth and 0V rail getting to input of amp.

For E+I power transformers, their yokes holding transformer and or pot must be well bolted to the chassis.

There are two wires coming into your house from the mains. One is black, and called the "Neutral" wire and is connected to ground at the house circuit distribution board via an earthing wire to copper water pipes or a copper clad stake buried in the ground. Vac between Earth and Neutral wires at amplifier is always a very low Vac.

The Vac between Active mains wire and Neutral wire = 240Vac in Australia (or other Vac in your country).

The Active Vac moves to +/- 340Vpeak as shown above and its shape is often not a perfect sine wave as shown, but has flat tops and bottom to peaks because so many people have devices connected which have rectifiers which cause high peak currents

at near maximum peak Vac swings.

House wiring in Australia uses red for Active, black for Neutral, green-yellow for Earth, and white for switched wires. All appliances which require their cases to be connected to Earth directly can be accommodated such as washing machines, but the energy carrying circuit is via the red and black wires.

In the US the mains active is about 110Vrms, and has $F = 60\text{Hz}$.

The Vac wave shape of primary input is the virtually the same within HT or any other secondary winding.

The diode bridge switches the direction of current flow in HT winding of each 1/2 wave of 50Hz so that the peak Vac is applied to C1. The output Vac wave after diodes is 100Hz with $V_{pk-pk} = V_{pk}$ of HT winding, and it contains a lot of 200Hz, 400Hz harmonic content plus Vdc content. The C1 is thus charged up with Vdc to nearly same as the peak Vac in HT winding. Winding losses and diode resistance cause the Vdc at C1 to always be less than the V_{pk} of HT winding.

Without any Idc flow, C1 will charge up to within $2V_{pk}$ of HT V_{pk} . So for a 300Vac winding, expect +420Vdc with no Idc load but when Idc flows, Vdc sags, and HT Vac also sags.

The non loaded ratio of Vdc : Vrms at HT = 1.4, but with Idc loading it may be 1.35 or much lower especially if vacuum diodes are used.

With no Idc flow, C1 and C2 have the same Vdc and there is no ripple Vac.

The diodes conduct for a small % of each 50Hz 1/2 wave. With 0.16Adc, I show conduction time = 2.3mS for each 1/2 wave of 10mS. For the Vdc to remain at a stable level, the power flowing out of C1 for 10mS must be equal to the power flowing in for 2.3mS. Thus it becomes obvious that when diodes conduct, their Ipk must be higher than Idc flow, and average Idc flow in diodes = $10 / 2.3 \times 0.16\text{Adc} = 0.696\text{A}$ and the peak charge idc = average charge current / 0.63 = $0.67\text{A} / 0.63 = 1.1\text{A}_{pk}$.

So the peak charge current can be much more than the Idc flow. But it is reduced by winding resistance losses.

There is Vac at C1 which will look like a saw tooth wave on CRO when examined.

You will usually see the V wave during C charge being steeper and lasting less time than the V wave when no charge is occurring and Idc is lowering Vdc at a rate governed by the time constant behavior of C1 and the amp input resistance. The time constant here is governed by $R = B+ / Idc = +380\text{V} / 0.16\text{A} = 2,375r$, and C1 value.

Time constant in S = $CuF \times R / 1,000,000 = (47uF \times 2,375r) / 1,000,000 = 0.111\text{Secs} = 111\text{mS}$. With no charging continuing, if Idc were to remain constant, Vdc falls at a constant rate to 0V in 111mS.

The amount of Vdc drop for 7.7mS = $380\text{V} \times 7.7\text{mS} / 111\text{mS} = 26.4\text{V}$, and this equals the V_{pk-pk} for ripple and each 1/2 wave of ripple = 13.2Vpk.

Because there is triangular wave, the Vrms value for Vripple = $0.577 \times V_{pk} =$

$13.2V_{pk} \times 0.577 = 7.6V_{rms}$.

A simpler way of working out Vripple for 50Hz is $V_r = I_{dc} \times 2,200 / C_u F$

and this case $V_r = 0.16A_{dc} \times 2,200 / 47\mu F = 7.5V_{rms}$. The $V_{pk-pk} \text{ ripple} = 3.4 \times V_{rms} = 25.8V_{pk-pk}$ which agrees with basic time constant calcs.

For the formula $V_r = I_{dc} \times 2,200 / C_u F$ to be correct, the $I_{dc} \text{ load} > 20 \times X_c$.

The L1 + C2 act as second order low pass LC filter.

They have $F_o \text{ pole} = 5,035 / \text{sq.rt} (L \text{ in mH} \times C \text{ in } \mu F)$

$= 5,035 / \text{sq.rt} (4,000\text{mH} \times 470\mu F) = 3.67\text{Hz}$.

At this F, L1 and C2 form a series resonant network which is not damped by low enough R to prevent LF resonance which tends to favor noise between 2Hz and 6Hz.

However, this is well below AF band and causes no trouble.

The $100\text{Hz} \text{ attenuation factor} = X_c / X_L \text{ at } 100\text{Hz}$.

$X_c = 159,000 / (C_{\mu F} \times F) = 159,000 / (470\mu F \times 100\text{Hz}) = 3.38r$.

$X_L = L \text{ in H} \times 2 \times \pi \times F \text{ Hz} = 4\text{H} \times 6.28 \times 100\text{Hz} = 2,512r$, so

Attenuation factor $= 3.38r / 2,512r = 0.00134$, so V_r at CLC output is reduced to $7.6V_{rms} \times 0.00134 = 0.01V_{rms}$, and this is not going to create any audible intermodulation harmonics in amp output.

The typical noise at C2 is mainly all below 10Hz, but typical total can be $50mV_{rms}$, not large enough to cause audible distortion at amp V_o .

When silicon diodes were invented, bridge rectifiers and voltage doubler arrangements which are shown in textbooks were rapidly adopted to replace vacuum diodes because they offered much greater efficiency, lower cost and far better V_{dc} regulation with change of I_{dc} due to their low "on" resistance.

Tube rectifiers have considerable series resistance often above $50r$ when conducting current and thus dissipate heat from their anodes and they need power to heat their cathodes. So tube rectifiers help make the chassis hot, but do nothing to improve the music.

There are strict limitations on the C value being charged by tube diodes because allowable peak charge currents are typically less than 250mA .

Exceeding this value with C1 being too high causes internal arcing and rapid tube diode failure. But a single 1N5408 has rating for $3A$ continuous, $R_{on} < 1r0$, and peak I_{dc} can be higher than $3A$.

With Si diodes, C1 could be $1,000\mu F$, but there is no need. Use of $220\mu F$ is OK, and V_r at C1 = $1.6V_{rms}$. But peak charge current is increased. But it is limited by the winding resistances, and 1N5408 has high enough current rating to handle $1,000\mu F$, even at turn on when very high peak charge currents flow to get V_{dc} high within 1 second after turn on.

The high peak charge currents with Si diodes and high C values could cause problems

with noise if the earth path is not correctly done.

The wires between diode cathodes and + terminal of C1 and between diode anodes and - terminal of C1 should be short, but not include any length along the 0V rail which usually is a 2mm dia copper wire about 300mm long between PSU and amp input.

Half wave rectifiers can be used where there is not high I_{dc} and V_{ripple} does not matter much.

The 1/2 wave rectifier may have the same V_{ac} at the 300Vac winding shown, but one end is taken to negative terminal of C1, with other end feeding C1 through 1N5408 to positive terminal of C1.

V_r for half wave rectifier = $I_{dc} \times 4,400 / C_{uf}$, so in this case, $V_r = 15.2V$ at C1. The attenuation factor of L1 + C2 = $6.76r / 1,256r = 0.0054$. So for the same CLC, 50Hz V_{ripple} at C2 = $0.081V_{rms}$, which is 8 times higher than with full wave rectifier.

All electrolytics must have high enough ripple current rating and V_{dc} rating.

Ripple current = V_{ac} / XC at 100Hz. For C1 = 47uF, and $V_r = 7.6V_{rms}$, $I_r = 7.6V / 33.8r = 0.22A_{rms}$, and most 47uF x 450V now made have much higher I_r rating because they are designed for SMPS where I_{dc} may be much higher than for a tube amp channel here which might supply 2 x KT88 plus its input tubes.

V_{dc} may be +390Vdc when I_{dc} flows. But with no I_{dc} , V_{dc} may rise to +420Vdc. Thus C1 and C2 must be rated for at least +450V. If tube diodes were used, to get +380Vdc with I_{dc} , the HT winding would have to be about 340Vac, and with no I_{dc} the V_{dc} could soar to +480Vdc, and the 450Vdc caps may arc internally and fail to become a short circuit.


Where V_{dc} is expected to be high without normal I_{dc} flow, use 470uF x 350V in series with R divider to ensure equal V_{dc} is across both C. The high V_{dc} can occur after turn on before power tubes warm up after 15 seconds. With 5U4 vacuum diodes which have directly heated cathode their warm up time is 2 seconds, so B+ can go much higher than the normal working value before the I_{dc} flow in tubes reduces the B+. So an amp with CT HT sec = 350V-0-350V and 5U4 will make B+ = +490Vdc but when output tubes conduct the B+ falls to +410Vdc, so V_{dc} to V_{ac} conversion factor = $410V_{dc} / 350V_{ac} = 1.17$.

The design of the power supply isn't difficult if we follow a path through a series of equations. I will base my mathematical processes upon an example of a power supply for the [8585 amplifier](#) :-

Fig 2. 8585 amp, latest version 2011.

8585 INTEGRATED 2 CHANNEL AMP. 2011

www.turneraudio.com.au

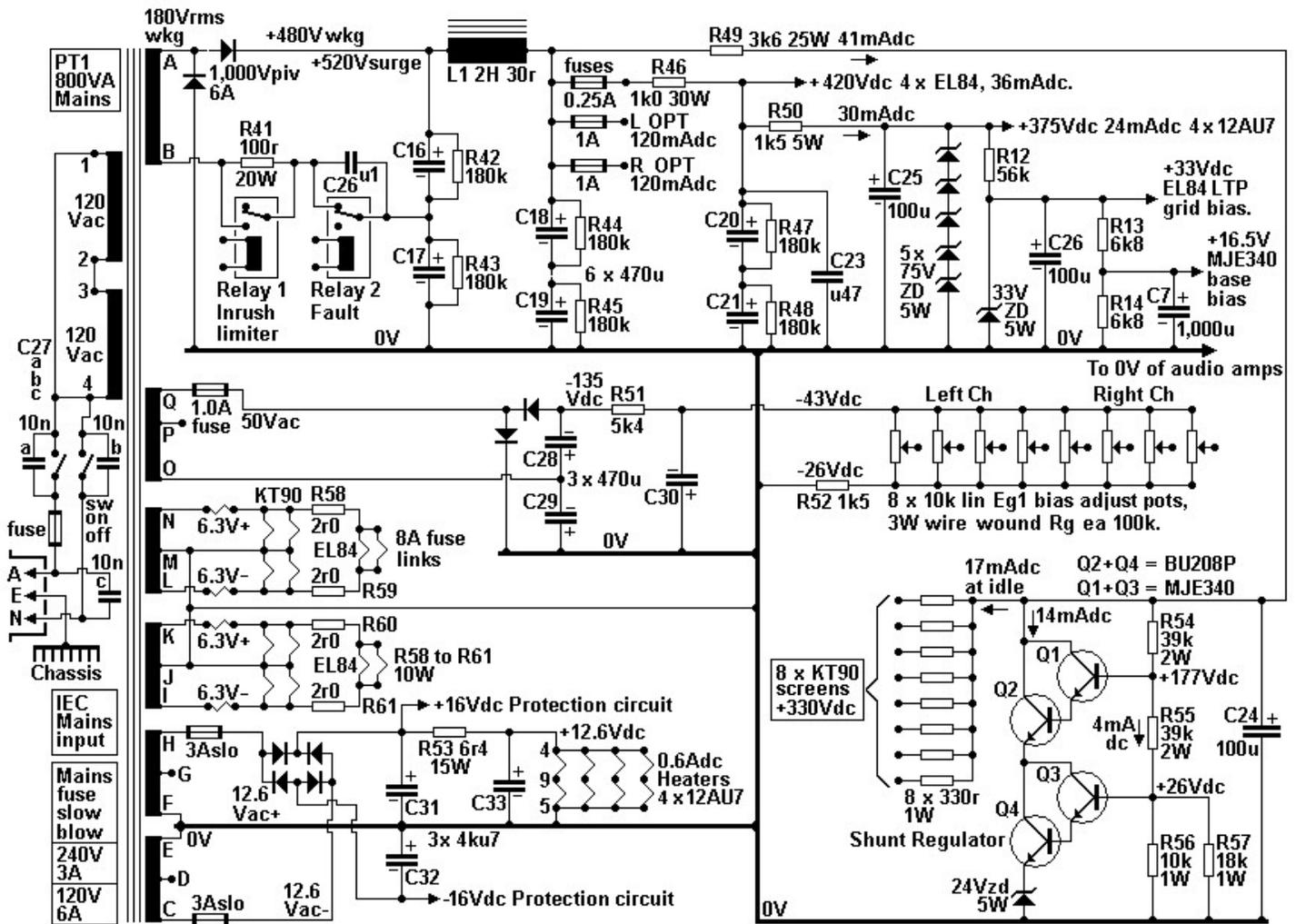

The above looks extremely complex, but it just uses repetition of a few basic simple ideas.

The principles in the explanation of the above can be applied to any other tube amp supply.

B+ plate supply.

The 8585 had two channels each with 4 x 6550 / KT88 / KT90, plus total of 4 x EL84, and 4 x 12AU7 input tubes.

Power needed for each function = $I_{ac} \times V_{ac}$ at output of Sec windings, of $I_{dc} \times V_{dc}$ at output of diode rectifiers.

I_{dc} at B+ needed :-

Anodes KT90, 2 x 4 x 30mAdc = 240mAdc at idle.

At 100W continuous, both channels, max I_{dc} = 720mAdc.

Screens KT90, (2 x 4 x 2.2mAdc) + (I_{dc} in shunt regulator) = 41mAdc.

Anodes EL84, 4 x 9mAdc = 36mAdc.

Anodes 12AU7, 4 x 6mAdc + plus shunt regulation 6mAdc = 30mAdc.

Miscellaneous other = 5mAdc.

Total maximum B+ I_{dc} = 672mAdc = 832mAdc.

The max B+ power = $0.832\text{A} \times 480\text{Vdc} = 399\text{W}$.

If the HT winding is designed for 400W the winding will remain cool for most operation where total Idc power = $352\text{mAdc} \times 480\text{Vdc} = 169\text{W}$.

Losses in Si diodes may be neglected, $< 3\text{W}$.

Heater power needed :-

KT90, $8 \times 6.3\text{Vac} \times 1.8\text{A} = 90.72\text{W}$.

EL84, $4 \times 6.3\text{Vac} \times 0.8\text{A} = 20.16\text{W}$.

12AU7, $4 \times 6.3\text{V} \times 0.15\text{A} = 3.8\text{W}$.

Losses = 5W, including in Idc rectifier for 12AU7 heaters.

Total heater power = 120W.

Bias Vdc for 8 x adjust pots for fixed bias = $135\text{Vdc} \times 0.017\text{A} = 2.3\text{W}$.

Total maximum power to amp from all Secondary windings of PT = $399\text{W} + 120\text{W} + 2.3\text{W} = 521\text{W}$.

Maximum power input to PT = 444.4W plus winding losses of 5%, and core losses of 2% = 558W.

Va rating for PT = 600VA or higher.

The 8585 toroidal power transformer was originally 800VA rated. I was originally made by Harbuch in Sydney but it hummed badly with 240Vac at primary without a load so I estimated the turns per volt were too low and Bac was far too high.

I removed the Secs, and added 33% more primary turns of same sized wire for Bac $< 0.9\text{T}$.

Then I added a sec winding for 180Vac HT winding for B+ doubler rectifier, and added heater windings. The noise was much reduced to just low enough when mounted in a sheet steel box between the two OPTs also in steel boxes.

The Primary winding resistance increased 33% but was still sufficiently low.

Altering this toroidal PT used up 2 days using a small shuttle of about 1 turn in length, made from a wooden dowel 22mm dia, with cut outs on each end on which to pre-wind the wire used for new turns.

I found that all toroidal PT purchased at Jaycar or anywhere else were too noisy to use in any amp I built, so nearly all amps I made after 1996 had E+I transformers which all ran silently.

I found cheap NOSS E+I was OK but the Bac should never exceed 0.8Tesla, and then they ran silently without getting hot from core losses. Core stack height for NOSS must be 50% higher than the same PT using GOSS E+I lams where Bac could be 1.2T.

The 8585 has a voltage doubler B+ supply because the HT winding for a doubler rectifier needs 1/2 the turns of the winding needed for a bridge, and 1/4 of the turns needed for a HT winding with CT.

The doubler is in fact two half wave rectifiers in series, so the 180Vrms charges C16 with positive going waves and C17 with negative going waves.

The resulting Vripple is 100Hz, and no larger than use of a bridge for same dc power.

Si diodes are 6A rated x 1,000PIV rated.

The efficiency of the doubler with Si diodes is very good. The ratio of $V_{dc} : V_{ac} =$ about 2.65 for working circuits with doublers, so HT Secondary $V_{rms} = V_{dc} / 2.65 = 480V / 2.65 = 181V_{rms}$.

The DC RL is lowest for maximum AB $P_o = V_{dc} B+ / I_{dc} \max = 480V_{dc} / 0.832A = 577r$. Most of the time the I_{dc} to KT90 anodes is low so RL_{dc} at idle $= 480V / 0.352A_{dc} = 1,364r$.

I used a CLC filter to reduce Vripple at top of C18+C19 to very low level. The choke is large, with $R_w < 30r$, so V_{dc} drop across choke at idle $< 11V_{dc}$.

There is no active regulation to keep V_{dc} constant at C18, and it is not needed. The slightly continuous change of mains levels creates a constantly changing V_{dc} level which creates very low frequency noise and C18 with spectrum between 0.0Hz and 10Hz, with average amplitude of +/- 50mVpk when most other people connected to the mains are busiest in their homes.

This VLF occurs in all amplifiers without active regulators and it causes ZERO audible artefacts.

The PP output stages of tube amps have naturally good common mode rejection of B+ rail noise which appears at their OPT CT.

The noise appears and each end of OPT primary, and little appears across the OPT primary, so virtually none is transformed to appear at the secondary.

Calculation of C16+C17. I have 2 x 470uF in series for 235uF. $X_c = 6r8$, and the minimum DC load $= 577r$. Ratio of Load : $X_c = 577r / 6r8 = 85 = OK$ at highest I_{dc} .

So V_r at C16 $= 0.832dc \times 2,200 / 235uF = 7.8V_{rms}$ max.

100Hz i_{ac} in 235uF $= V_{rms} / X_c = 7.8V / 6r8 = 1.15A_{rms}$.

Chosen C16+C17 have ripple current rating of several amps.

The maximum dc power at C16 $= 480V \times 0.832A = 400W$.

The power from HT secondary $= 400W + 2\% R_w \text{ loss} = 408W$, and with HT 180Vac, $i_{ac} = 408W / 180V = 2.27A_{rms}$. Each 50Hz 1/2 wave is 10mS.

If the charge time is 2.5mS, average charge $i_{ac} = 2.27A_{rms} \times 10mS / 2.5mS = 9.08A$ and peak i_{ac} for charging C $= 9.08 / 0.63 = 14.4A_{pk}$.

I found the 2 diodes with 6A rating and 1,000Vpiv were fine, because $180V \times 6A$ gives 1,080W.

The peak rating for Si diodes is much higher than the steady state condition.

The temperature rise for the Si diodes is less than +30C so you can hold a finger on the plastic body and not get a burn.

But peak charge currents in HT winding are highest in the second after turn on where the V_{dc} in C16+C17 has to rise from 0V to +480V in a few wave cycles.

In Fig 2 I show R41 100r 20W in series with with HT winding. At turn on from cold, the 100r limits inrush currents to more than 2.5A_{pk} and after a second or two B+ will reach 70% of max and after 4 seconds, R41 is shunted by Relay 1, and peak charge currents are not much higher than 3A_{pk} and B+ then reaches max unload value of +508V_{dc} with reducing charge currents. The tube heaters have 1/2 their hot resistance when cold so at turn on the mains winding has high inrush current to warm the cathodes but peak I_{ac} is not as high as the charge I_{ac} to C.

Tube cathodes begin emitting after about 20 seconds and reach nearly full emission in 60 seconds.

If the amp is turned off, and on again after say 2 seconds and all cathodes remain hot, the delay circuit always works to reduce input charge current to C16,17,18,19, 470uF. With limited inrush current, mains fuse can be 3A slow blow, a lot less than 6A slow blow without limiting. The 3A fuse means input power can be 3A x 240Vac = 720VA, and fuse would blow at about 850VA.

The mains fuse would only ever blow if the HT sec has a short circuit, if two of the series electro caps become a short, or if the OPT primary shorts to a secondary winding. There are 8A fuse links soldered in to each 6.3Vac phase of two x 12.6Vac heater windings for 8 x KT90 and 4 x EL84, so that a short in heater circuit will blow a fuse. There are 2 x 3A fuses on each 12.6Vac phase of two other 12.6Vac heater winding to make 12.6V_{dc} x 0.6A_{dc} to 4 x 12AU7 preamp and input tubes.

The 50Vac bias winding has 1A fuse.

All these fuses will prevent having the "minor Sec" windings fuse open or overheat.

But in some amps I have used a permanent series R between HT winding and C, with typical R value = 4 x X_c at 100Hz. So for a bridge of diodes charging 235uF, and with low winding resistance of power transformer, using 27r x 10W resistance in series with HT winding will much reduce peak charge currents without causing a large reduction of B+. I have no such permanent R in 8585 but if there was one, it would be say 15r x 10W between terminal B of HT winding and R41.

The effect of the added series R is to make the charge time to caps much longer, perhaps 4mS for each 1/2 50Hz wave cycle lasting 10mS.

The 100Hz Vripple will become more like a triangular wave, less like a sawtooth wave and average charge current will be slightly more than twice the I_{dc} to B+.

In a class A amp, the slight reduction of B+ with the added series R does not matter because while the amp is in class A, there is no change to I_{dc} and no change to V_{dc}.

Some people are fanatics about capacitors. They say all PSU caps should be polypropylene with high V_{dc} ratings. I cannot share the zeal of fanatic extremists because nobody I met during 18 years hand crafting amps for extremists, not one could ever identify an amp which did not have polypropylene filter caps and / or coupling caps. But I always used the brand of caps they asked for. They paid the higher price.

I have only ever used low value polypropylene well rated "motor start capacitors" in a power supply for a pair of 60W class A SE amps. The 1kW rated transformer I wanted to use had a HT winding with CT, 420V-0-420V, and would give +560Vdc at the 700mA required for the two 60W class A channels. But I only wanted +470Vdc for the cathode biased 6550 and did not want to have a hot running series resistance to lower the B+ by 90Vdc which meant resistor heat = 63W.

So I used series 6Amp x 1,000V rated Si diodes to charge a pair of series 60uF x 450V rated polypropylene motor start caps each about 52mm dia x 100mm long. Effective input C = 30uF to CLC filter. I used 22k across each C to equalize Vdc.

With $I_{dc} = 0.7A$, 100Hz ripple = 53Vrms. The 30uF was followed by a large 4H choke with $R_w = 20r$ which dissipated 10W. I then used 6 x 470uF x 350V rated caps in series / parallel for total of 705uF which gave V_{ripple} of 50mV, quite OK for the anode supply with CFB arrangement of 12 x 6550 in the two channels. I then had additional RC filtering to the screen supply and input stages.

If ever the I_{dc} was low at say 0.5Adc, the B+ would rise, and if I_{dc} was high at say 1Adc the B+ would go low, and all 12 x 6550 had cathode biasing and shunt regulated E_{g2} , so the tubes would survive the change of I_{dc} and B+ for any reason.

For all power supplies, you must think about **THE WAY SHIT CAN HAPPEN**, and install the means to minimise the smoke production and the cost of following repairs.

With input RCA sockets shorted to 0V, the 60W SE amps had noise at the outputs < 0.25mV.

Although ripple voltage across the C1 30uF capacitor was high, there is no dissipation in the reactive elements of C or following L, and I got the V drop I wanted without wasting heat in a resistance. Pure class A amps don't need regulated power supplies and their B+ voltage can be allowed to drop if there is a fault and without causing damage.

The 420V HT could have been used to make a choke input filter with just LC, ie, without the 30uF. The theoretical **Vdc at output of LC = 0.88 x Vrms of Sec winding**. But this assumes the choke and HT winding has no resistance, and Vdc is less than theory suggests. But LC filters must have a bleeder resistance so that without the load to tubes, the bleeder resistance provides a load of 1/10 of maximum normal load and then the R_w losses of choke and HT winding is minimised.

The minimum L for choke = $R_L \text{ dc at minimum } I_{dc} / 900$ for 50Hz mains.

Thus if you expect perfect condition $V_{dc} = 0.88 \times 420V_{rms} = 369V_{dc}$, and you have bleeder $I_{dc} = 70mAdc$, $R_L \text{ dc} = 369V_{dc} / 0.07Adc = 5,271r$, and $L = 5,271 / 900 = 5.86H$. In the real world anything over 6H will do but if its $R_w = 25r$, then with 0.77Adc the Vdc drop is 19Vdc so you get 350Vdc, and the 3% R_w of PT will reduce this to 340Vdc and if you want cathode biasing with E_k at = +25Vdc, the E_a is +315Vdc and maybe there is - 10V drop on OPT windings and E_a is down to +305Vdc, and for the 60W amps I made this did not suit the OPT primary load.

So LC input is a good idea but you MUST have the right Vac to begin with. But a 6H

choke for 800mA_{dc} is a real monster, maybe as big as the large heavy OPTs I used.

I wanted $E_a = +435V_{dc}$, and an additional 35V for cathode biasing.

Thus any amp with CLC which has B+ that is too high can have C1 cap value reduced so the Vripple is high, peak charge currents are low, and B+ can be varied by simply varying the C value of C1. C2 can be as large as you like. The L must be able to withstand V_{ac} without its core saturating with the high V_{ac} ripple.

Rules for CRC filters.

Wherever you have a CRC or CRCRC input filter for B+, the total R should not exceed $0.05 \times RL_{dc}$.

Suppose your amp requires $+400V_{dc} \times 0.16A_{dc}$ at OPT for 2 x KT88 with input tubes.

$RL_{dc} = 400V / 0.16A = 2,500r$ so total R should be $0.05 \times 2,500r = 125r$ max.

The DC power to $2,500r = 400V \times 0.16A = 64W$, and heat in $125r = 3.2W$.

If CRC is used, and $C1 = 470\mu F$, then V_r at $C1 = 0.16A_{dc} \times 2,200 / 470\mu F = 0.75V_{rms}$.

If the wanted C at OPT to $0V = 470\mu F$, attenuation factor = XC at $100Hz / R = 3.4r / 125r = 0.272$ and the V_r at $C2 = 0.0272 \times 0.75V_{rms} = 0.02V_{rms}$, not a bad result.

V_{dc} drop across $125r = 20V_{dc}$ so V_{dc} at $C1 = +420V_{dc}$.

The V_r attenuation factor = $0.02V_{rms} / 0.75V_{rms} = 0.027$, or $1 / 37.5$.

The minimum attenuation factor for R+C section = 0.1.

2 x R+C sections would give factor = 0.01.

Now if you had CRCRC with 3 x $470\mu F$, the R for both RC sections may be $10 \times XC = 33r$, and total $R = 2 \times 33r = 66r$ and v_r at $C3 = 0.75v_{rms} / 100 = 0.0075V_{rms}$ which is probably as good as anyone needs, and there is no problem with resonance with L + C below 20Hz. The choke need only be 0.54H but its F_o with $470\mu F = 10Hz$, and this is a bit high, so for 5Hz the L must be 2.2H for $F_o = 5Hz$.

Such a choke could have $R_w 40r$ and for the expense of the choke there is not a huge benefit, especially for a PP amp with CMRR. But for SE amp, the choke is best for very low $V_r = 0.002V_{rms}$ at OPT connection.

But consider CRCRC for 12 x 6550 for SE class A needing total B+

$= 470V_{dc} \times 800mA_{dc}$. $RL_{dc} = 589r$. Total R should be $0.05 \times 589r = 30r$.

Heat in R = 19.2W. For two RC sections the R = $15r$ for each and XC should be

$15r / 10 = 1.5r$, and required $C3$ at OPT to $0V = 159,000 / (1.5r \times 100Hz) = 1,060\mu F$.

You would use 10 x $470\mu F$ in series parallel for $1,175\mu F$, and for CRCRC you need

30 x $470\mu F \times 350V$ rated. V_r at $C1 = 1.5V_{rms}$ and at $C2 V_r = 0.15V_{rms}$, and at $C3$

$V_r = 0.015V_{rms}$. V_{dc} drop across $30r = 24V_{dc}$. Total attenuation factor = 0.01.

Now if you don't want so many C, you can use higher R value but then the heat in R increases.

This is where choke begins to make sense and for CLC you may have $C2$ at OPT to

$0V = 470\mu F$ with 4 x $470\mu F$. If $C1 = 470\mu F$, $V_r = 3.75V_{rms}$, and if V_r at $C2 = 0.015V_{rms}$,

the attenuation factor = $0.015V / 3.75V = 0.004$, so $X_L = X_c / \text{atten factor} = 3.4r / 0.004$

= 850r and L might be $850r / (6.28 \times 100\text{Hz}) = 1.35\text{H}$ with $F_o = 6.3\text{Hz}$, probably OK, and experience tells me it is not too hard to make a 4Kg choke for 0.8Adc, $L = 2\text{H}$, and $R_w = 20r$.

30 x 470uF at \$15.00 each costs \$450. 8 x 470uF cost \$120, and a choke might cost \$200, so CLC is cheaper than CRCRC.

For a preamp where I_{dc} may never be more than say 60mAdc for 2 channels, then CRCRC should be fine with 470uF and 100r so that 100Hz V_r at $C_1 = 0.28V_{rms}$ is reduced to 0.00032Vrms at C_3 . The heat in $2 \times 100r = 0.72\text{W}$, and quite acceptable, with V_{dc} drop = 12Vdc, also OK.

For 8585 PSU, Choke $L_1 = 2\text{H}$. I wound L_1 with E&I T 25mm x S 40mm and filled the bobbin with 0.55mm Cu dia wire. With correct air gap material I got 2H at 0.6Adc.

X_L at 100Hz = $6.28 \times L \times F = 6.28 \times 2\text{H} \times 100\text{Hz} = 1,256r$. X_C for 235uF at 100Hz = 6r8. Attenuation factor = $6r8 / 1,256r = 0.0054$, (or about -46dB).

At idle, with $I_{dc} = 320\text{mAdc}$, V_r at $C_1 = 3.0V_{rms}$, and at OPT primary CT, $V_r = 0.016V_{rms}$ = low enough!

The F_o between L_1 2H and following 235uF = $5,035 / \text{sq.rt} (2,000\text{mH} \times 235\text{uF}) = 7.4\text{Hz}$, a little high, but I found no strange behaviour occurred.

The amp DC Load = $480\text{Vdc} / 0.32\text{A} = 1,500r$, and this is not low enough to damp F_o resonance for 2H + 235uF.

However, the 8 x 6550 or KT90 are all in parallel with each having R_a at dc = 35k, so with 8 tubes, dynamic resistance = 4k4 approx. The high R_a is maintained by having screen V_{dc} shunt regulated so V_{dc} between screens and cathodes will not vary.

Triode connection of 6550 or KT90 will give each $R_a = 1k1$, so 8 tubes give 138r, and this will damp the LF resonance because wanted damping R should be $1.4 \times X_L$ or X_C at F_o . X_C 235uF at 7.4Hz = 92r, and 137r is close enough to keep the LC filter response flat without a peak at 7.4Hz.

But because the CFB connection with regulated E_{g2} is used, R_a is high, but there is very little change of I_a if the $B+$ wobbles up and down below 10Hz. There is no change to operating gm, and the $B+$ wobble is rejected by common rejection, so the LF F_o resonance of less than 100mVrms at around 7.4Hz just does not matter.

For SE amplifiers, low V_r at $B+$ connection at primary is essential because there is no common mode rejection. But where output tubes have CFB with fixed E_{g2} , effective R_a at very low F is quite high, and usually much higher than the OPT primary load.

For ONE EL34 in pentode mode, its R_a at dc = 20k, but its anode load = 5k0, so if V_r at $B+$ = 20mVrms, it is divided over 25k, and the V_r across load = 4mVrms.

If the OPT ZR = 5k0 : 5r0, then TR = 31.6 : 1, so V_r at sec = $4\text{mV} / 31.6 = 0.126\text{mV}$.

But the CFB and GNFB will reduce this by about 1/10 or -20dB to be 0.0126mV, well

below the other noise made by the amp.

Screen Vdc in 8585 and some of my other amps has been shunt regulated by having Idc to all screens fed through resistance to the B+. See R49 3k6 in Fig2 above. as the screen Idc input increases with output power, the Eg2 Vdc tends to reduce and cause the tubes to become under biased with less Idc at the zero crossing point so THD becomes worse. But some slight reduction of Eg2 is allowable and as Ig2 increases a shunt regulator reduces its Idc, so the Eg2 does decrease until sustained high level Po is maintained.

See Fig 2 above, with two series Darlington pairs with MJE340 + BU208P.

If one or more 6550 or KT90 malfunction and Iadc goes high, then Ig2 may go high, and if high enough, the Vdc across the feed resistance R49 3k6 can increase, and the regulated Eg2 will be allowed to reduce, tending to turn off all tubes. The shunt regulation shown works well when music signals are taken up to clipping levels, but without regulation, Eg2 will reduce so much it causes high THD.

The shunt regulator is better than the series type regulator for screens because the series regulator does not allow the Eg2 to fall so easily if there is a faulty tube where Idc to its screen may increase from normal 3mAdc to 23mAdc, and the tube overheats and can cause trouble.

DC heater supplies for 8585 to 4 x 12AU7 give 12.6Vdc at 0.6A. There is no need for CLC, and I used CRC which worked fine.

There are more power supply schematics of working amplifiers with PSU at my listed web pages :-

300W mono blocs,

100W mono blocs,

5050 integrated,

SEUL 32W, 2012 version,

SE35W,

Quad II power amp mods,

Leak amp mods,

Dynaco ST70 mods,






10-tube preamp.

Chokes for CLC, LC are covered at my page [powertranschokes.html](#)

For a bench top PSU for testing tube circuits see [power-supply-for-tube-tests.html](#)

Fig 3. SHEET 3 Remote PSU on separate chassis for 300W monobloc.

Crest Factor for various waves. www.turneraudio.com.au

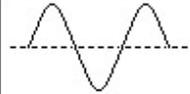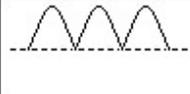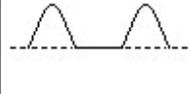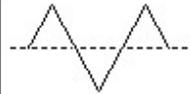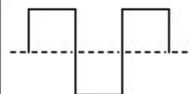Wave type	Wave form	Mean magnitude (rectified)	Wave form Factor	RMS value	Crest Factor	Crest Factor
DC		1.00		1.00	1.00	0.0dB
Sine wave		$\frac{2}{\pi} \approx 0.6363$	$\frac{\pi}{2\sqrt{2}} \approx 1.1112$	$\frac{1}{\sqrt{2}} \approx 0.7071$	$\sqrt{2} \approx 1.4142$	3.01dB
Full-wave rectified sine wave		$\frac{2}{\pi} \approx 0.6363$	$\frac{\pi}{2\sqrt{2}} \approx 1.1112$	$\frac{1}{\sqrt{2}} \approx 0.7071$	$\sqrt{2} \approx 1.4142$	3.01dB
Half-wave rectified sine wave		$\frac{1}{\pi} \approx 0.3182$	$\frac{\pi}{2} \approx 1.5714$	$\frac{1}{2} = 0.50$	2.000	6.02dB
Triangle wave		$\frac{1.00}{2} = 0.50$	$\frac{2}{\sqrt{3}} \approx 1.1547$	$\frac{1}{\sqrt{3}} \approx 0.5773$	$\sqrt{3} \approx 1.7320$	4.77dB
Square wave		1.00	1.00	1.00	1.00	0.0dB

π = greek letter pi, = $22 / 7 = 3.142857134.....$ and is a mysterious and significant mathematical figure used in countless equations. \approx = symbol for "approximately equal to".

[Back to Index Page](#)