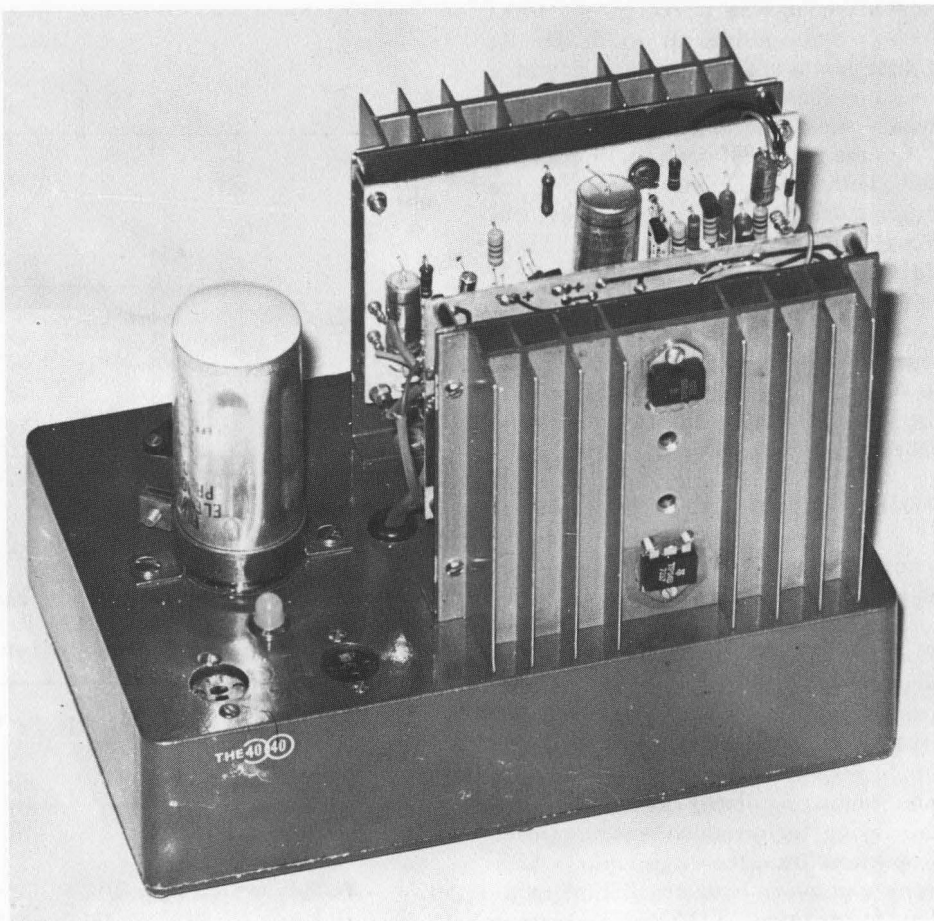


IF I MIGHT SUGGEST a further comparison to your readers, the Twin Twenty schematic shows the age of the amplifier. While this type of amplifier was considered quite good in 1969 when it was designed, it can hardly be considered State-of-the-Art any longer."

So opined a critic of one of my creations back in 1970. My goodness, was it really that long ago? I must confess to a twinge of surprise that this, my very first design published in the newly-hatched *Audio Amateur* (TAA 1/70, p.4), is now a decade old. At the time, I never did regard it as State-of-the-Art (whatever that may mean) since by 1969 most of the serious problems surrounding the design of transistor audio amplifiers had been identified and were well on the way to being solved. The principal factors usually preoccupying the circuit designer were those of the cost and compromise in meeting the design specification; and so it was for me in the case of the 20/20. No revolutionary ideas, no innovations; in short, it followed concepts firmly proved by others before me.

It worked well and presented no problems for the competent home constructor, the latter prerequisite imposing certain constraints frequently overlooked by some of my contemporaries specializing in "do-it-yourself" projects. Despite the gentle brick thrown at it by one of my readers, of all the projects I have ever prepared for the home constructor this one still brings in the most letters of comment and query. The kit of parts is still available—yet to the best of my knowledge Old Colony have never declared a policy of going into the antique business! So clearly it met then and continues to meet the needs of many of TAA's readers.

This is not to ignore the fact that it is 10 years old and in the context of today's standards it does fall short in certain areas. In power, at a 20 watt rating per channel and with speaker efficiencies steadily drifting downwards, its muscles are a bit puny. This factor persuaded me to take a further critical look at the design, especially after my good friend Alan Watling announced his intention of going "four channel" with the 20/20 at the heart of the system. And, of course, it was Alan who in his article last year ("Pandora's Box," TAA, 1/78, p. 4) revealed the existence of the updated 20/20 in his elegant four-channel set-up. The inevitable letters followed; so, with a little arm twisting from our Editor, here it is for you to consider as your next constructional project.



*The author's prototype 40/40 amplifier.*

# The Williamson 40/40 Power Amplifier

by REG WILLIAMSON  
Contributing Editor

As before, Old Colony will probably offer a kit of parts soon after this article appears. My design philosophy has remained unchanged. Components should always be reasonably accessible to the constructor, avoiding any exotica. The project should need no fiddly setting up. Above all, the builder should have some leeway in component selection: in my experience home builders always write to ask if so-and-so's make of transistor can be used instead of that suggested by the designer. In this respect, the new version is even more indulgent than the old one.

Since owners of the '69 version may wish to update, some of the original

parts may be used again—but not, I regret, the etched board; that must be replaced. [See Figs. 3 and 4.]

## IS IT BETTER?

Now you'll be asking, is the performance improved? To be honest, I suspect the improvement is less audible than measurable. The inherent distortions introduced by the amplifier were already much lower than those contributed by the rest of the transmission chain, particularly in the program source, anyway. For example, the THD is nearly all low order, predominantly second harmonic (the "nice" sort);

measured, it was never greater than 0.05% from 40Hz up to 8kHz. At 15kHz it was still less than 0.1% with a resistive load and much less with a typical speaker system.

On the matter of power rating, here I can claim some enhancement over the original design, which, incidentally, was for a nominal 16 ohm loading. These days the norm is more likely to be 8 ohms. So taking advantage of a wider range of semiconductors, plus some changes in the power supply, I am ready to accept Alan Watling's suggestion that the updated design may legitimately be called the 40/40. So be it.

## PHILOSOPHY MATTERS

Before discussing the design changes in detail, let me—as the Irish say—trail my coat a little by airing a few personal observations. As a practicing design engineer with over 30 years experience, I think far too much is being made today of newly discovered aberrations in audio amplifiers, which seem to appear with monotonous regularity. If nothing else, I'm trying to introduce some sense of proportion into the arguments which seem to go on *ad infinitum*. Let me mention, for example, TIM and SID about which a great deal of smoke is currently being generated in respected quarters.

In the first place, there has never been any great difficulty in producing test signals that audio amplifiers will mangle to death or malform in some way. Consistently overlooked is their relevance to *real* program material and the parameters required in the program chain for this material to be transmitted without significant deterioration. In connection with this contentious subject alone, I commend to TAA readers one of the important series of articles on the whole subject of audio amplifier distortion written for *Wireless World* by my friend Peter Baxandall. The one I have in mind appeared in the January, 1978 issue.

I know of no more down-to-earth, realistic engineer than Peter. In this superb essay, he carefully dissects most of the pro-SID/TID arguments; subjects them to critical analysis with complementary tests; and reaches some startling conclusions undermining many cherished beliefs concerning amplifier performance criteria that are being carefully nurtured in certain quarters.

Yet Peter Baxandall is no wilful iconoclast; his arguments are almost unchallengeable. Let me mention one conclusion he reached: a power amplifier

FIG. 2

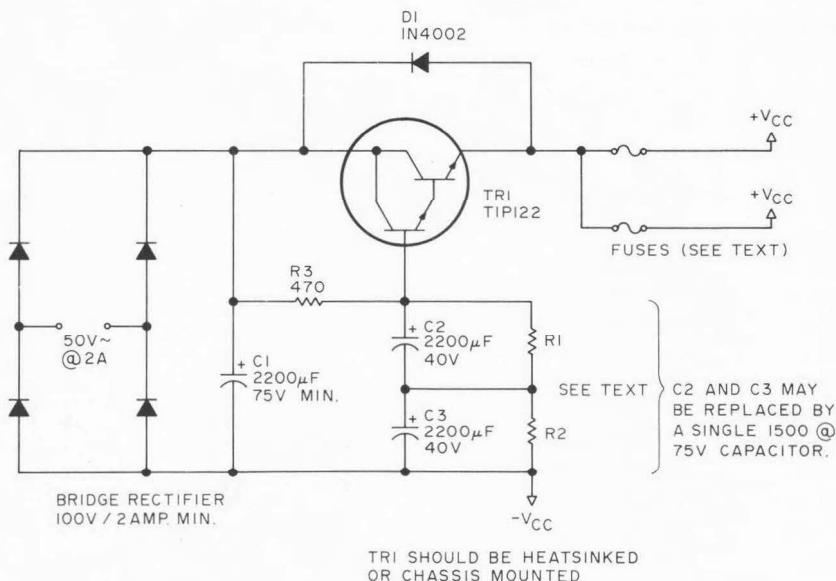


Fig. 2. The power supply schematic. The Darlington semiconductor acts as a capacitance multiplier. The two resistors equalizing the two output capacitors should be between 470k and 1Meg, but reasonably well matched, at least to  $\pm 5\%$ .

## PARTS LIST: POWER SUPPLY

TR <sub>1</sub>	Texas TIP 122	C <sub>2 3</sub>	2200µF not less than 40V.
D <sub>1</sub>	1N4002	R <sub>3</sub>	470Ω
R <sub>1 2</sub>	1MΩ	FWB	Bridge rectifier, (silicon) 200piv, 2A or better
C <sub>1</sub>	2200µF, not less than 70V	T <sub>1</sub>	Transformer, 118/50V, not less than 100V RRM @2A.

capable of full power output on sine waves up to 2.2kHz, without suffering from slew rate distortion and with sufficient freedom from ordinary non-linear distortion, will subjectively be perfectly satisfactory. No, that is not a misprint—I did say 2.2kHz. Surprised? I need hardly add that even a 10-year-old design such as the 20/20 would have no difficulty meeting that sort of requirement.

This is not to deny, of course, that any design engineer should always take measures to avoid feeding into the system program material that the individual elements are incapable of handling without degradation; and in the system itself, any economically possible improvements should be introduced, even though they may seem of academic value. In the case of the new 40/40, I have included those I have felt worthwhile.

## POWER SUPPLY ISSUES

So to the circuit itself. I'd like to begin with the power arrangements. Yes, I'm well aware that these days it is customary to power with balanced feeds and the technique certainly has virtues.

The major one is economic: it does save a few parts and is inherently superior on the point of regularity. Other claims for it are suspect. For example, consider the suggestion that low frequency performance is improved because of so-called "direct coupling." I have yet to meet a hifi enthusiast who can convince me this method of power supply provides true direct coupling. One has only to trace out the signal path at any point in any audio amplifier to end up going through a capacitive element.

The technique has one major potential disadvantage: I speak with some feeling after seeing the divider network in an expensive speaker disappear in smoke after an output transistor failed in a "direct coupled" amplifier. Protection measures are mandatory and fusing alone is hardly adequate. The dc "sit" point at the speaker terminals must also be very low, since only a few millivolts offset across a low Z speaker will cause a significant current to flow through the system with possible performance degradation. So I still feel a single ended and possibly regulated power supply is preferable if the user wishes; the one still on offer from Old Colony for the old 20/20 is suitable. [See Jim Boak's regulated

**FIG. 1**

-3dB @ 83.6kHz BUT GREATER THAN  
10kHz SOURCE 19.5kHz @ -3dB

ALL DIODES = IN4002  
NOTE:  
2K2 = 2.2KΩ  
2R2 = 2.2Ω  
OR5 = 0.5Ω

### PARTS LIST: AMPLIFIER ONE CHANNEL

R <sub>1</sub>	2k2†	R <sub>13</sub>	2R2†
R <sub>2</sub>	820k	R <sub>14</sub>	6k8
R <sub>3</sub>	820k ±5% or better	R <sub>15</sub>	6k8
R <sub>4</sub>	10k ±5% or better	R <sub>16</sub>	1k
R <sub>5</sub>	3k9 ±5% or better	R <sub>17</sub>	1k
R <sub>6</sub>	5k6 ±5% or better	R <sub>18</sub>	270
R <sub>7</sub>	27Ω	R <sub>19</sub>	270
R <sub>8</sub>	470Ω 1 watt	R <sub>20,21</sub>	0R5† w/w 2 watt
R <sub>9</sub>	680Ω	R <sub>22</sub>	10Ω
R <sub>10</sub>	680Ω	R <sub>23,24</sub>	56Ω
R <sub>11</sub>	100Ω	VR <sub>1</sub>	50Ω preset, cermet or lg. carbon
R <sub>12</sub>	120Ω		

C <sub>1</sub>	1μF tantalum, not less than 40V	C <sub>7</sub>	680pF polystyrene
C <sub>2</sub>	680pF polystyrene	C <sub>8</sub>	33μF elec. not less than 6V rating
C <sub>3</sub>	100μF elec. not less than 50V	C <sub>9</sub>	33μF elec. not less than 6V rating
C <sub>4</sub>	10μF elec. not less than 15V	C <sub>10</sub>	0.1 polyester not less than 40V
C <sub>5</sub>	500μF elec. not less than 40V	C <sub>11</sub>	2200μF elec. not less than 40V
C <sub>6</sub>	2700pF polystyrene		

D1-9	1N4002	TR <sub>5</sub>	BFR79 (As for TR <sub>2</sub> )
TR <sub>1</sub>	BC477 (MPS8598, 2N2907A)	TR <sub>6</sub>	BC182
TR <sub>2</sub>	BFR79 (MPS U06, BFX40)	TR <sub>7</sub>	BC212
TR <sub>3</sub>	BFR39 (MPS U56)	TR <sub>8</sub>	2SD426 Toshiba (2N5632, 2N6059, BD546C*)
TR <sub>4</sub>	BFR39 (MPS U06, BFX40)	TR <sub>9</sub>	2SB556 Toshiba (2N6229, 2N6052, BD5445C*)

THE AUDIO AMATEUR 4/1979 7



materially affected. It requires, simply, introducing an unusual circuit configuration into the power line. The time constant of the power filter is now, near enough, the product of the R and C in the filter, which works out in my design to about 0.5 second. The capacitor need not be a high ripple type; in fact, because of size considerations, I used two in series (with high value resistors across to equalize the polarizing potential). To permit enough current at maximum power levels to pass through the Darlington power transistor, the R element should be no larger, but the C element may be bigger if you wish. I use one filter element for a stereo pair but, again, you may use one per amplifier which improves regulation.

The first virtue of this technique, apart from cost saving, is ripple will now not exist on peaks of high power. The second is the power supply eases on gently, which is a good thing in many ways, notwithstanding avoiding the nasty plops one gets as the various capacitive elements in the amplifiers charge up. The peak power rating is also improved and moves closer to the ideal one normally achieves with a more costly regulated supply.

Readers may be a little puzzled on seeing the photograph (Fig. 5) and may speculate where the power transformer has gone. Here's an end to the mystery: it's in the base, mounted in the case with the remainder of the power section. I permitted myself the indulgent luxury of using a toroidal type. It isn't essential, of course, and at the time of writing I'm not at all sure whether they are easily obtainable in the USA from normal parts sources. I'm sure with their characteristic ingenuity Old Colony will locate some if at all possible—but don't regard a toroid as a *sine qua non*.

## AMPLIFIER CIRCUITRY

Now let's have a look at the amplifier, beginning with the input section. No great changes here: a single p-n-p transistor, moderately high  $h_{fe}$  and with a  $V_{ceo}$  not less than 60V operating in the common emitter mode. Base bias is via a star configuration whose junction is bootstrapped into the main feedback loop to eliminate the shunting effect of the bias network across the signal path. The bias potential also determines the basic "sit point" at the output stage and is  $\frac{1}{2} V_{cc}$ . Needless to say, the resistors in this network should be of close tolerance and not worse than 5%.

If you have the old 20/20 schematic to

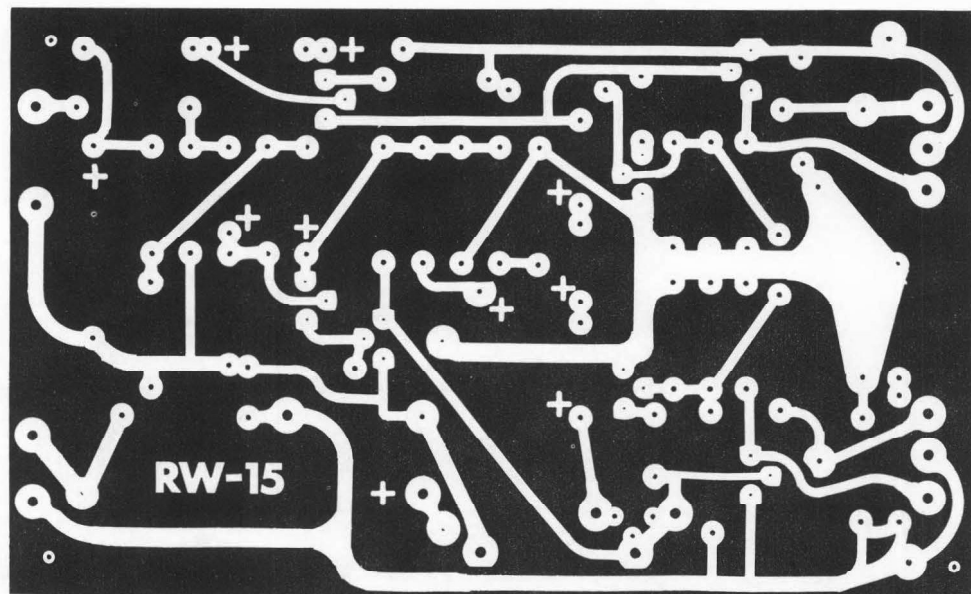


Fig. 4. Negative pattern, full size of the 40/40 amplifier circuit board.

hand, you'll notice too we are sneaking a bit of the voltage drop across this network via two diodes in the  $+V_{cc}$  line. More on that later. One extra addition, a simple first order low pass filter at the input, inhibits supersonic components in the program from getting into the amplifier. The turnover point is a function of the source  $Z$ , so it should not be greater than 5k $\Omega$ .

Most of the voltage gain takes place in TR<sub>3</sub>, an n-p-n transistor. It should again be of moderately high  $h_{fe}$ , with a  $V_{ceo}$  not less than 80V and preferably higher. Plenty of suitable devices exist and the  $P_{diss}$  should always be not less than 750mW. This stage also operates in the common emitter mode, but we have a fundamental change compared with the old 20/20 design in the use of a static constant current load. For minimum non-linearity in the transfer characteristic for the output stage, drive it from a constant current source. I achieved this in the original 20/20 by a dynamic bootstrapping circuit from the output to the resistive load of the predriver stage. On reflection, the alternative I'm now proposing is much better since it carries with it other advantages such as less critical bias setting. (An early criticism of my original choice was quite correct and I failed to appreciate it at the time.)

The constant current load is a p-n-p transistor of moderate  $h_{fe}$ , a  $V_{ceo}$  not less than 80V, and  $P_{diss}$  not less than 750mW (actually, the recommended complement to the predriver device will do nicely). The base bias for this transistor is from the constant voltage across the two diodes I referred to earlier in the

$+V_{cc}$  line; so since the base requires 0.6V to turn the transistor "on" and we have 1.2V, then the transistor will require 0.6V at the emitter before current limiting begins. In this case the current will be held constant at  $\frac{0.6}{120}$  where 120 $\Omega$

is the value of the emitter resistor. So simple arithmetic yields a current of 5mA. Agreed? Sorry if this has offended all the pundits who naturally knew this, didn't you? But I am surprised at the number of enthusiasts who fail to appreciate how this simple and often-used circuit technique works.

## OUTPUT DEVICES

Now to the output stage which is virtually unaltered except for the introduction of some protection circuitry. Leaving that for the moment, we still have two compound, complementary common collector pairs; and as before, the base/emitter inputs consist of four diodes in series which have to be biased "on." This forward bias is provided by the network of three diodes plus a small 50 $\Omega$  trimmer potentiometer as part of the pre-driver load. The setting of this p-meter which should be either the larger conventional sort or a cermet type, determines the quiescent current in the output stage which, as I said earlier, is not especially critical. [Note that two sets of holes are provided on the board for this trimmer: large for a vertical type, small for a cermet type.—Ed.] If you have a distortion factor meter available, then set bias just above the value at which the last vestiges of crossover distortion



FIG. 3

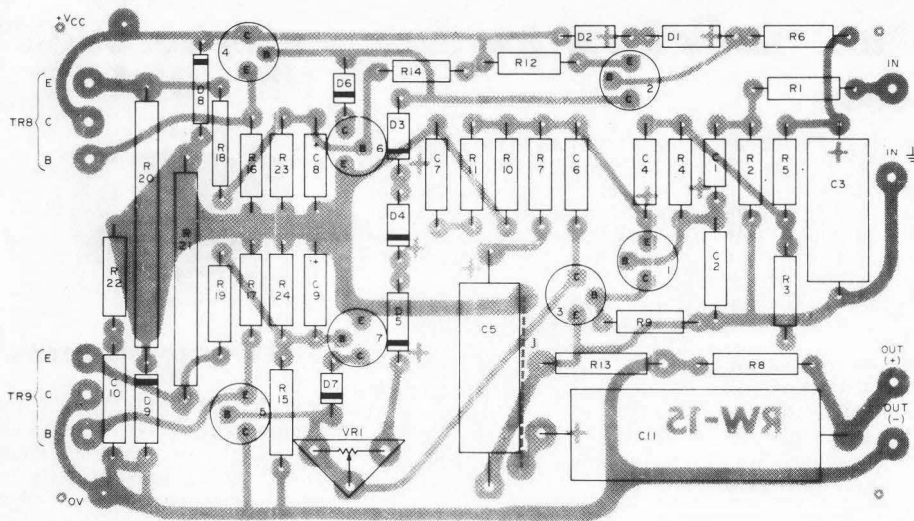


Fig. 3. Stuffing guide for the RW15 circuit board. Two sets of holes are supplied for VR1. The larger trio for an ordinary large preset. The smaller set are for a vertical cermet type. Do not use a small carbon preset here as it is likely to fail.

disappear, as viewed on an oscilloscope. This will normally be for a typical quiescent current (total for the whole amplifier—one channel) of about 50mA. I suggest, by the way, that this setting-up procedure, if preferred, be at a 1 watt level into  $7.5\Omega$ , at a frequency of 1kHz.

As for the protection circuitry I have added to the amplifiers, the particular type used must be designed with some care and will be no substitute for generously rated devices in the output stage. It must, in other words, be regarded as a lifejacket to be brought into use when all else fails! That which I have adopted is designed to protect the output devices and their compound drivers from excessive loading under overvolt as well as overcurrent conditions and, in restricted circumstances, from the simultaneous occurrence of both where the loading is highly reactive—as indeed, it is likely to be with real loads. D<sub>8</sub> and D<sub>9</sub> protect the output devices against the possibility, with reactive loads again, of the center rail voltage rising above or below that standing at the collector of each of the output transistors. (Yes, it can really happen.) Clamp transistors TR<sub>6</sub> and TR<sub>7</sub> limit the current drive to the output stage when biased on, and this condition will obtain when current at the sampling point—the output transistor emitters—exceeds a certain value, or when the voltage across the devices also exceeds a certain value. To allow again for the probably simultaneous occurrence of both under reactive loading conditions, I have added a short time constant to the

network providing the “bias on” potential for the clamping transistors. Other protection measures are orthodox, the inclusion of fuses in the power lines being one obvious measure. These should be of the “slo-blo” type.

### BUILDING TIPS

A few final words about construction technique. First, don't be stingy about heatsinks. Second, observe carefully the important matter of grounding. I've provided an independent output ground return on the board—use it and no other. The other ground and 0V rails of each channel should common together at two points only. One is at the  $-V_e$  terminal of C<sub>1</sub> in the power supply (and use heavy gauge conductor throughout for all power wiring including the one jumper on the circuit board which should be at least #20). The other point is at the inputs, where the common point may also be grounded to the chassis. Even so, you will observe we still have a ground loop between the two channels by virtue of this wiring technique, and unless we take certain precautions heavy currents could circulate through the small signal stages giving rise, possibly, to a significant increase in distortion at peak power levels. This, by way of answer to many silent questions, is the function of R<sub>13</sub>, the  $2.2\Omega$  resistor in the middle of the 0V line between the driver and output stages. This resistor should never get warm; and if it does, look for a wiring error somewhere.

As for using other than recommended transistors and diodes: as I intimated

earlier, this updated design is rather more tolerant than the original back in '69. Alan, for example, is happily getting away with MJ2955 and its n-p-n complement the ubiquitous 2N3055; but I have reason to think his custom-built speaker system presents a “kindly” load to the 40/40, and with four channels working he probably never runs anywhere near the rated output of the individual amplifiers. Back in '69 we didn't have a wide choice, and deliberately going for high-rated devices in the output stage meant also a sharp increase in cost for the home builder. This is not quite so bad now. With a wider range to choose from and with normal market forces as a consequence keeping the prices down, the home builder can afford to select high-rated devices; and with the odd load conditions presented by some speaker systems today this is a sensible move. The alternative list I have given is by no means exhaustive but merely represents those I have actually tried in the circuit.

### CORRUPTION LEVELS

Now for a few comments about performance. Those who look for a catalog of numbers before feeling confidence in the design will be sadly disappointed. If I say the amplifier is rated at 40 watts per channel into  $7.5\Omega$ , then at this level with a 550mV sinusoidal input signal of insignificant harmonic content over a frequency range from 50Hz to 10kHz, the output signal sampled across the resistive load will measure 17.4 volts and the harmonic corruption introduced by the amplifier will also be insignificant—for those who do like a number, certainly less than 0.1% THD and predominantly second order. In other words, distortion's a tiny fraction of that inherent in the program source or contributed by the rest of the program chain. No new square wave oscillograms, either. If our Editor still has those published for the original 20/20 (TAA, 1/70, p. 4), then these will suffice because there is no change.

I hope I needn't emphasize that this assessment of how the updated design performs is the worst possible. Real loads, for example, are not purely resistive and a speaker system with a nominal  $8\Omega$  loading is likely to deviate upward from this value. Unless you spend your time playing tapes of sustained organ chords, the actual power available on most program-type signals will be substantially higher than the

*Continued on page 22*

## AUDITORY PERCEPTION: PART I. THE SAGA OF GOLDEN- EAR AND METER-READER

*Continued from page 20*

such that failing to detect a difference when one exists (a Miss) and claiming to detect a difference when one does not exist (a False Alarm) are given exactly equal importance. In fact, they are merely two ways of saying precisely the same thing: what is the biased viewpoint of the observer? If False Alarms are frequent then Misses must be infrequent, and the relative frequency of the two errors depends exclusively on the personal reasons (bias) of the observer for perceiving, or reporting a perception of, a difference, or no difference.

**Air Freshener Midrange.** An observer can be trained to be unbiased (i.e., to produce equal proportions of False Alarms and Misses) but the procedure is long and very tedious; moreover, the effects tend to be highly specific to the exact conditions of training. Observer bias is a volatile phenomenon, being easily pushed one way or another by the conditions under which the observations are made, by momentary changes in the attitudes and beliefs of the observer as to what is "true," and by the payoffs that are provided for the various responses that one might make.

The Traditional Scientist, for example, operates on a payoff scheme that provides a strong penalty (loss of credibility) for claiming to perceive something that does not exist, whereas the Adept Believer suffers a similar loss of guru-ness for appearing insensitive to the wonderfully subtle phenomena in the universe. When the typical audiophile is experiencing one of those overwhelmingly passionate desires for a new set of purple capacitors in his power supply, he really wants to hear a difference and tends toward the golden-ear type of bias. But when his friendly audiophile-rival claims to have cleaned up his midrange by spraying the room with air-freshener, that same typical audiophile turns into the most strait-laced of meter-readers.

All perceptions are influenced by a host of subtle, and not-so-subtle, conditions, attitudes, and payoffs. And to make matters worse, the individual observer is usually not aware of the existence of many of these biasing factors, feeling instead a sense of certainty about the truth of his perceptions. It is this egocentric belief in one's own

perceptions that fires the belligerent stand-off between Golden ear and Meter reader, the former *believing* a difference to be real if he perceives a difference and the latter *believing* a lack of difference to be real if he perceives no difference.

**Choosing your side.** It should now be clear that it is not possible for the audiophile to really know when Julian Hirsch, for example, has failed to hear a difference that exists or when J. Gordon Holt has claimed to hear one that does not exist. Neither Julian nor J. Gordon know for sure; both are merely reporting their honest perceptions and are equally susceptible to observer bias. Whether you believe one or the other depends on the payoff to you personally (in terms of dollar costs vs. musical pleasures, for example) and on what *you* can hear (or think you can hear).

Similarly, you cannot know for sure the truth of your own claims as to what are and are not real differences, partly because you do not know the full nature of the conditions, attitudes, and payoffs that are biasing your observations. All you know for sure is that you *are* biased (one way or another), and that changing your bias (one way or another) will not produce truth but merely different proportions of False Alarms and Misses. The best you can do is to become more tuned-in to your own pattern of perceptual bias, and to speak and write with a humble sense of skepticism about your own perceptions.

As for our position, we lean toward the golden-ear type of bias because we believe it is advantageous to suffer more False Alarms (as long as we are reticent in our public claims) in order to Miss fewer potentially important facets of auditory perception. We believe the more daring approach of Golden-ear is amply justified because False Alarms in the audio hobby, while misleading and potentially expensive, create no real danger to humans, whereas the improvements in audio quality resulting from golden-ear design and critique are being perceived and appreciated by more and more audiophiles.

**An ear, is an ear, is an ear.** As an example of the latter, R. R. recently conducted a two-week workshop (three hours a day) entitled "Auditory Perception and High - Fidelity." Participants who could barely tell the difference between midrange and treble when the workshop began were mak-

ing judgments about three dimensionality, imaging, resolution of inner detail, graininess (slew-rate induced, we suppose), and a myriad of other golden-ear perceptual terms by the end of the workshop. While we don't claim that they "really" heard these auditory dimensions, they, at least, were personally convinced that they had heard what they heard.

We hope now that the Saga of Golden-ear and Meter-reader is ended. Neither is correct, and yet neither is wholly wrong. Each merely errs commensurate with his own built-in observer bias. And as for the audiophile trying to make a little sense of it all, he should listen to both points of view *and* listen to his own perceptions. After all, none of us can do anything but hear what we hear.

*Drs. Rees and Shaeffer teach at Western Washington University, Bellingham, Wa.*

### NOTES

1. Green, D.M. and Swets, J.A. *Signal detection theory and psychophysics*. New York: Wiley, 1966.

## THE WILLIAMSON 40/40 POWER AMPLIFIER

*Continued from page 9*

rated figure, and will certainly be far higher for both sustained and program-type signals if a regulated power supply is used.

Before ending, and anticipating the question that is bound to arise: am I proposing to also update the preamplifier? Frankly, I don't know—certainly some small improvements are possible. Let's just see how you get on with the new 40/40. □

### AUDIO AIDS: CONTINUED

*Continued from page 43*

$$R = \frac{(8)(12)}{1} = 96\Omega$$

By (3) the power rating is:

$$P_R = \frac{8^2}{96} = 0.67 \text{ watts,}$$

so you'll use a 100 ohm, 1 watt resistor. By (4) the maximum current is:

$$I_{max} = \frac{3}{100} = 30\text{Ma.}$$

For a negative supply, reverse the zener and do the same computations ignoring minus signs.

**DAVID CARLSTROM**  
Huntington Woods MI 48070