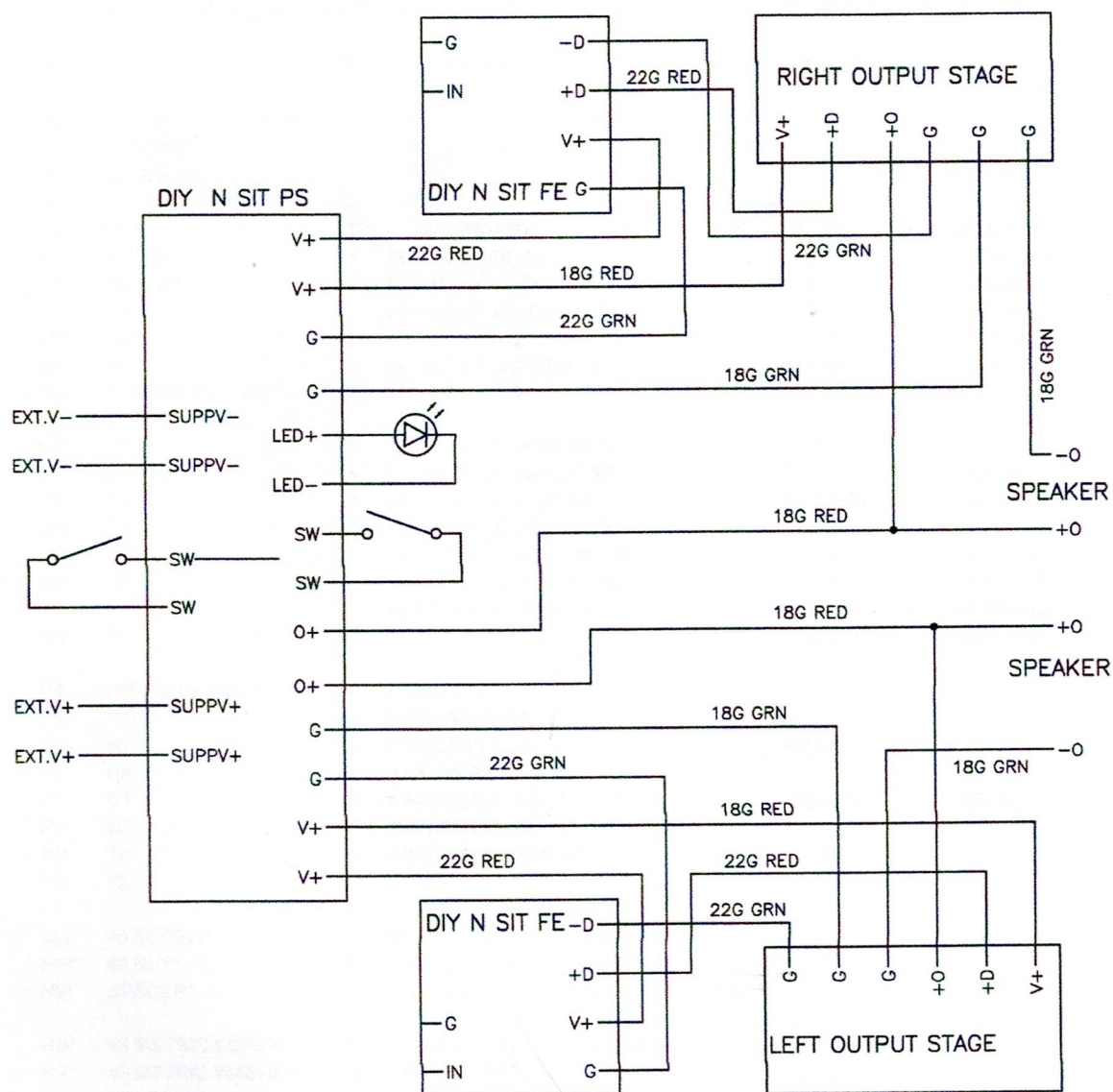


Here is the wiring diagram showing the wiring between components:



Conclusion

So here we are. With a little luck, this offering of 90 N channel Sony VFET amplifiers at www.diyAudio will be as successful as the P channel version.

It is planned that there will also be kits for those who already have the 2SK82 or 2SJ28, and a new (different) kit for those who have the 2SK60 or 2SJ18 VFETs.

Enjoy.