

Fig.2. The experimental amplifier circuit diagram function in three modes, A, B and non-switching B.

timebase 2ms full scale.

